

# **LTS defense assignments -**

## **Week 2.1 (Tuesday) in**

## **Tellegen Hall**

In this lab in week 2.1, you will analyze and simulate three assignments using LTS defense as follows:

- A second-order circuit (a series RLC circuit)
- AC-DC rectifier using one diode
- Simulation of the nodal analysis circuit (which you had in the Python assignment)

### **Preparation:**

- Make sure that you have the LTS defense installed on your laptop (**note:** do not forget to bring your laptop to EWI)
  - Installation URL link: <https://www.analog.com/en/design-center/design-tools-and-calculators/lts-defense-simulator.html>

- There are a number of LTSpice tutorial available on internet. (As an example, you can optionally use<sup>1</sup> <http://denethor.wlu.ca/ltspace/>)
- Always provide your simulation results with a non-black preferably white background waveform (see <https://spiceman.net/ltspace-initial-setting/>, in Tools > Control Panel > "Waveforms" in Color Scheme - Color Palette Editor. Go to "selected item", click on Background > then set R & G and B at 255)

## Assignment 1: Second-order circuit (a series RLC circuit)

You became familiar with the Second-order circuit (a series RLC circuit) in the EE1C11 course in Q1.

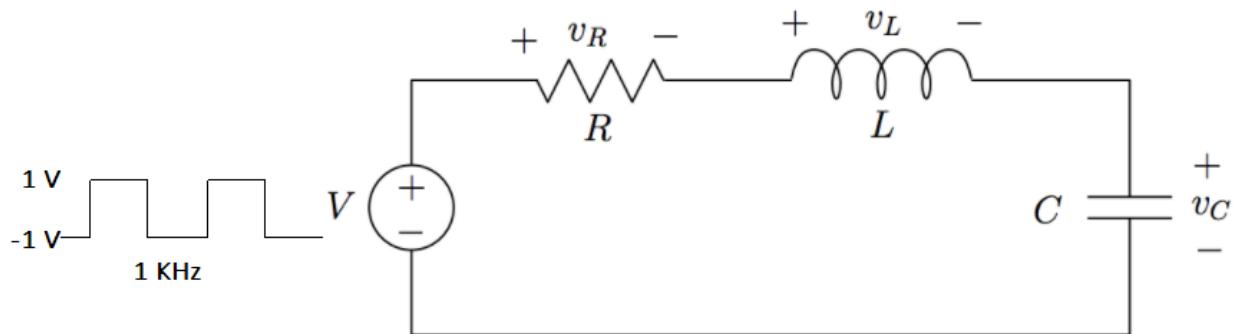


Fig 1. Series RLC circuit with a square wave voltage source.

Consider the RLC circuit shown in Figure 1 ( $C=100$  nF,  $L=1$  mH).

- Calculate the value of the resonant frequency  $\omega_0$  (rad/s) and  $f_0$  (Hz).
- Calculate the value for the resistance  $R$  where the damping factor ( $\alpha$ ) is equal to  $\omega_0$  (rad/s).
- Calculate the value for the resistance  $R$  where the damping factor ( $\alpha$ ) is equal to  $0.25 * \omega_0$  (rad/s).
- Calculate the value for the resistance  $R$  where the damping factor ( $\alpha$ ) is equal to  $5 * \omega_0$  (rad/s).

Start to create and simulate the RLC circuit in LTSpice. The input voltage is a square wave (Pulse) with a peak-to-peak voltage of 2 V (-1 to +1 V) with the frequency of 1 KHz. Do not forget to connect the ground and use `.tran` for simulations.

**Attention:** Make sure you show the simulation results after five or six cycles.

<sup>1</sup> **Disclaimer:** The TUD EE programme does not take the responsibility for the content provided in the (optional) LTSpice links.

- Obtain the simulation result for the voltage across the capacitor using the value of R where the damping factor ( $\alpha$ ) is equal to  $\omega_0$  (rad/s).
- Obtain the simulation result for the voltage across the capacitor using the value of R where the damping factor ( $\alpha$ ) is equal to  $0.25\omega_0$  (rad/s).
- Obtain the simulation result for the voltage across the capacitor using the value of R where the damping factor ( $\alpha$ ) is equal to  $5\omega_0$  (rad/s).
- Compare your simulation results for the previous three cases with three different values for R (overdamped, underdamped and critically damped).
- For the underdamped case, obtain the value of the damped natural frequency  $\omega_d$ . Then, give the damped natural frequency from your simulation results. Does the damped natural frequency from your simulation results match the calculated value?

## Assignment 2: AC-DC rectifier using one diode

In this assignment, you become familiar with an AC-DC rectifier. The rectifier converts the AC input signal to an output DC signal.

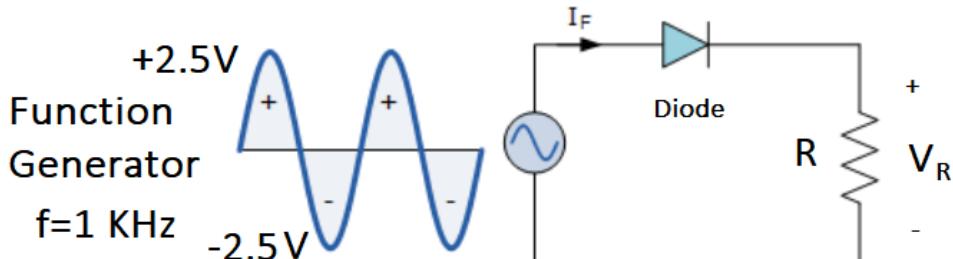


Fig 2. AC-DC rectifier using one diode and a resistor

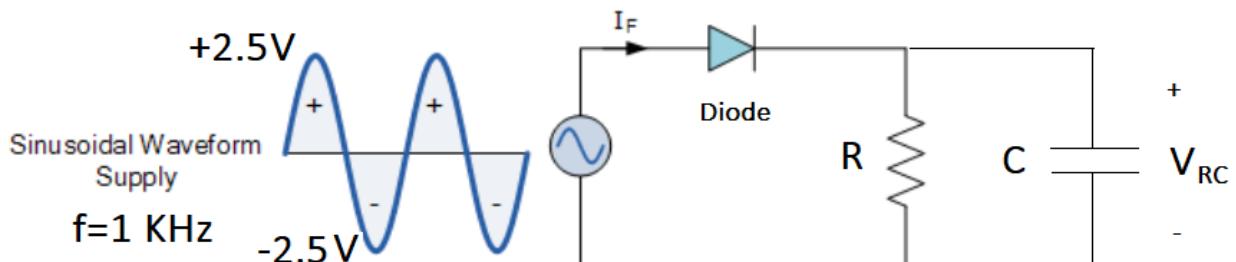


Fig 3. AC-DC rectifier using one diode, a resistor, and a capacitor.

Figure 2 shows an AC-DC rectifier using one diode and a resistor ( $R=10\text{ k}\Omega$ ). Taking into account the input AC voltage (5 V peak-to-peak), draw the output DC voltage  $V_R$  where the diode is 1N4148 type.

Figure 3 shows an AC-DC rectifier using one diode, a resistor ( $R=10\text{ k}\Omega$ ), and a capacitor ( $C=100\text{ nF}$ ). Taking into account the input AC voltage (5 V peak-to-peak), draw the output voltage  $V_{RC}$  where the 1N4148 diode is used.

Start to create and simulate the circuits in LTSpice. The input voltage is an AC sinusoidal wave with a peak-to-peak voltage of 5 V (-2.5 to +2.5 V) with the frequency of 1 KHz.

- Obtain the simulation results for  $V_R$  in the circuit shown in Fig. 2. Does the simulation result match your drawings?
- Obtain the simulation results for  $V_{RC}$  in the circuit shown in Fig. 3. What is the impact of the capacitor on the output DC voltage?
- Repeat the simulations where you use a  $20\text{ k}\Omega$  resistor (instead of a  $10\text{ k}\Omega$  resistor). What is the impact of the value of the resistance on the output DC voltage?