

# End-of-term exam

## EE1C1 “Linear Circuits A”

Place: Dreibelweg Exam Hall 2

Date: 07-11-2025

Time: 9:00 – 11:00


- This exam consists of 4 exercises.
- Each exercise accounts for **10 points**; the total number of points to be obtained is **40**. The exam grade is obtained by dividing the total number of points by 4, rescaling linearly the result to the 1-10 scale and rounding off to 1 decimal/to half-a-point, after accounting for the bonus points.
- **Each exercise must be solved on a separate double-sheet.** Writing more solutions on the same sheet may result in only one of the solutions being graded!
- Indicate your name and study number on **each** submitted sheet. **You must hand in (blank) signed sheets even for the exercises that you do not handle.**
- Students benefitting of the “Extra Time” (ET) rule are entitled to a 20 minutes extension of their exam provided they produce the relevant supporting document.
- Should any question not be completely clear, you are allowed to ask the instructors in the exam hall; the answer will be confined to rephrasing the text of the exercise such that to make it more intelligible.
- Should a part of an exercise depend on a previous result, mistakes made at a previous step will only be penalised once.
- Give your solution as completely as possible and never state numerical results without indicating how you derived them. **Simply stating numerical results will yield no points.**
- **When requested, fill in the measure units for all calculated quantities.** This holds for intermediate results but definitely for the final ones.
- Write clearly and avoid messy solutions. Should errors occur in your solution, cross the erroneous part out and give clear indications on where the correct solution resumes.
- For this exam you are allowed to use:
  - i. a simple calculator – programmable and graphic calculators are explicitly prohibited;
  - ii. a handwritten, double-sided A4 sheet with formulas.
- The text of this exam is offered only in English. Inasmuch as possible, instructors will assist you with the Dutch translation of formulations that you may have difficulties to understand.

**The Linear Circuits team wishes you a lot of success!**

## - Take a new double-sheet -

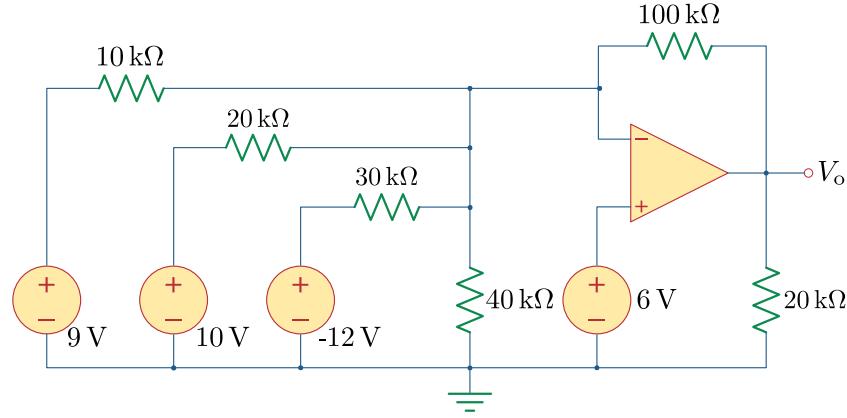
### Exercise 1

Consider the circuit in the figure below, in which the op amp is taken to be ideal:



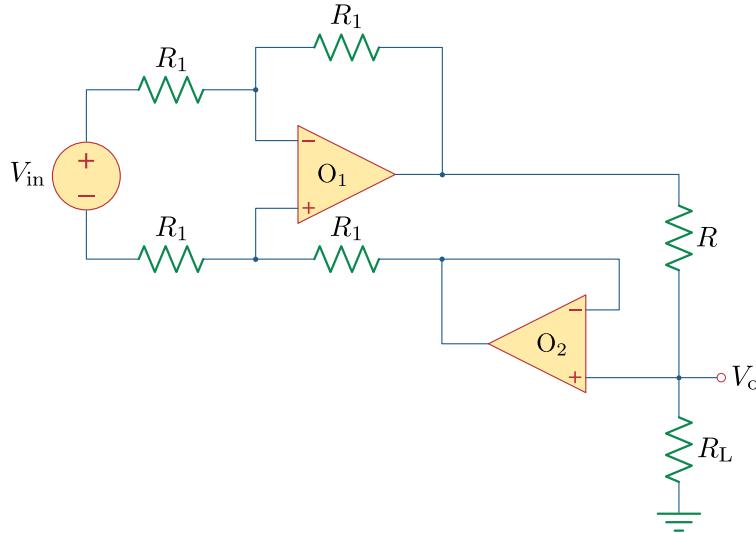a) Calculate the output voltage  $V_o$  for the indicated input voltages. (5 points)

Now consider the circuit in the figure below, in which the op amps  $O_1$  and  $O_2$  are both taken to be ideal:



b) Calculate the output voltage  $V_o$  as a function of the input voltage  $V_{in}$ . (5 points)

*Hints:* (i) Recall that the terminal input current is always zero for ideal op amps.  
(ii) Examine the subcircuit comprising op amp  $O_2$  and recognise it as a voltage follower  
(iii) Avoid applying KCL at the output terminal of an op amp.

***Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.***

## Solution

### Sub-point (a)

For ideal op-amp: Both input terminals of the op-amp have the same voltage and zero input currents.

$$1- V^- = V^+ = 6V$$

$$2- i^- = i^+ = 0A$$

3- Applying KCL at the -ve input terminal of the op-amp yields:

$$(6 - 9)/10 + (6 - 10)/20 + (6 + 12)/30 + (6 - V_o)/100 + (6 - 0)/10 = 0$$

$$V_o = 31V$$

### Sub-point (b)

For ideal op-amps: Both input terminals of the op-amp have the same voltage and zero input currents.

$$1- V^- = V^+$$

$$2- i^- = i^+ = 0A$$

3- Applying KVL at the input terminals of O1 the op-amp yields:

$$I_{in} = V_{in} / 2R_1 = (V_x - V_z) / R_1 = - (V_x - V_y) / R_1$$

$$\therefore (V_x - V_z) = V_{in} / 2 \quad \text{----- ①}$$

$$\text{And } (V_y - V_x) = V_{in} / 2 \quad \text{----- ②}$$

$$V_y = V_o \quad \text{----- ③}$$

$$\text{Also, } (V_z - V_o) / R = V_o / R_L \quad \text{----- ④}$$

$$\text{From ①, ②, ③ and ④ : } V_{in} = V_o - V_z = -V_o R / R_L \quad \text{----- ⑤}$$

$$V_o / V_{in} = - R_L / R$$

## - Take a new double-sheet -


### Exercise 2

The voltage at the terminals of a  $100 \text{ mH}$  inductor has the expression:

$$v_L(t) = 0.1e^{-t} + 0.2t \text{ (V)}$$

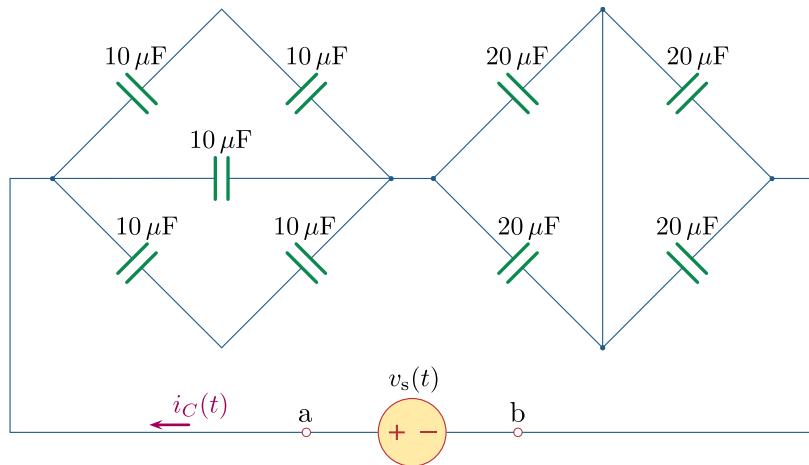a) By knowing that  $i_L(0) = 0 \text{ A}$ , determine the expression of the current  $i_L(t)$  at  $t = 2 \text{ s}$ . (2 points)

Consider the circuit in the figure below:




b) Calculate the equivalent capacitance  $C_{\text{eq}}$  at the terminals a–b. (2 points)

c) By knowing that the voltage source has the expression

$$v_s(t) = 3t^3 + 2t^2 + 3 \text{ (V)}$$

calculate the current  $i_C(t)$  through the capacitor network at  $t = 2 \text{ s}$ . (2 points)

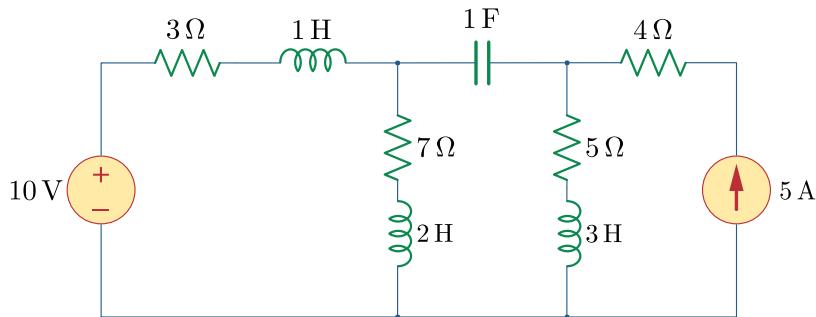Now consider the new circuit in the figure below, **operating under DC steady state conditions**:



d) Calculate the total energy  $w_{\text{tot}}$  stored in the capacitor and the three inductors. (4 points)

**Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.**

## Solution

### Sub-point (a)

The inductor current follows by integrating the voltage at its terminals as:


$$\begin{aligned} i_L(t) &= \frac{1}{0.1} \int_{\tau=0}^t (0.1e^{-\tau} + 0.2\tau) d\tau + i(0) = -e^{-t} + 1 + t^2 \\ &= -e^{-t} + t^2 + 1 \text{ (A)} \end{aligned}$$

where the initial condition that  $i_L(0) = 0$  A was also accounted for. By filling in the time  $t = 2$  s, the relevant current becomes

$$i_L(2) = 4.87 \text{ (A)}$$
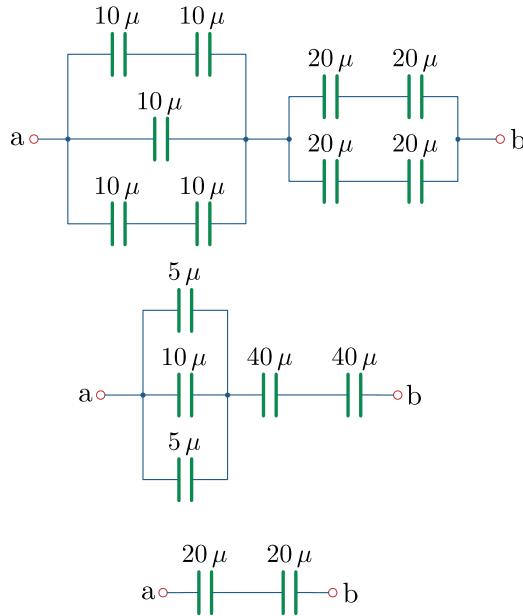
### Sub-point (b)

The given circuit is successively transformed as



that, clearly, yields the equivalent capacitance

$$C_{\text{eq}} = 10 \mu\text{F}$$

### Sub-point (c)

The capacitor current follows from the voltage at its terminal via time-differentiation as


$$i_C(t) = C \frac{dv_s}{dt} = 10 \cdot 10^{-6} (9t^2 + 4t) \text{ (A)}$$

By filling in the time  $t = 2$  s, the relevant current becomes

$$i_C(2) = 440 \mu\text{A}$$
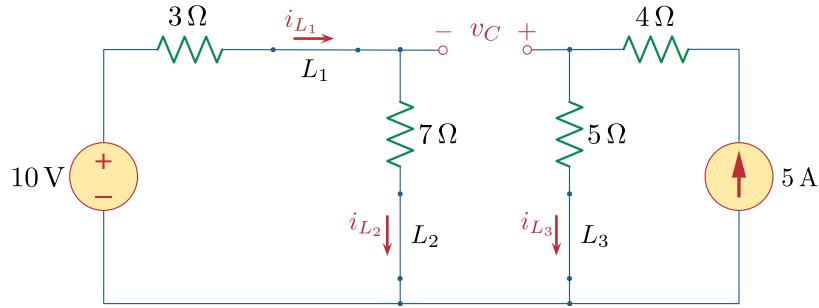
### Sub-point (d)

Under DC conditions, the circuit becomes:



Based on this schematic, the calculation of the needed currents/voltages is elementary:

$$i_{L_1} = i_{L_2} = \frac{10}{3+7} = 1 \text{ (A)}$$

$$i_{L_3} = 5 \text{ A}$$

$$v_C = 5 \times i_{L_3} - 7 \times i_{L_2} = 5 \times 5 - 7 \times 1 = 18 \text{ (V)}$$


These quantities are then used in the expressions of the energy stored in the relevant circuit elements, the total energy being

$$\begin{aligned} w_{\text{tot}} &= \frac{Cv_C^2}{2} + \frac{L_1 i_{L_1}^2}{2} + \frac{L_2 i_{L_2}^2}{2} + \frac{L_3 i_{L_3}^2}{2} \\ &= \frac{1 \times 18^2}{2} + \frac{1 \times 1^2}{2} + \frac{2 \times 1^2}{2} + \frac{3 \times 5^2}{2} = 201 \text{ (J)} \end{aligned}$$

## - Take a new double-sheet -
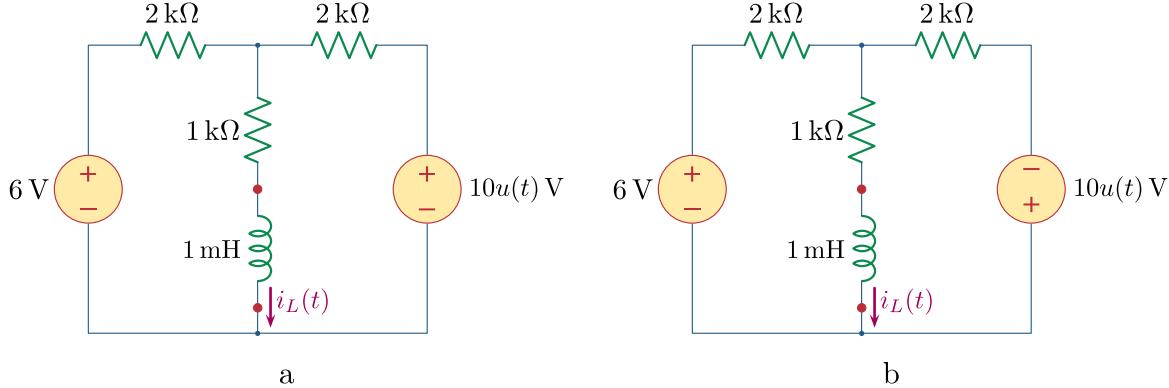
### Exercise 3

Consider the circuit in subfigure (a) of the figure below:




- Calculate the value of the current  $i_L(0^+)$ . (2 points)
- Calculate the value of the current  $i_L(\infty)$ . (2 points)
- Calculate the circuit's time constant  $\tau$ . (2 points)
- Determine the expression of the current  $i_L(t)$  for  $t > 0$ . (1 point)

Assume now that the polarity of the  $10u(t)$  voltage source is reversed, as in subfigure (b).

- Select which **one** of the following statements applies: (i) only the time constant  $\tau$  will change; (ii) only the value of the current  $i_L(\infty)$  will change; (iii) both parameters will change; (iv) none of the two parameters will change. (1 point)

*Hint: Please write down the statement that you deem correct, and justify briefly your choice (no points will be granted if no justification is provided).*

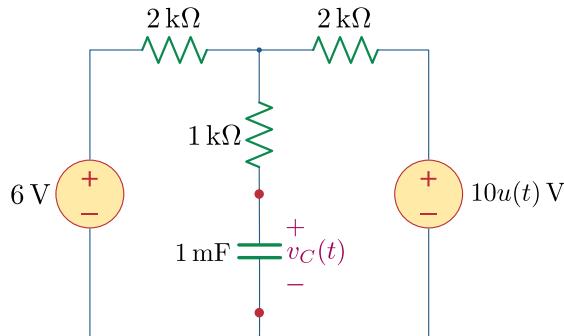Consider now the circuit in the figure below, in which the inductance was replaced in the original circuit via a capacitance.




- Calculate the new time constant  $\tau_C$ . (2 points)

**Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.**

## Solution

### Sub-point (a)

The schematic for  $t < 0$  is

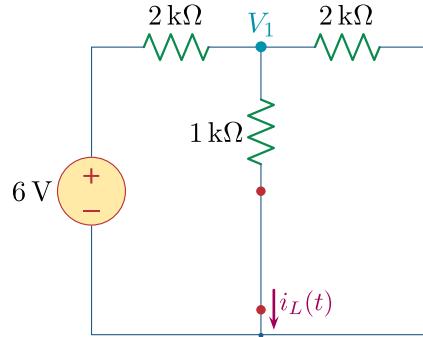

where use was made of the fact that the source at the right has the value zero (short-circuit) for  $t < 0$ . It then follows consecutively that

$$R_{\parallel} = 1\text{k} \parallel 2\text{k} = \frac{1\text{k} \cdot 2\text{k}}{1\text{k} + 2\text{k}} = \frac{2}{3}(\text{k}\Omega)$$

$$V_1 = \frac{R_{\parallel}}{2\text{k} + R_{\parallel}} 6 = \frac{\frac{2}{3}\text{k}}{2\text{k} + \frac{2}{3}\text{k}} 6 = \frac{3}{2}(\text{V})$$


$$i_L(0^-) = \frac{V_1}{1\text{k}} = \frac{\frac{3}{2}}{1\text{k}} = \frac{3}{2}(\text{mA})$$

By now applying the continuity of  $i_L(t)$  at  $t = 0$ , it immediately follows that

$$i_L(0^-) = i_L(0^+) = \frac{3}{2} \text{mA}$$
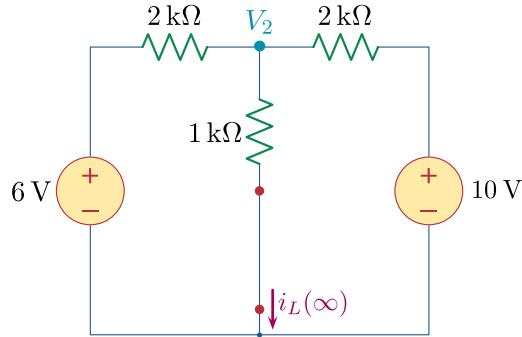
### Sub-point (b)

The schematic for  $t \rightarrow \infty$  is



By now applying nodal analysis at the node 2 it follows that


$$\frac{V_2 - 6}{2\text{k}} + \frac{V_2}{1\text{k}} + \frac{V_2 - 10}{2\text{k}} = 0 \implies 4V_2 = 16 \implies V_2 = 4\text{V}$$

and, thus

$$i_L(\infty) = \frac{V_2}{1\text{k}} = 4\text{mA}$$
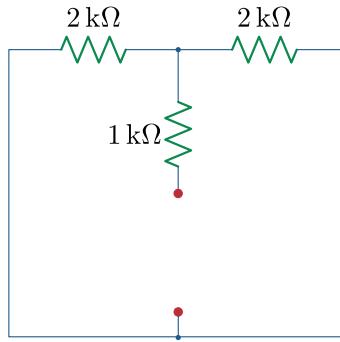
### Sub-point (c)

The passivised circuit at the inductance's terminals is



It is then clear that the Thévenin resistance is

$$R_{\text{Th}} = 1 \text{ k} + (2 \text{ k} \parallel 2 \text{ k}) = 1 \text{ k} + 1 \text{ k} = 2 \text{ (k}\Omega\text{)}$$

that, in turn, yields the time constant

$$\tau = \frac{L}{R_{\text{Th}}} = \frac{1 \text{ m}}{2 \text{ k}} = 0.5 \text{ (\mu s)}$$

### Sub-point (d)

By now collecting all partial results in the initial-final values formula, the requested current is

$$i_L(t) = 4 + \left(\frac{3}{2} - 4\right) e^{-t/0.5\mu} = 4 - \frac{5}{2} e^{-2 \cdot 10^6 t} \text{ (mA)}$$

### Sub-point (e)

Since the only change in the circuit was flipping the specified source, it is evident that **the passivised circuit at the inductance's terminals will not change** and, thus, the time circuit's constant cannot change. However, flipping the source will definitely influence the final value. Consequently, the only applicable statement is: **only the value of the current  $i_L(\infty)$  will change**.

$$v_L(\infty) = -1 \text{ mA}$$

*Note:* By employing the same reasoning as the one used at subpoint (b), it is an easy exercise to show that, in this case,

### Sub-point (f)


By replacing the inductance by a capacitance in the original circuit, **the passivised circuit at the reactive element's terminals will again remain the same**. As a result, calculating the requested time constant is immediate, its value being

$$\tau_C = CR_{\text{Th}} = 1 \text{ m} \cdot 2 \text{ k} = 2 \text{ (s)}$$

## - Take a new double-sheet -
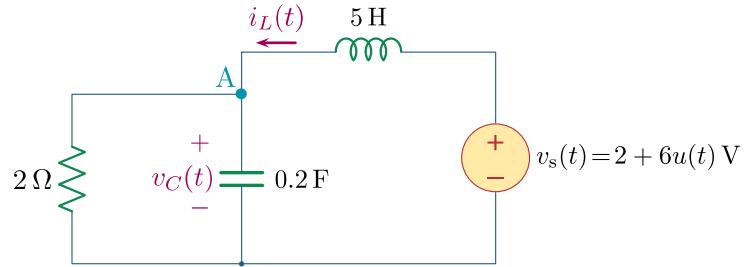
### Exercise 4

Consider the circuit in the figure below:



- a) Calculate  $v_C(0^+)$  and  $i_L(0^+)$ . (1 point)
- b) Calculate  $v_C(\infty)$  and  $i_L(\infty)$ . (1 point)
- c) Apply the KCL at node A to derive an expression for the integro-differential equation for  $v_C(t)$  for  $t > 0$ . (2 points)
- d) Derive the characteristic equation and motivate if the circuit is overdamped, critically damped, or underdamped (no points will be granted if no justification is provided). (2 points)
- e) Determine  $v_C(t)$  for  $t > 0$ . (4 points)

***Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.***

## Solution

### Sub-point (a)


In view of continuity

$$V_C(0^-) = V_C(0^+) = 2V$$

$$I_L(0^-) = I_L(0^+) = \frac{2V}{2\Omega} = 1A$$

### Sub-point (b)

The schematic for  $t > 0$  is

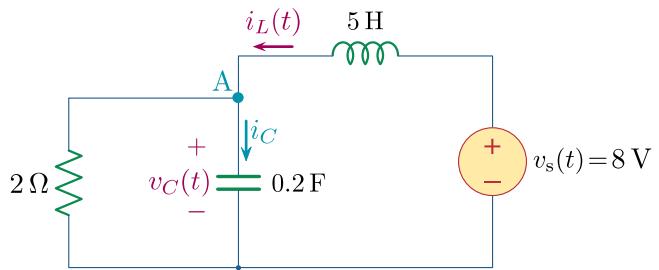

AT  $t \rightarrow \infty$  THE VOLTAGE SOURCE PROVIDES  $V_s = 8V$  SO

$$V_C(\infty) = 8V \text{ AND } I_L(\infty) = \frac{8V}{2\Omega} = 4A$$

### Sub-point (c)

$$i_C(t) + i_R(t) = i_L(t)$$

$$C \frac{dV_C(t)}{dt} + \frac{V_C(t)}{R} = i_L(t)$$

$$C \frac{dV_C(t)}{dt} + \frac{V_C(t)}{R} = \frac{1}{L} \int_{0}^t V_L(\tau) d\tau + I_L(0^+) = \frac{1}{L} \int_{0}^t [V_s - V_C(\tau)] d\tau + 1$$

$$C \frac{d^2V_C(t)}{dt^2} + \frac{1}{R} \frac{dV_C(t)}{dt} + \frac{1}{LC} V_C(t) = \frac{V_s}{L} - \frac{V_C(t)}{L} \Rightarrow \boxed{\frac{d^2V_C(t)}{dt^2} + \frac{1}{RC} \frac{dV_C(t)}{dt} + \frac{1}{LC} V_C(t) = \frac{V_s}{LC}}$$

### Sub-point (d)

$$\underline{s^2 + \frac{s}{RC} + \frac{1}{LC} = 0} \quad s^2 + \frac{s}{0.4} + 1 = 0 \quad s^2 + 2.5s + 1 = 0$$

$$s_{1,2} = \frac{-2.5 \pm \sqrt{625-4}}{2}$$

$$s_1 = -2 \quad s_2 = -0.5$$

OVERDAMPED

(ROOTS DISTINCT AND REAL)

Sub-point (e)

GENERAL SOLUTION FOR  $V_C(t)$  is  $V_C(t) = A e^{-2t} + B e^{-0,5t} + V_C(\infty)$

AT  $t=0^+$   $V_C(0^+) = A + B + 8 = 2 \rightarrow A + B = -6$

$$\frac{dV_C(t)}{dt} = -2A e^{-2t} - 0,5B e^{-0,5t}$$

$$\text{AT } t=0 \quad \frac{dV_C(t)}{dt} = \frac{I_C}{C} = \frac{I_L - I_R}{C} = \frac{1}{C} (I_L(0) - I_R(0^+)) =$$

$$= \frac{1}{C} \left( 1 - \frac{V_C(0^+)}{R} \right) = \frac{1}{C} \left( 1 - \frac{2}{2} \right) = 0 \quad \text{so} \quad 0 = -2A - 0,5B$$

$$\begin{cases} A + B = -6 \\ 0 = -2A - 0,5B \end{cases} \quad \begin{cases} A - 4A = -6 \\ B = -4A \end{cases} \quad \begin{cases} -3A = -6 \rightarrow A = 2 \\ B = -8 \end{cases}$$

$$V_C(t) = 2e^{-2t} - 8e^{-0,5t} + 8V$$

$$\text{FINALLY } I_C(t) = C \frac{dV_C(t)}{dt} = 0,2 \left( 2(-2)e^{-2t} - 8(-0,5)e^{-0,5t} \right) =$$

$$i_C(t) = \boxed{-0,8e^{-2t} + 0,8e^{-0,5t} A}$$