

## Mid-term

### EE1C2 “Linear Circuits B”

Place:

Date:

Time:

- This exam consists of 4 exercises.
- Each exercise accounts for **10 points**; the total number of points to be obtained is **40**. The exam grade is obtained by dividing the total number of points by 4, rescaling linearly the result to the 1-10 scale and rounding off to 1 decimal.
- **Each exercise must be solved on a separate double-sheet.** Writing more solutions on the same sheet may result in only one of the solutions being graded!
- Indicate your name and study number on **each** submitted sheet. **You must hand in (blank) signed sheets even for the exercises that you do not handle.**
- Students benefitting of the “Extra Time” (ET) rule are entitled to a 20 minutes extension of their exam provided they produce the relevant supporting document.
- Should any question not be completely clear, you are allowed to ask the instructors in the exam hall; the answer will be confined to rephrasing the text of the exercise such that to make it more intelligible.
- Should a part of an exercise depend on a previous result, mistakes made at a previous step will only be penalised once.
- Give your solution as completely as possible and never state numerical results without indicating how you derived them. **Simply stating numerical results will yield no points.**
- **When requested, fill in the measure units for all calculated quantities.** This holds for intermediate results but definitely for the final ones.
- Write clearly and avoid messy solutions. Should errors occur in your solution, cross the erroneous part out and give clear indications on where the correct solution resumes.
- For this exam you are allowed to use:
  - i. a simple calculator – programmable and graphic calculators are explicitly prohibited;
  - ii. a handwritten, double-sided A4 sheet with formulas.
- The text of this exam is offered only in English. Inasmuch as possible, instructors will assist you with the Dutch translation of formulations that you may have difficulties to understand.

**The Linear Circuits team wishes you a lot of success!**

Summary of Bode straight-line magnitude and phase plots.


Factor	Magnitude	Phase
$K$	$20 \log_{10} K$	$0^\circ$
$(j\omega)^N$	$20N \text{ dB/decade}$	$90N^\circ$
$\frac{1}{(j\omega)^N}$	$-20N \text{ dB/decade}$	$-90N^\circ$
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N \text{ dB/decade}$	$0^\circ, \frac{z}{10}, z, 10z$
$\frac{1}{(1 + j\omega/p)^N}$	$-20N \text{ dB/decade}$	$\frac{p}{10}, p, 10p$
$\left[1 + \frac{2j\omega\zeta}{\omega_0} + \left(\frac{j\omega}{\omega_0}\right)^2\right]^N$	$40N \text{ dB/decade}$	$0^\circ, \frac{\omega_0}{10}, \omega_0, 10\omega_0$
$\frac{1}{[1 + 2j\omega\zeta/\omega_0 + (j\omega/\omega_0)^2]^N}$	$-40N \text{ dB/decade}$	$0^\circ, \frac{\omega_0}{10}, \omega_0, 10\omega_0$

Reproduced from C. Alexander and M. Sadiku, *Fundamentals of Electric Circuits*, 7th ed., NY: McGraw-Hill, 2021 for private use during the EE1C2-B exam, only.  
**Reproduction and dissemination, in any form, of this table is prohibited.**

## - Take a new double-sheet -

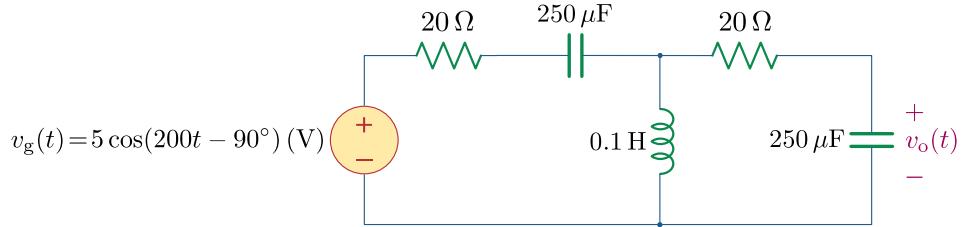
### Exercise 1

Consider the circuit in the figure below:



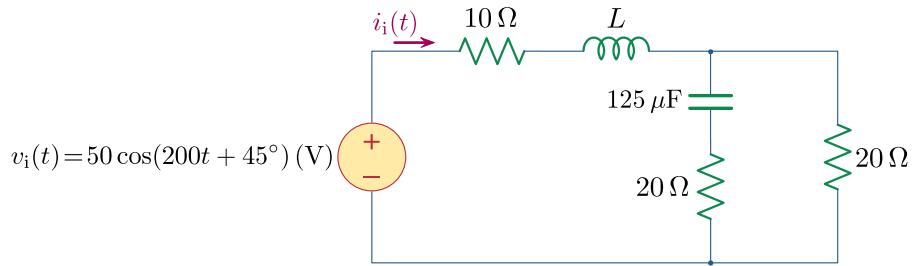a) Calculate the time-domain expression for the output voltage  $v_o(t)$ . (4 points)

Now consider the new circuit in the figure below:



b) Calculate the value of the inductance  $L$  such that to ensure that the phasor-domain input current  $\mathbf{I}_i$  is in phase with the phasor-domain input voltage  $\mathbf{V}_i$  (or, in time-domain,  $i_i(t)$  does not lead or lag  $v_i(t)$ ). (4 points)

c) Calculate the time-domain expression for the input current  $i_i(t)$ . (2 points)

*Hint: Use  $L = 0.15H$  if you did not succeed in obtaining a value for  $L$  at subpoint (b) – this is not the solution of that exercise!*

***Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.***

## - Take a new double-sheet -


### Exercise 2

Consider the following transfer function  $H(s)$  :

$$H(s) = \frac{100(s + 10)}{(s + 1)(s + 100)}$$

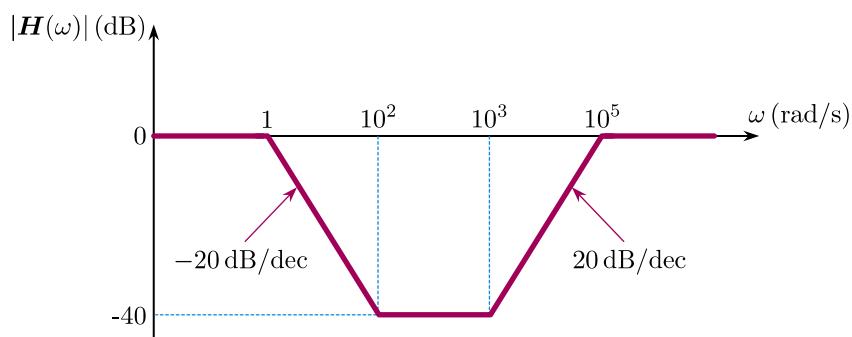a) Construct the **Bode magnitude plot** indicating for each slope the amount of dB per decade. (5 points)

Now consider the Bode magnitude plot in the figure below:




b) Find the corresponding transfer function  $H(\omega)$ . (5 points)

*Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.*

## - Take a new double-sheet -
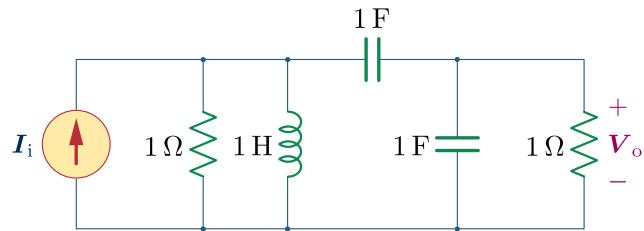
### Exercise 3


Consider the circuit in the figure below:



a) Find the transfer function  $H(\omega) = \frac{V_o}{I_i}$ . (5 points)

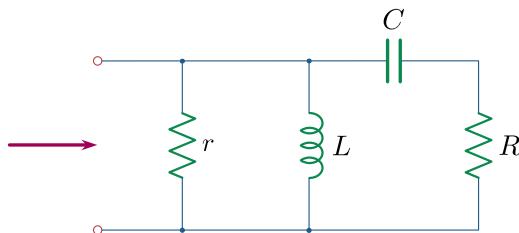b) Calculate the values of transfer function  $H(0)$  and  $H(\infty)$ . (1 point)

Now consider the new circuit in the figure below:




b) Calculate its resonant angular frequency  $\omega_0$ . (4 points)

**Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.**

## - Take a new double-sheet -

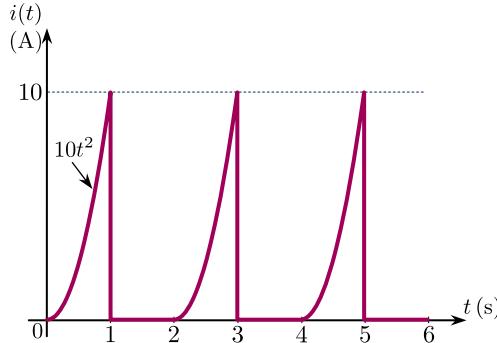
### Exercise 4

Consider the waveform in the figure below:



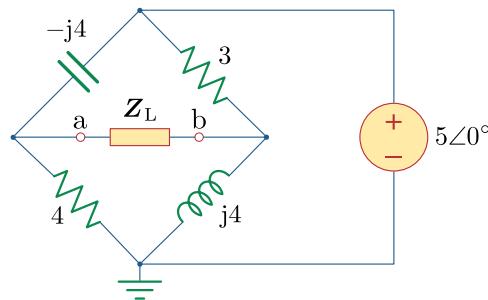a) Obtain the rms current  $I_{\text{rms}}$  of this current. (3 points)

Now consider the circuit in the figure below:



b) Calculate the Thévenin voltage  $\mathbf{V}_{\text{Th}}$  at the terminals a – b. (3 points)

*Hint: Redraw the circuit such that to make it easier to interpret.*

c) Calculate the Thévenin impedance  $\mathbf{Z}_{\text{Th}}$  at the terminals a – b. (2 points)

*Hint: Redraw the circuit such that to make it easier to interpret.*

d) Calculate the value of  $\mathbf{Z}_L$  in the circuit in order for  $\mathbf{Z}_L$  to receive maximum average power. (1 point)

*Hint: If you were not able to solve the previous subpoints, adopt an own  $\mathbf{V}_{\text{Th}}$  and  $\mathbf{Z}_{\text{Th}}$  and continue with those values.*

e) Calculate the maximum average power received by that  $\mathbf{Z}_L$ . (1 point)

***Indicate the measure units for all calculated quantities. Show all steps in your reasoning and never give numerical results without justification.***