

EE1C1 “Linear Circuits A”

Week 1.1

Francesco Fioranelli / Ioan E. Lager


Today

- The basis:
 - principles
 - terminology
 - basic quantities
- Circuit elements: independent/dependent sources
- Resistance & Ohm's law
- Summary and conclusions
- Next tasks

The basis

The basis: principles

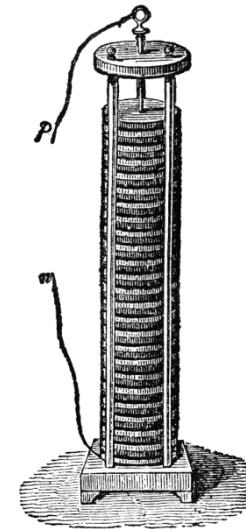- A Volta pile generates a **sustained** electrical stimulus
- More cells (“Volts”) → more “energetic” a stimulus
- Number of “Volts” = voltage
- One always needs two points for taping the energy



Volta pile
(1800)




Alessandro Antonio Volta
(1745–1827)

Voltage + 2 access points

The basis: principles

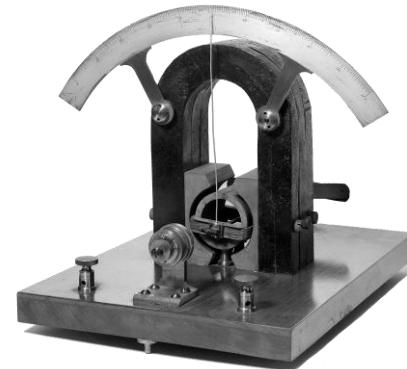- An electric current deflects a magnetic needle
- A precise method for measuring electric currents
- One always needs two points for measuring a current
- Swapping the connection gives a negative measurement



Galvanometer
(1820-1850)



Hans Christian Ørsted
(1777-1851)

Electric current + 2 access points + polarity

The basis: principles

- Two basic, easily measurable (“observable”) quantities:
voltage + (electric) current
- Pairs of access points
 - at which the supplied energy
 - between which the current

} can be unambiguously measured (predicted)

Ports

Circuit analysis = the analysis of the relations between voltages and currents at given ports

The basis: principles

Accounting for the electric charge
= a property of matter

- Two basic, easily measurable (“observable”) quantities:
voltage + (electric) current

Movement of electrical point charges and their energy


analogy with fluid dynamics (be careful, be wise)

Circuit analysis = the analysis of the relations between voltages and currents at given ports

The basis: principles

In circuit analysis we study **electric circuits**

Electrical elements (lumped elements)

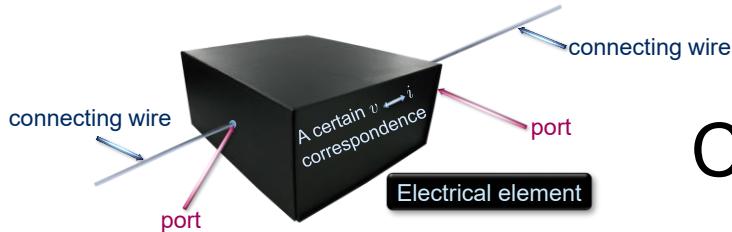

+

Connecting wires

Models

More details in “Basic concepts in circuit analysis” on Brightspace

The basis: quantities, measure units

- SI standard system:
 - length \longleftrightarrow meters (m)
 - time \longleftrightarrow second (s)
 - current \longleftrightarrow ampere (A)
- Derived quantities and units:
 - charge \longleftrightarrow $s \cdot A =$ coulomb (C)
 - electric potential \longleftrightarrow volt (V)
 - power \longleftrightarrow watt (W)
 - energy \longleftrightarrow joule (J)

The basis: electric charge & electric current

- The charge: an electrical property of sub-atomic constituents, measured in coulomb (C)
- The charge of an electron $e = -1.602 \times 10^{-19}$ C
- The electric current: a measure of the temporal variation of the electric charge, measured in ampere (A)

equal, by definition

$$i \triangleq \frac{dq}{dt}$$


$$q = \int_{t_0}^t i \, dt + q(t_0)$$

positive charges!


Only finite values!

The basis: electric charge & electric current


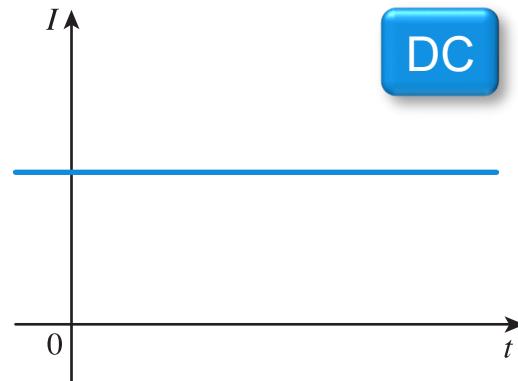
- A **direct current (dc)** is a current that remains constant with time



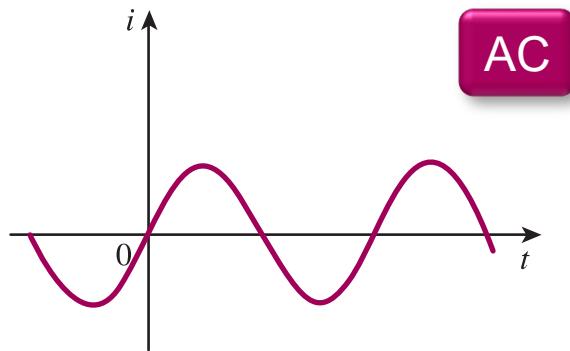- An **alternating current (ac)** is a current that varies sinusoidally with time




The basis: electric current direction

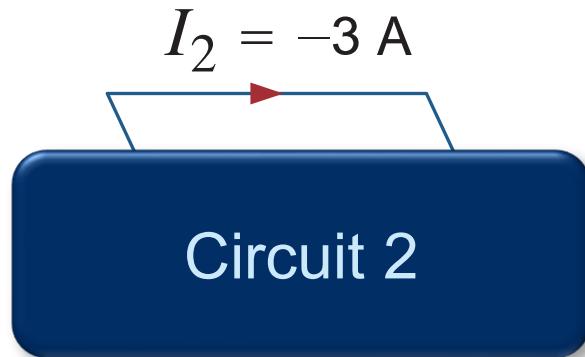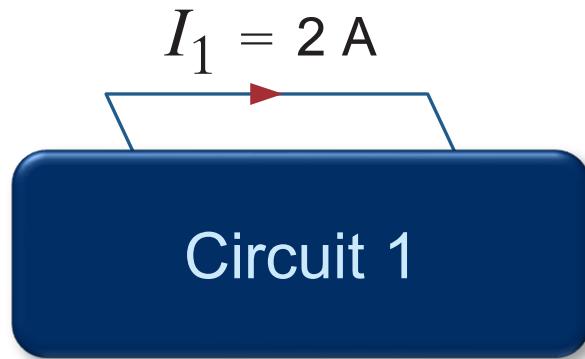

A **positive value** for the current indicates a flow in the direction of the arrow (the reference direction)


A **negative value** for the current indicates a flow in the direction opposite to the reference one

The basis: electric current direction

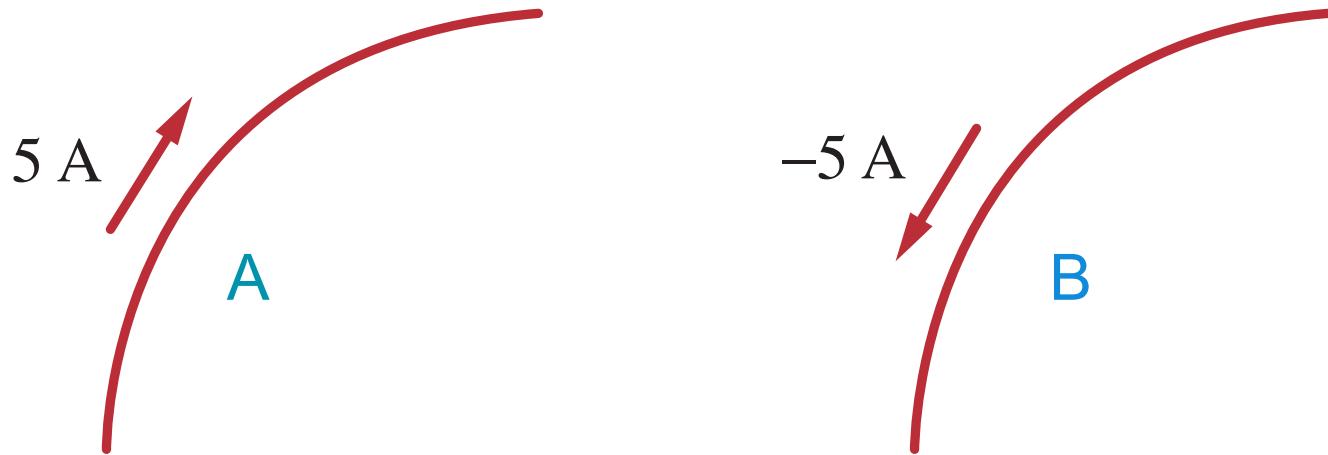

1. The current in B flows in opposite direction as in A
2. The current in B flows in the same direction as in A
3. This notation is misleading and should never be used

The basis: electric current direction

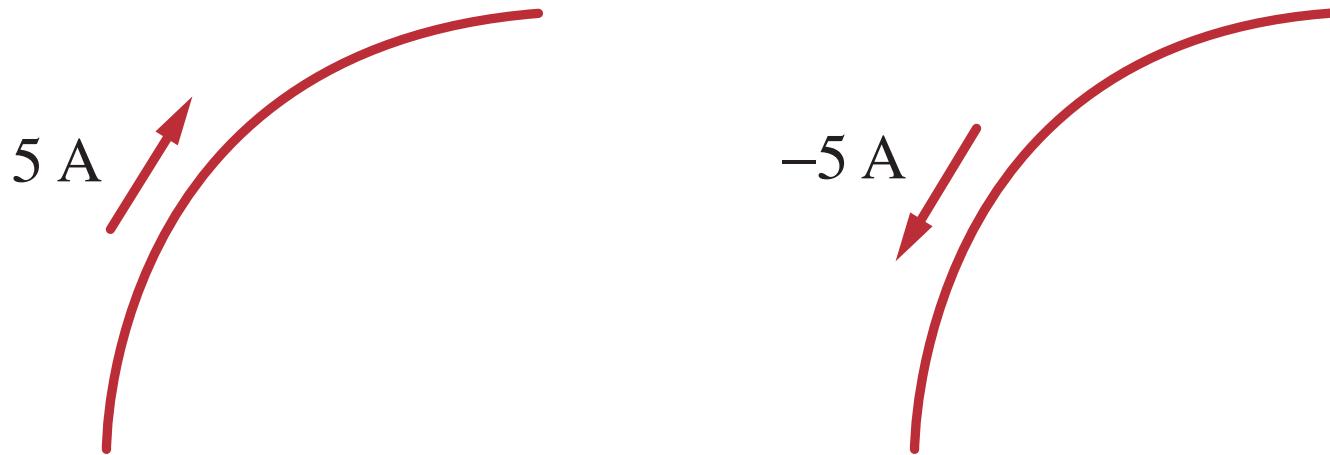

This can be a connecting wire or an electric element


The basis: potential & voltage

- The potential is the (electrical) potential energy per unit charge




$$v_{ab} \triangleq \frac{dw}{dq}$$

- The potential difference between two points is denoted as voltage

Only finite values!


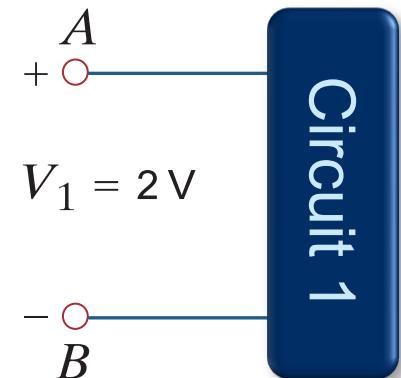


The basis: voltage direction

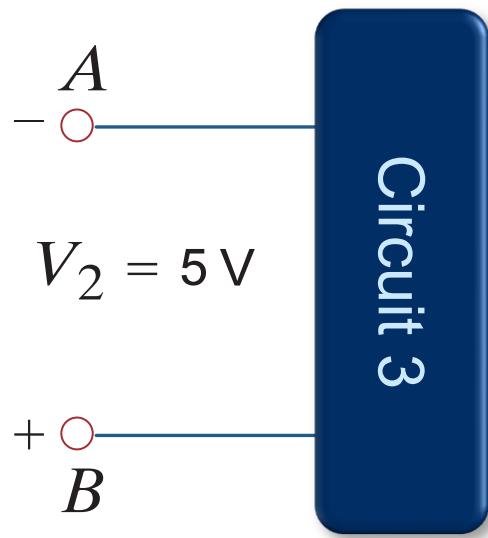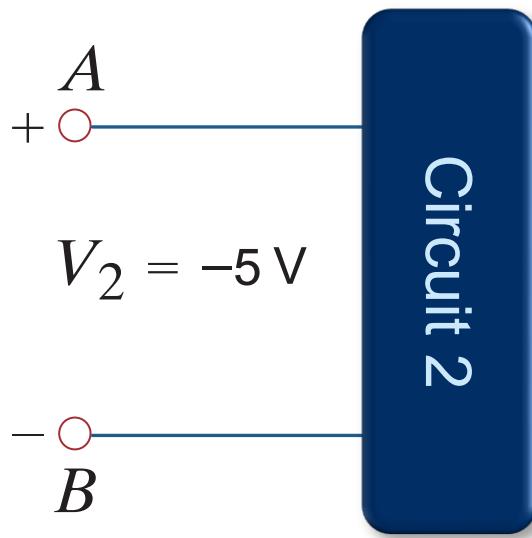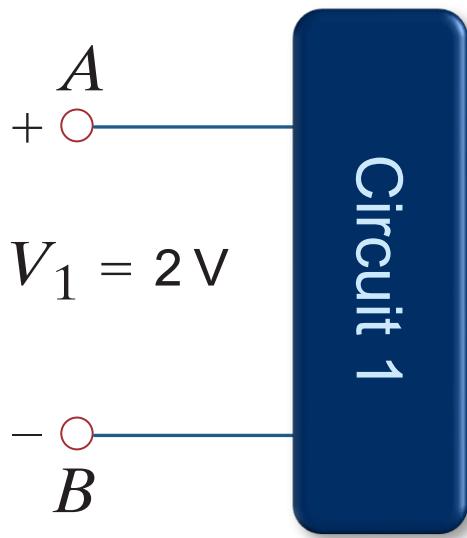


1. The voltages in circuits 1 and 3 have the same polarity
2. The voltages in circuits 1 and 3 have opposite polarities

The basis: voltage direction

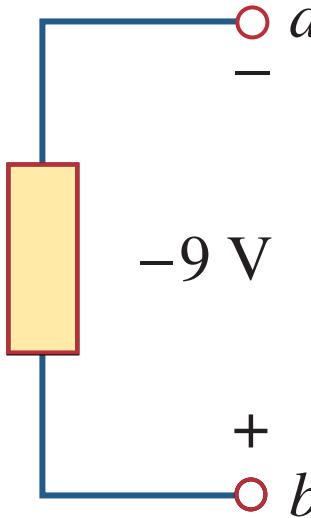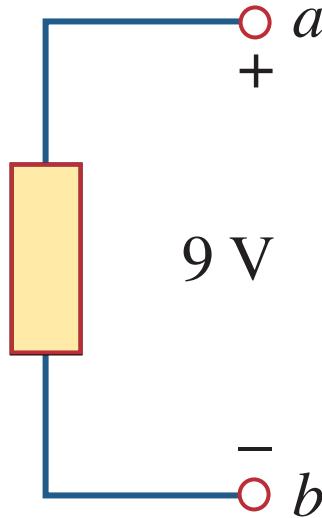

This is always an electric element!

The basis: electric current & voltage

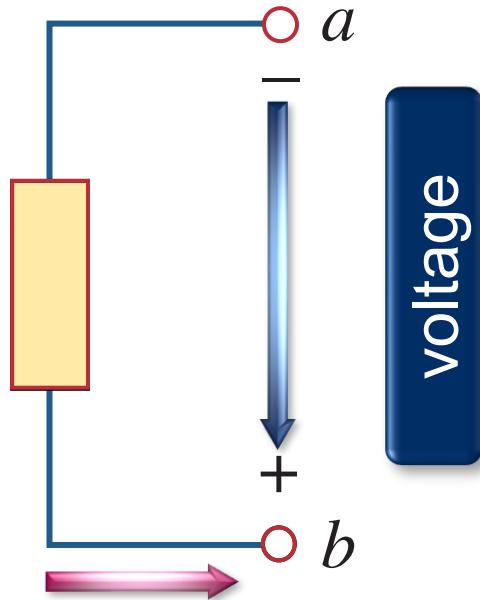



electric current

- Voltage → “across”

- Electric current → “through”

The basis: energy & power

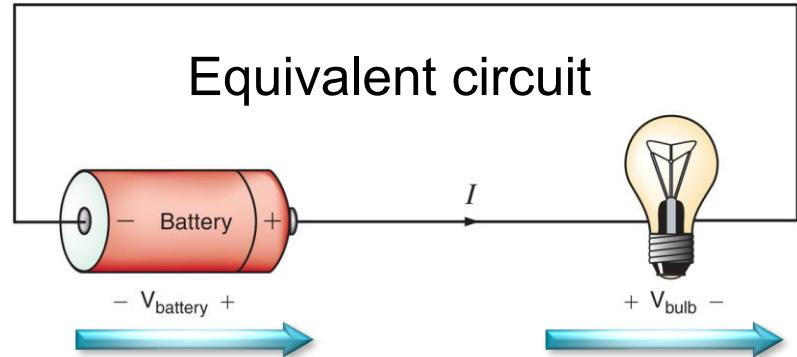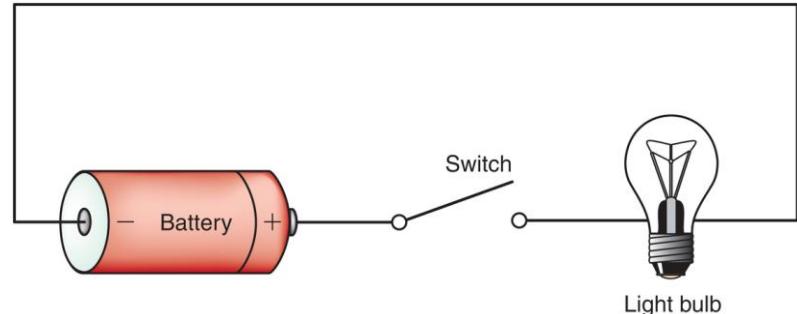- Energy is transformed
- Power is supplied to the lamp




The basis: energy & power

- How much **energy** you need for moving 120 C from B to A?

$$v_{ab} = 2V$$

$$v_{ab} \triangleq \frac{dw}{dq} = \frac{w}{q}$$

$$w = q \cdot v_{ab} = 240 \text{ J}$$

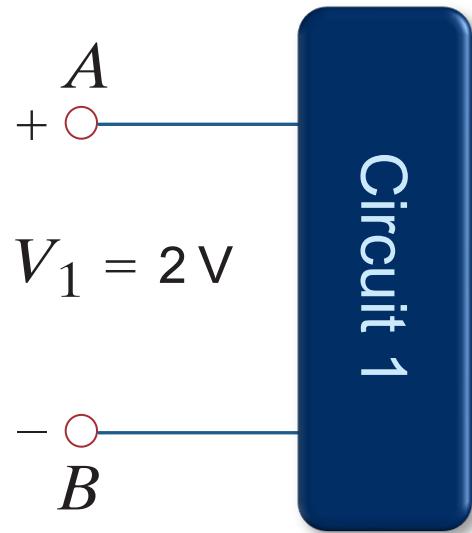

The basis: energy & power


- Power = energy / time

- Instantaneous power:
$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$



- Energy \longrightarrow power:
$$w(t) = \int_{t_0}^t p(t) dt = \int_{t_0}^t v(t)i(t) dt$$

The basis: power – passive sign convention

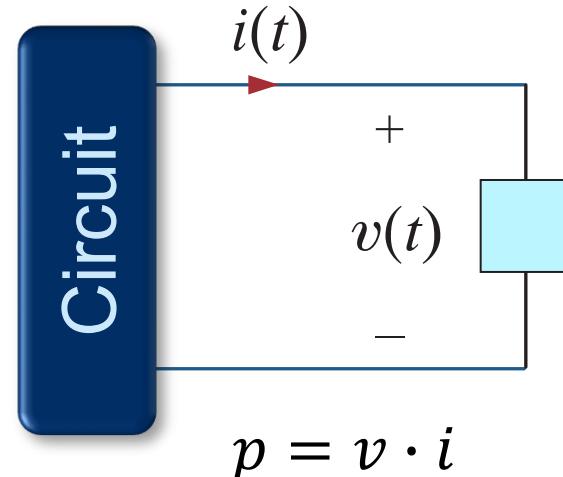- If the voltage and the current are both positive, then the **positive charges** move from a higher potential to a lower potential
- The component **absorbs** power
- Such an element is referred to as “**passive**”



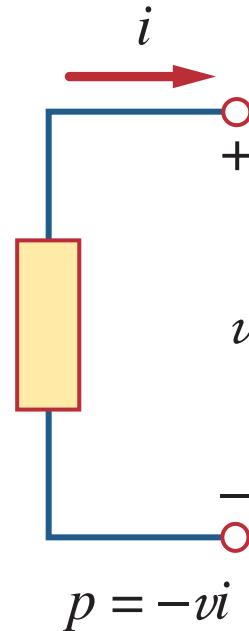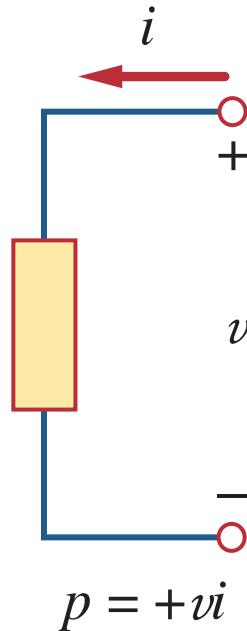
The basis: power – passive sign convention



Power is absorbed

Power is supplied

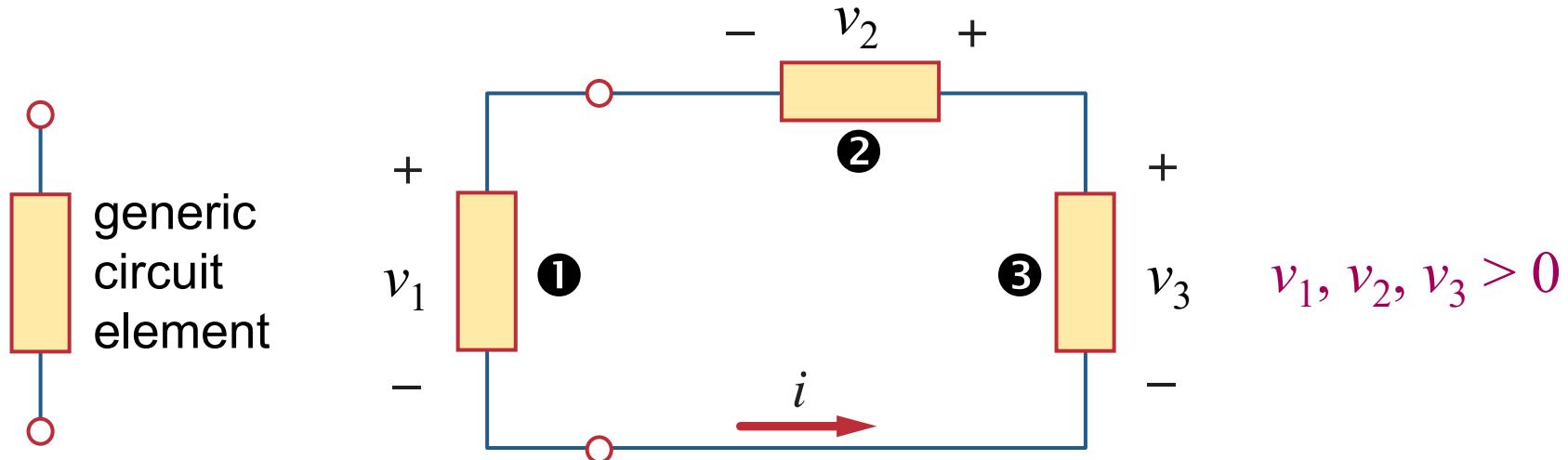The basis: power – passive sign convention




1. Element ② absorbs the power supplied by element ①
2. Element ③ absorbs the power supplied by element ①
3. None of the above

Circuit elements

Circuit elements: independent sources

- The voltage / current supplied by the source is **independent** of the voltage across / the current through it
- **Ideal situation**
- Ideal sources can supply infinite power
- A socket can be construed as a **voltage source**

Independent sources

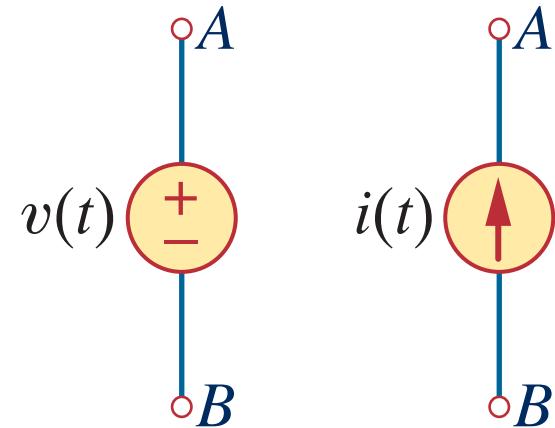


European symbols


Circuit elements: independent sources

- Passive sign convention revisited:

Positive power: $p = iv$

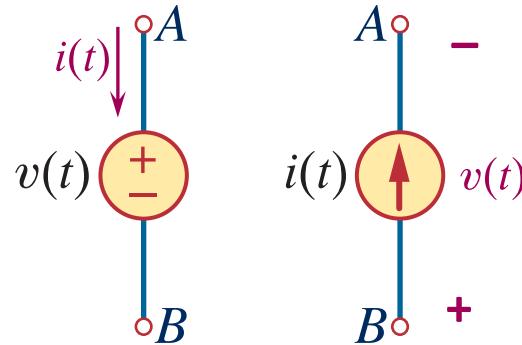

Negative power: $p = -iv$

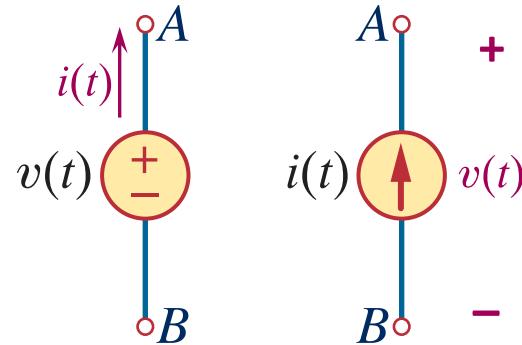


- Summarising:

- positive power \longrightarrow absorbed power \longrightarrow the device is 'driven'
- negative power \longrightarrow supplied power \longrightarrow the device 'drives'


Circuit elements: voltage-controlled sources

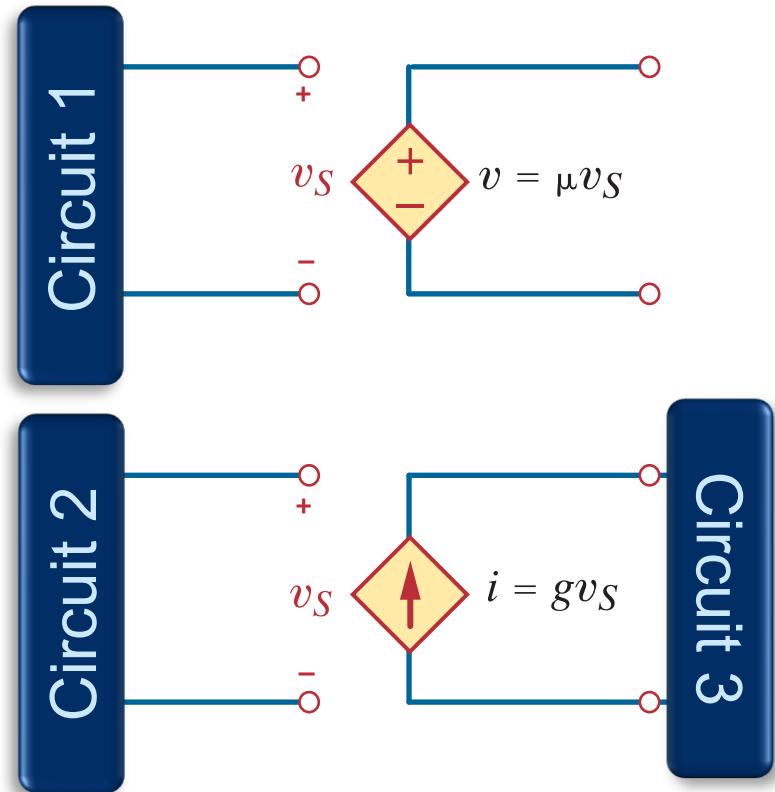- The voltage or current supplied by the source depends on the **voltage** between the source's **controlling terminals** v_S
- **Attention:** the two circuits are electrically disjoint!



Circuit elements: current-controlled sources

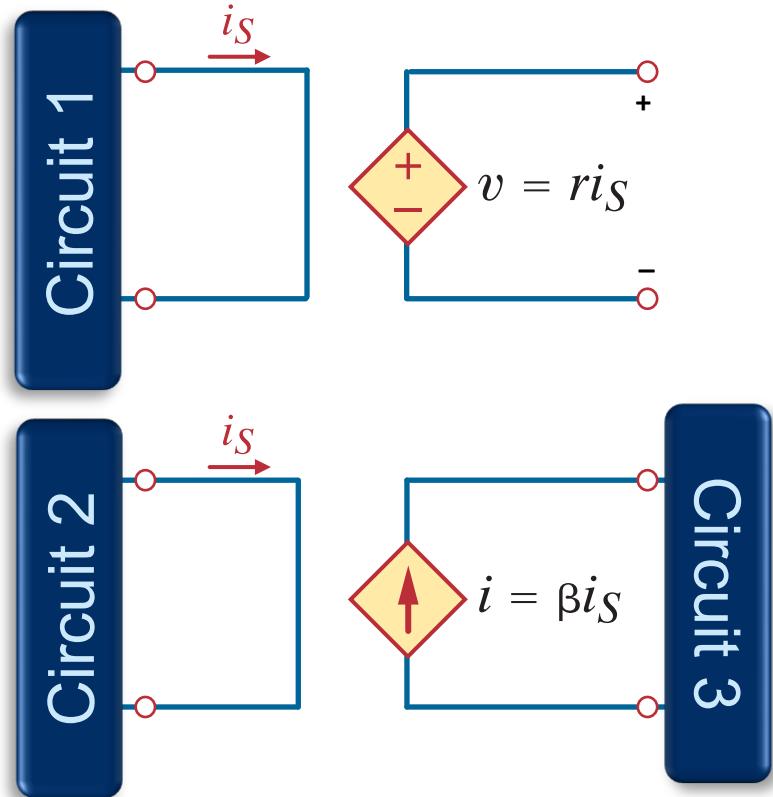- The voltage or current supplied by the source depends on the **current** flowing between the source's controlling terminals i_S
- **Attention:** the two circuits are electrically disjoint!



Resistance & Ohm's law

Resistance & Ohm's law

- Resistance = the ratio $v(t)/i(t)$ at the same instant t
- Historically: Ohm's law (1827)

$$R = \frac{v}{i}$$

- established in DC
- R is measured in ohms (Ω)
- Resistance: interpreted as an element's ability to resist the flow of electric current





Georg Simon Ohm
(1789–1854)

Resistance & Ohm's law


- For wire-like conductors: $R = \rho \frac{\ell}{A}$
 - ρ = resistivity
 - ℓ = length of the wire
 - A = cross-sectional area (uniform current distribution)

Material	Resistivity ($\Omega \cdot \text{m}$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Silicon	6.4×10^2	Semiconductor
Teflon	3×10^{12}	Insulator

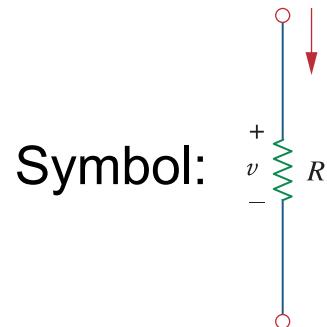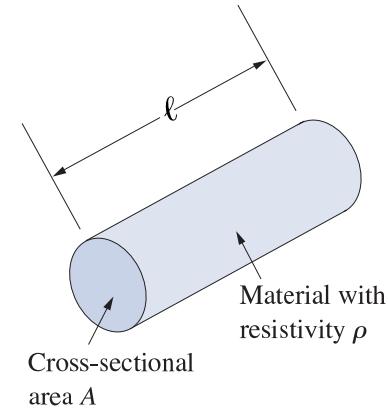


Resistance – particular situations

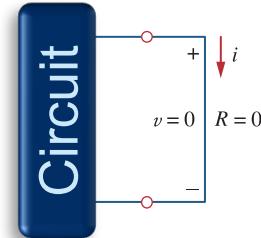- **Short circuit** = a circuit element across which the voltage is zero for any finite current
 - **book**: a circuit element with resistance approaching zero $\longrightarrow v = iR = 0$



- **Open circuit** = a part of the circuit through which the current is zero (for any finite voltage)
 - **book**: a circuit element with resistance approaching infinity
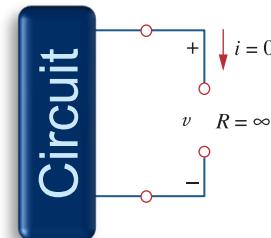
$$\longrightarrow i = \lim_{R \rightarrow \infty} \frac{v}{R} = 0$$





Resistance – derived quantities

- Conductance = reciprocal of resistance

$$G = \frac{1}{R} = \frac{i}{v}$$

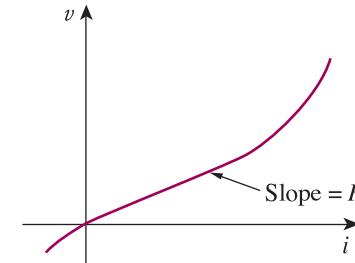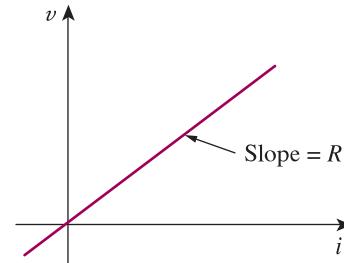- it is measured in siemens (S)
- Nonlinear resistance



Summary of the day

- The basic concepts in electric circuits:
voltage, current → charge, energy, power
- Independent / dependent sources
- Resistance & Ohm's law
- These concepts & elements will be heavily used
in the coming weeks for:
 - circuit analysis
 - circuit design

Next tasks

- Next week the lecture will be given by Francesco
 - Monday, September 9: Chapter 2 (continued)
- This week:
 - seminars tomorrow and on Friday
- Don't forget to register on MS Teams



- For your attendance
- For reviewing this lecture
- For reading the book's chapter
- For participating in the week's seminars