

EE1C1 “Linear Circuits A”

Week 1.3

Francesco Fioranelli/ Iordan E. Lager

My e-mail address: F.Fioranelli@tudelft.nl / room 20.280 (20th floor of EWI building)

My group website: radar.tudelft.nl

Today

- **Recap:** Ohm's law, KVL/KCL
- **Week 1.3:**
 - Methods for circuit analysis
 - Visual Inspection
 - Nodal analysis
 - Mesh analysis
 - Suitability of each method
- **Summary and Next Week**

Recap

Ohm's Law, KVL, KCL

- Ohm's law holds for a linear resistance:
The measure unit for resistance is ohm, Ω

$$v = i \cdot R$$



Kirchhoff's Current Law (**KCL**):


- The sum of all currents in a node is zero.

$$\sum_{j=1}^n i_j(t) = 0$$

Kirchhoff's Voltage Law (**KVL**):



- The sum of all voltages in a mesh is zero.

$$\sum_{j=1}^n v_j(t) = 0$$

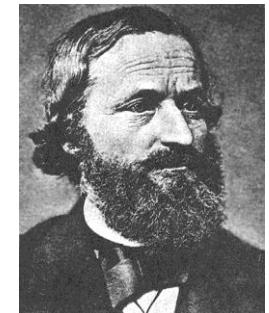

Series and Parallel Connections

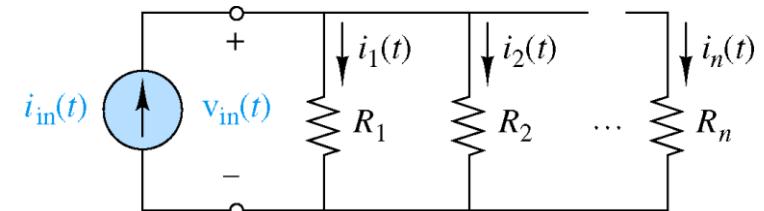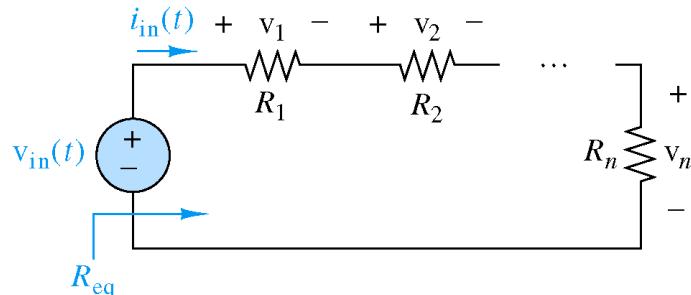- Voltage (left) and current (right) dividers, respectively:



$$v_j(t) = \frac{R_j}{R_1 + R_2 + \dots + R_n} v_{in}(t) = \frac{R_j}{R_{eq}} v_{in}(t)$$

$$i_j(t) = \frac{\frac{1}{R_j}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}} i_{in}(t)$$

Week 1.3

Please mind that...



Linear Circuits
in Week 1

Linear Circuits
in Week 2

Linear Circuits in
Week 3 and onward

Analysing an electric circuit...

This means in first instance being able to **calculate the voltages and currents at each branch**.

-You may be asked to calculate a numerical value (with unit)

-You may be asked to write an equation that links the different quantities (without numbers, but with variables)

How to do it?

Analysing an electric circuit...

First, we need to be **aware of the tools** we have in our toolbox, so far:

- Ohm's law
- KCL
- KVL
- calculation of equivalent resistance in series/parallel
- voltage/current dividers



Method of Visual Inspection

Literally, **look** at the circuit and...

- a) see if there are simplifications to make (e.g., equivalent resistances)
- b) start writing the relevant equations (Ohm, Kirchhoff, V/I dividers)

Method of Visual Inspection




- Requires experience and insight
- Is difficult to implement algorithmically
- Can fail if the circuit increases in complexity



We prefer a **generally applicable method** working according to an algorithm! Let's look at them...

Planar Networks

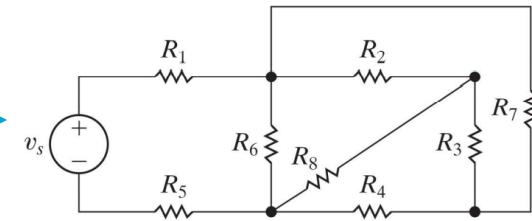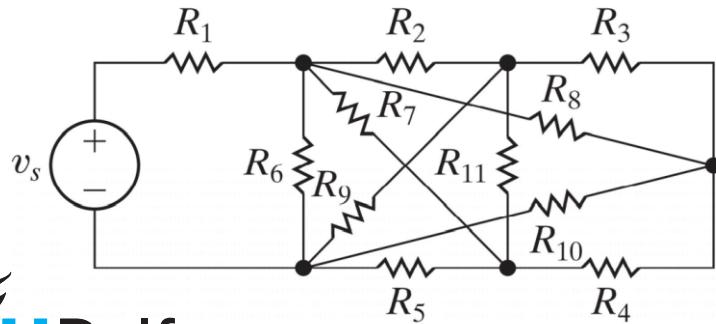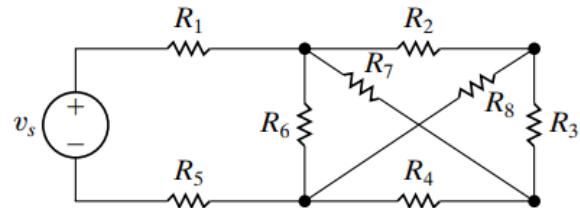First though a definition. **Planar** circuits \rightarrow on a plane with no crossing branches.



Planar

Nodal Analysis

Nodal Analysis - Steps

Step 1: Bookkeeping:

- Determine the number of nodes (N)
- Choose the reference (the ground)
- Draw the current directions in each circuit branch

LINEAR
CIRCUITS...

Step 2: Assemble the needed equations:


- Assemble the Kirchhoff current equations for all nodes except the ground (N-1 equations)
- Express the currents in terms of voltages (KCL)

Step 3: Solve the equations

- Solve the system of linear equations

MATHS...

Nodal Analysis: example 1

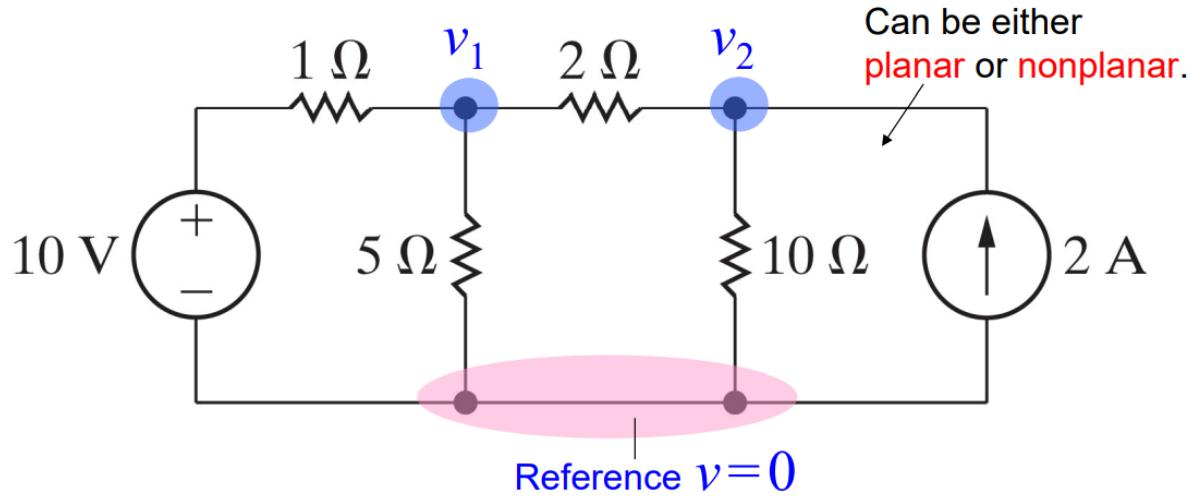


- Select one of the essential nodes, i.e. a node where three or more circuit elements join. → revisit the definition of reference and non-reference nodes.

Nodal Analysis: example 1

- Write the system of KCL equations

Node 1: $\left\{ \frac{v_1 - 10}{1\Omega} + \frac{v_1}{5\Omega} + \frac{v_1 - v_2}{2\Omega} = 0, \right.$

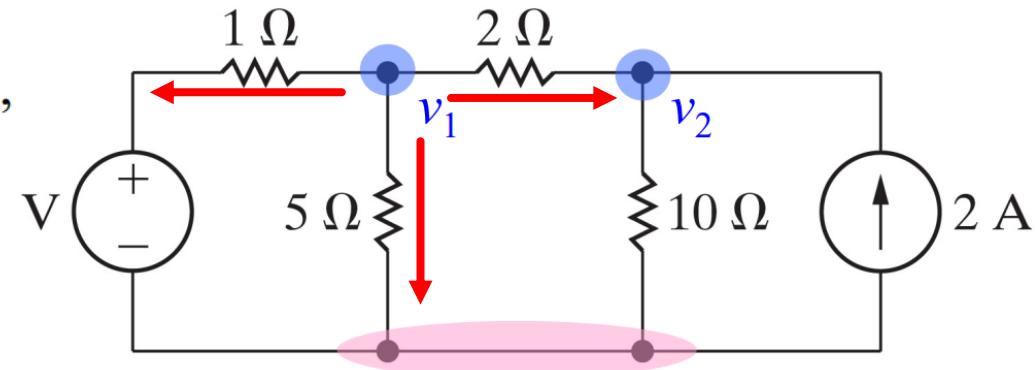Node 2: $\left. \frac{v_2 - v_1}{2\Omega} + \frac{v_2}{10\Omega} = 2. \right.$




Nodal Analysis: example 1

- Write the system of KCL equations

$$\text{Node 1: } \left\{ \frac{v_1 - 10}{1\Omega} + \frac{v_1}{5\Omega} + \frac{v_1 - v_2}{2\Omega} = 0, \right.$$
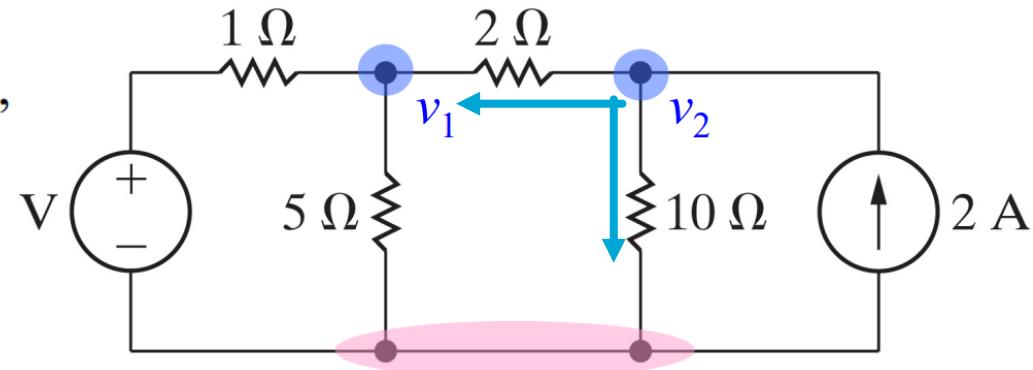
$$\text{Node 2: } \left. \frac{v_2 - v_1}{2\Omega} + \frac{v_2}{10\Omega} = 2. \right.$$




Nodal Analysis: example 1

- Solve the system, with the technique you prefer


$$\text{Node 1: } \left\{ \frac{v_1 - 10}{1\Omega} + \frac{v_1}{5\Omega} + \frac{v_1 - v_2}{2\Omega} = 0, \right.$$
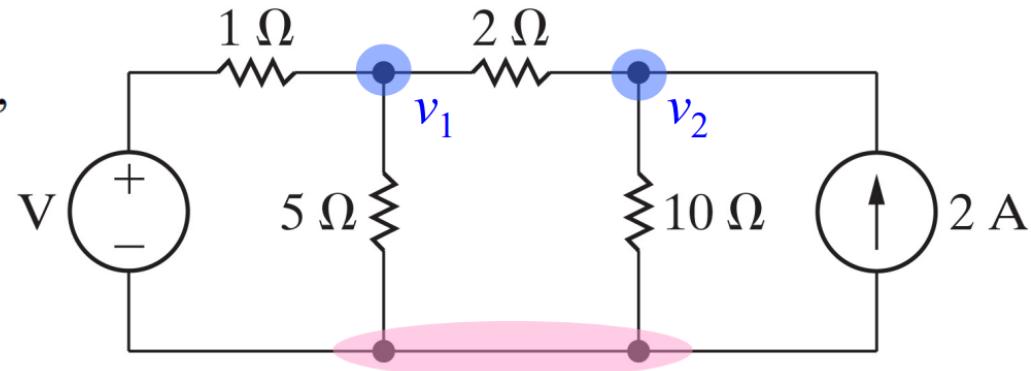
$$\text{Node 2: } \left. \frac{v_2 - v_1}{2\Omega} + \frac{v_2}{10\Omega} = 2. \right.$$



$$\left\{ \begin{array}{l} 10v_1 - 100 + 2v_1 + 5v_1 - 5v_2 = 0 \\ 5v_2 - 5v_1 + v_2 = 20 \end{array} \right. \quad \left\{ \begin{array}{l} v_1 = 9,09 \text{ V} \\ v_2 = 10,9 \text{ V} \end{array} \right.$$

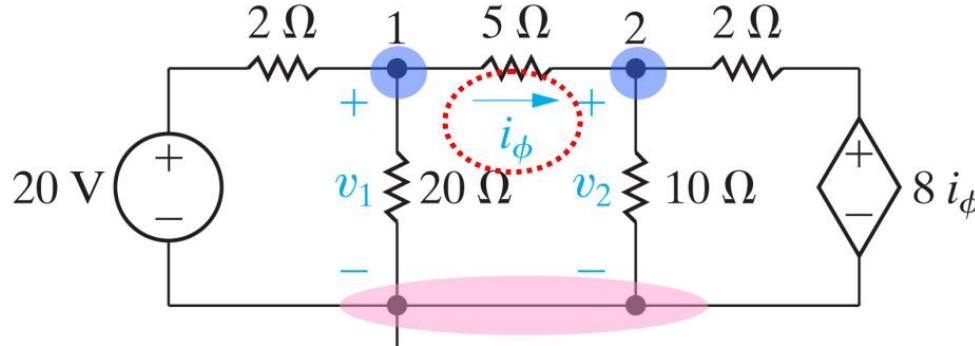Nodal analysis: circuits with dependent sources




Node 1: $\frac{v_1 - 20}{2\Omega} + \frac{v_1}{20\Omega} + \frac{v_1 - v_2}{5\Omega} = 0, \Rightarrow \begin{bmatrix} 0.75 & -0.2 \\ -1 & 1.6 \end{bmatrix} \times \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$

Node 2: $\frac{v_2 - v_1}{5\Omega} + \frac{v_2}{10\Omega} + \frac{v_2 - 8i_\phi}{2\Omega} = 0, \Rightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 16 \\ 10 \end{bmatrix} \text{ V}, i_\phi = 1.2 \text{ A.}$

Constraint: $i_\phi = \frac{v_1 - v_2}{5\Omega}.$


Nodal analysis: voltage source between 2 nodes

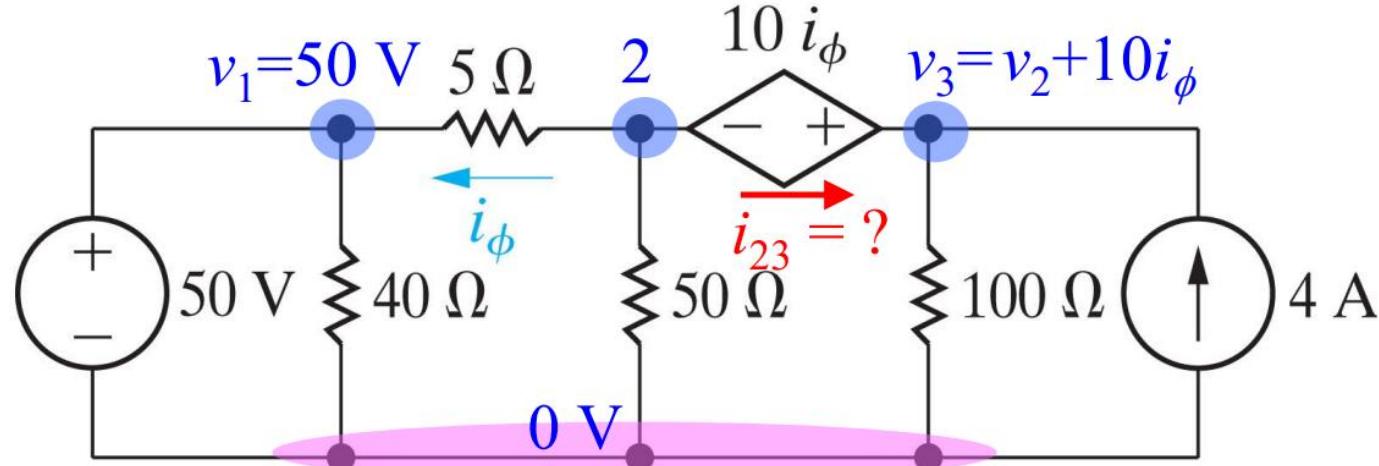- When an independent or a dependent voltage source is the only element between two nodes → the branch current is undetermined!
- We cannot apply KCL to those nodes.
- What now?!



Nodal analysis: voltage source between 2 nodes

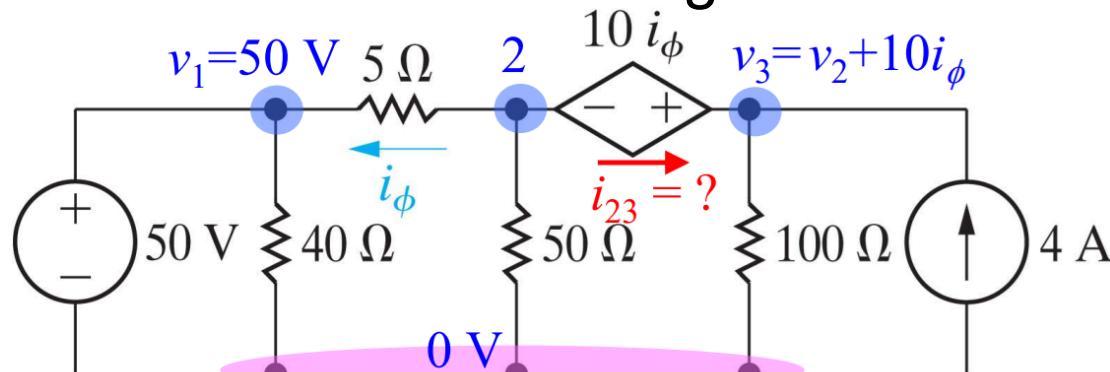Apply the elimination method to remove one variable; then use the constraint that comes from the voltage source.



$$\begin{aligned} \text{Node 2: } & \left\{ \frac{v_2 - 50}{5 \Omega} + \frac{v_2}{50 \Omega} + i_{23} = 0, \right. \\ & \left. \Rightarrow \frac{v_2 - 50}{5 \Omega} + \frac{v_2}{50 \Omega} + \frac{v_3}{100 \Omega} = 4 \right. \\ \text{Node 3: } & \frac{v_3}{100 \Omega} = i_{23} + 4. \end{aligned}$$


Source constraint: $v_3 = v_2 + 10(v_2 - v_1)/(5 \Omega)$

Still missing an equation? Yes,
the KCL at the node 1...

Nodal analysis: voltage source between 2 nodes


- Alternative approach: apply KCL to a **supernode** formed by the combination of two essential nodes; one can get the same equation as in the previous slide without the intermediate elimination step.
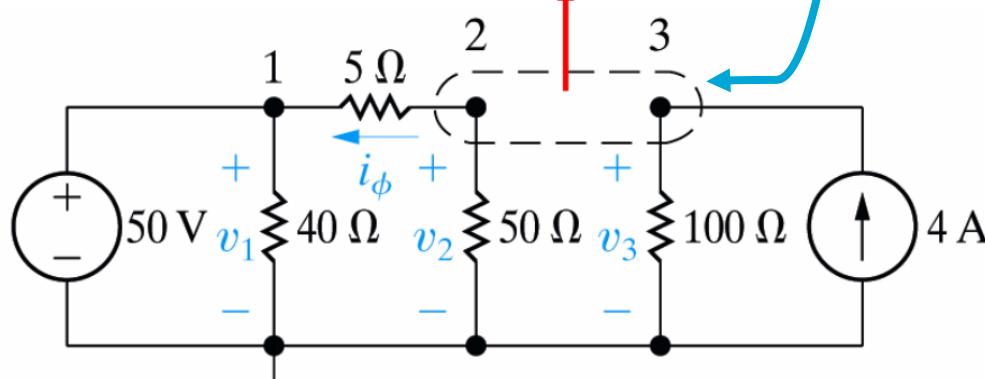
$$\frac{v_2 - 50}{5 \Omega} + \frac{v_2}{50 \Omega} + \frac{v_3}{100 \Omega} = 4$$



Supernode is a kind of big node with 4 currents in this case...

Nodal analysis: Supernode with ground?

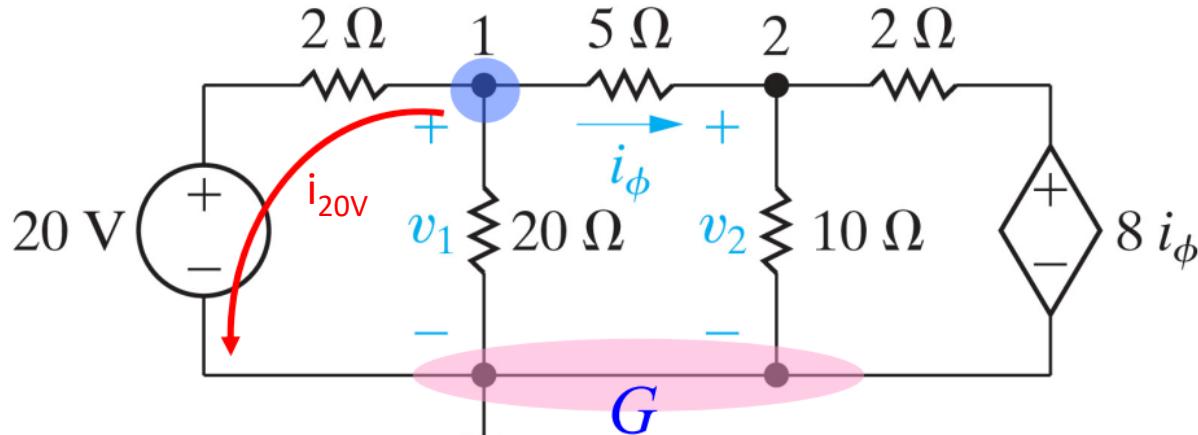


- Another example
- 20-V source is not the only element between nodes 1 and Ground (G)
- The branch current $i_{20V} = (v_1 - 20)/(2)$ is still available, KCL can still be applied to Node 1 → no need to use supernode!!!



Nodal analysis: Your turn

Calculate I_x with nodal analysis.

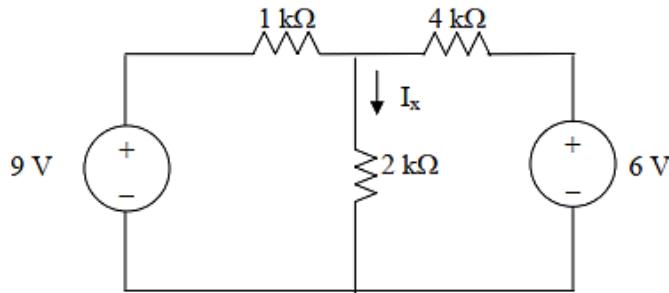


Steps:

- Look at the circuit to identify essential nodes. How many here?
- Write the KCL equations for each essential node (not for the ground)
- Express the currents in the KCL equations as a function of nodal voltage
- Solve the system of equations -> in this problem then calculate I_x from the nodal voltage.

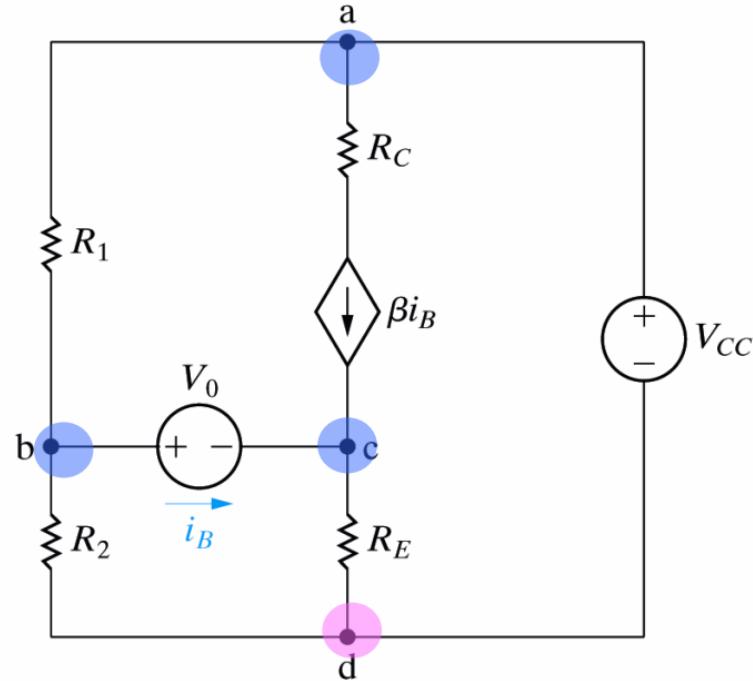Example: Amplifier Circuit

- There are 3 unknown voltages.
- Since i_B cannot be derived by node voltages, we have 4 unknowns.
- The 2 voltage sources provide 2 constraints

$$\begin{cases} v_a = V_{CC} \\ v_c = v_b - V_0 \end{cases}$$



Example: Amplifier Circuit


- Apply KCL to Node b:

$$\frac{v_b}{R_2} + \frac{v_b - V_{CC}}{R_1} + i_B = 0$$

- Apply KCL to Node c:

$$i_{cd} = (1 + \beta)i_B,$$
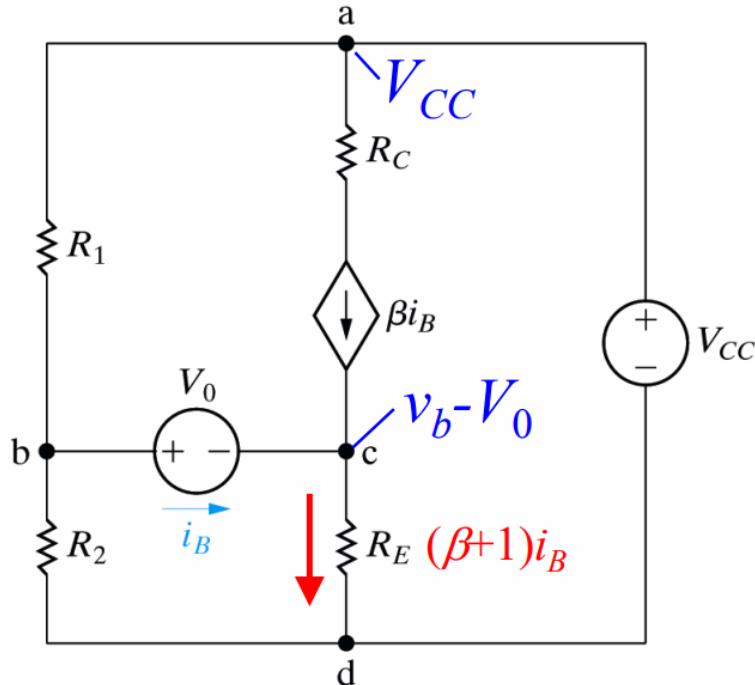
$$\Rightarrow (1 + \beta)i_B = \frac{v_c}{R_E}$$



This was just an example to demonstrate Nodal analysis to a circuit modelling a real amplifier. Nodal analysis is typically used by computer circuit simulators like Pspice.


Mesh Analysis

Mesh Analysis: Overview

- Comparable with the nodal analysis
- Makes use of Kirchhoff's **voltage** law
- But it is only applicable to planar circuits (no crossings)
- $B-N+1$ equations (N nodes, B branches)


Mesh Analysis: Advantages

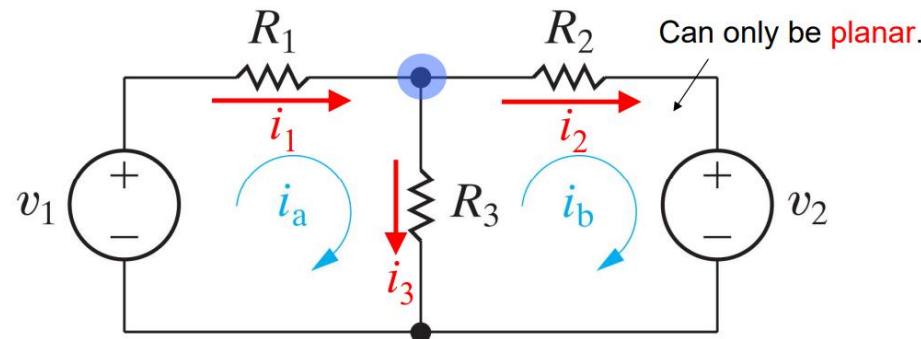- Each mesh current flows into and out of any node on the way → automatically satisfy KCL
- Relation between branch currents and mesh currents:
 $i_1 = i_a$, $i_2 = i_b$, $i_3 = i_a - i_b$



Mesh Analysis: example (without numbers)

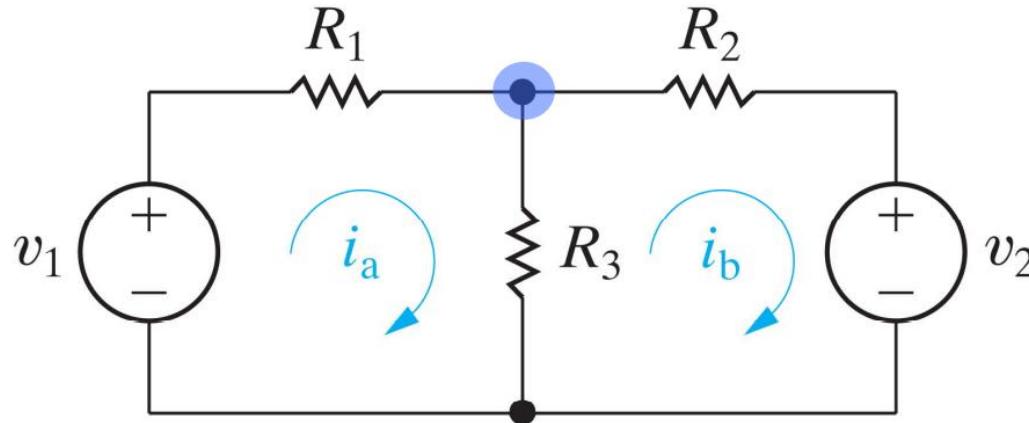Start by drawing mesh currents and then write KVL equations




$$\text{Mesh a: } v_1 = i_a R_1 + (i_a - i_b) R_3$$

$$\text{Mesh b: } i_b R_2 + v_2 + (i_b - i_a) R_3 = 0 \Rightarrow \begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \times \begin{bmatrix} i_a \\ i_b \end{bmatrix} = \begin{bmatrix} v_1 \\ -v_2 \end{bmatrix}$$


Mesh Analysis: current source between 2 meshes

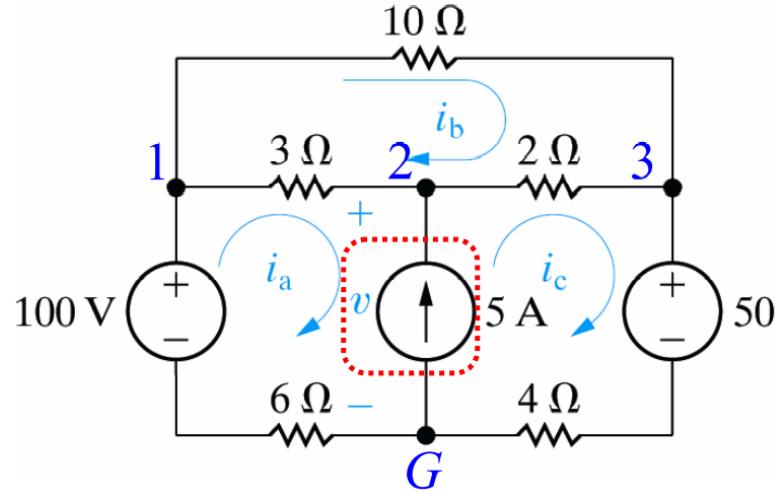- When a current source is between two essential nodes (no need to be the only element), the voltage drop across the source is undetermined, \rightarrow cannot apply KVL to either mesh!



If the voltage at node 2 is not known (i.e. we cannot apply KVL) then we cannot write the mesh currents in a and c.

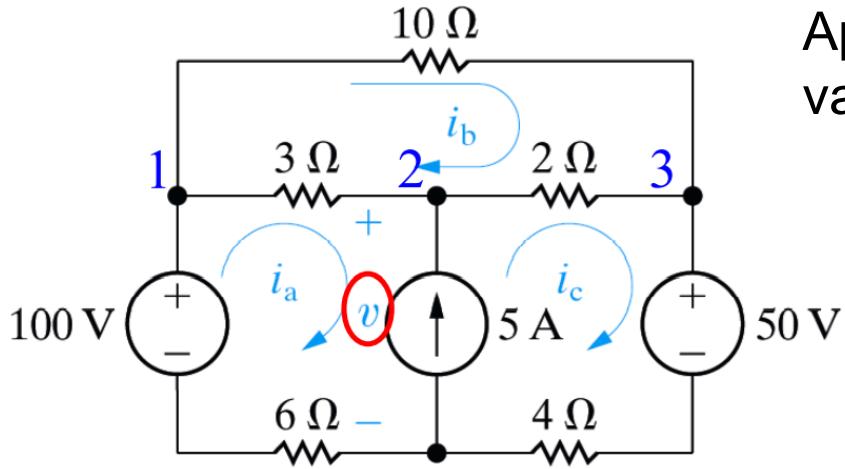Mesh Analysis: current source between 2 meshes



Apply the elimination method to remove one variable and obtain the 1st equation.

$$\begin{aligned} \text{Mesh a: } & \left\{ (3 \Omega)(i_a - i_b) + v + (6 \Omega)i_a = 100, \right. \\ \text{Mesh c: } & \left\{ (2 \Omega)(i_c - i_b) + 50 + (4 \Omega)i_c = v. \right. \\ & \Rightarrow 9i_a - 5i_b + 6i_c = 50 \end{aligned}$$

The 2nd equation comes from the top mesh with i_b :

$$10i_b = 3(i_a - i_b) + 2(i_c - i_b)$$



Then use the constraint coming from the current source in a KCL to get the 3rd equation: $i_a + i_b + 5 = i_c$

Mesh Analysis: current source between 2 meshes

- Alternative approach: apply KVL to a **supermesh** formed by the combination of two meshes; one can get the same equation as in the previous slide without the intermediate elimination step. The other two equations are derived as in the previous slide.


$$(3\Omega)(\underline{i_a} - \underline{i_b}) + (2\Omega)(\underline{i_c} - \underline{i_b}) + 50 + (4\Omega)i_c + (6\Omega)i_a = 100$$

$$\Rightarrow 9i_a - 5i_b + 6i_c = 50$$

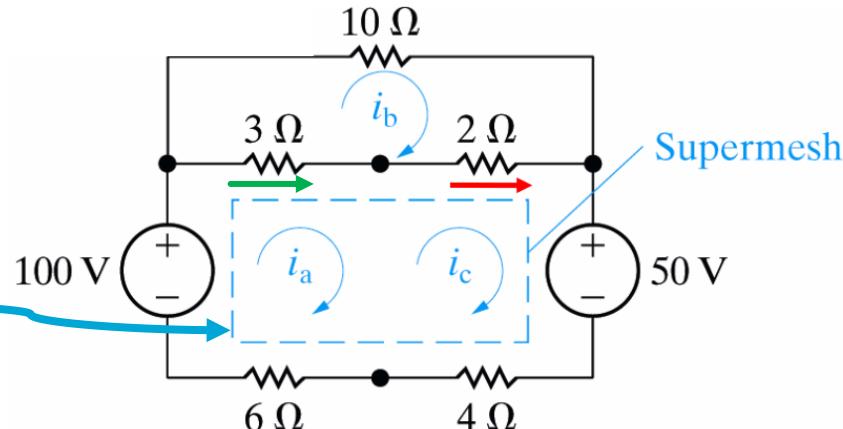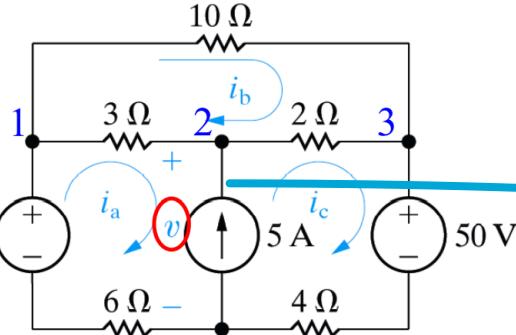

Mesh analysis: Your turn

Calculate V_o with mesh analysis.

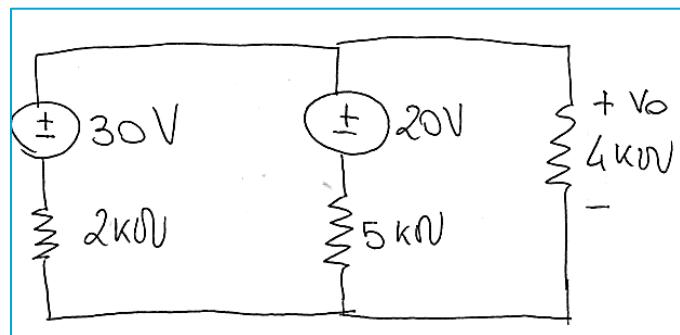

Steps:

- No panic (always!)
- Look at the circuit to identify meshes and write the mesh currents
- Write the KVL equations for each mesh
- Express the voltages in the KVL equations as a function of mesh currents
- Solve the system of equations then find V_o using Ohm's law.

Expected result $V_o=20V$

Coffee Break



Suitability of Each Method

Suitability of Each Method

- In principle both the nodal analysis and mesh analysis are useful for any given circuit.
- What then determines if one is going to be more efficient for solving a circuit problem?
- There are two factors that dictate the best choice:
 - The topology of the particular network is the first factor.
 - The second factor is the information required (i.e. what the problem asks for).

Suitability of Each Method


Mesh analysis:

- If the network contains:
 - Many series connected elements.
 - Voltage sources.
 - Supermeshes.
 - A circuit with fewer meshes than nodes.
- If branch/mesh currents are the unknown quantity

Nodal analysis:


- If the network contains:
 - Many parallel connected elements.
 - Current sources.
 - Supernodes.
 - A circuit with fewer nodes than meshes.
- If nodal voltages are the unknown quantity

Example: Suitability of Each Method

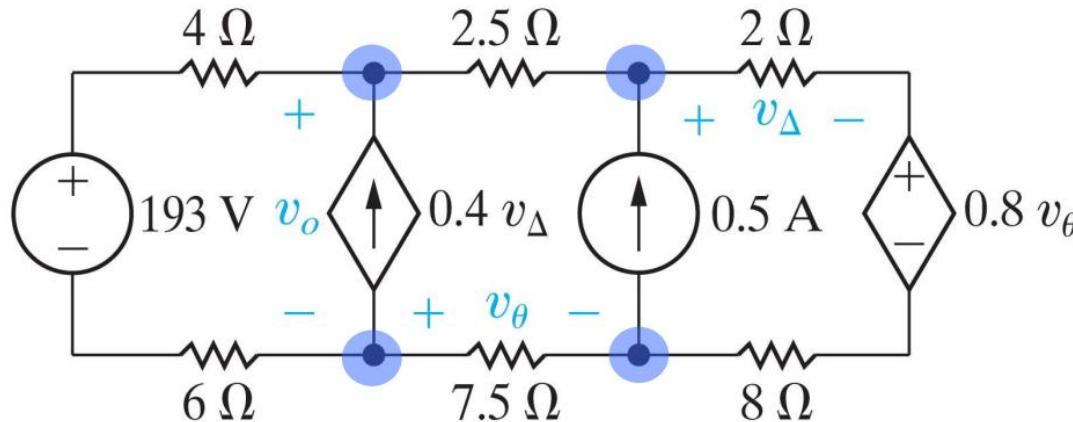


- 3 meshes, 2 current sources (2 supermeshes) → 1 mesh equation.
- 4 essential nodes, no voltage source is the only element on one branch (no supernode) → (4-1)= 3 node equations

Example: Suitability of Each Method

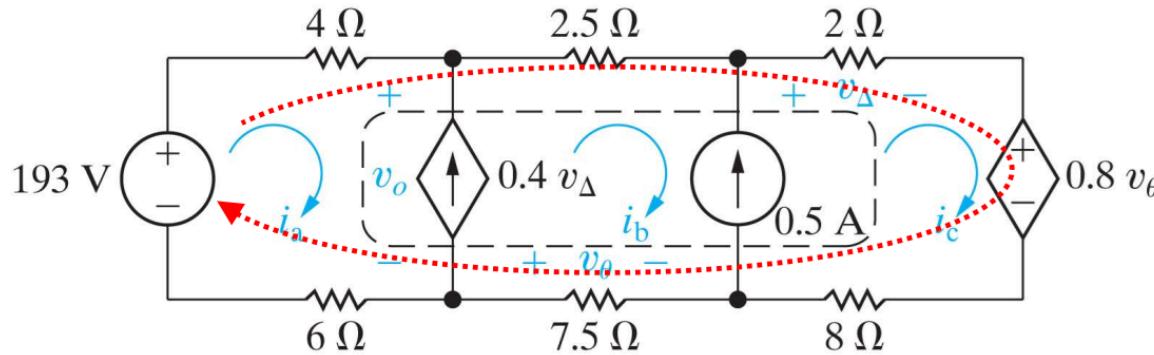

- Apply KVL to supermesh a, b, c
$$193 = 4i_a + 2.5i_b + 2i_c + 0.8v_\theta + 8i_c + 7.5i_b + 6i_a$$
- But note that $v_\theta = -7.5i_b$ (do not forget the minus!)
- So eventually: $193 = 10i_a + 4i_b + 10i_c$

Example: Suitability of Each Method

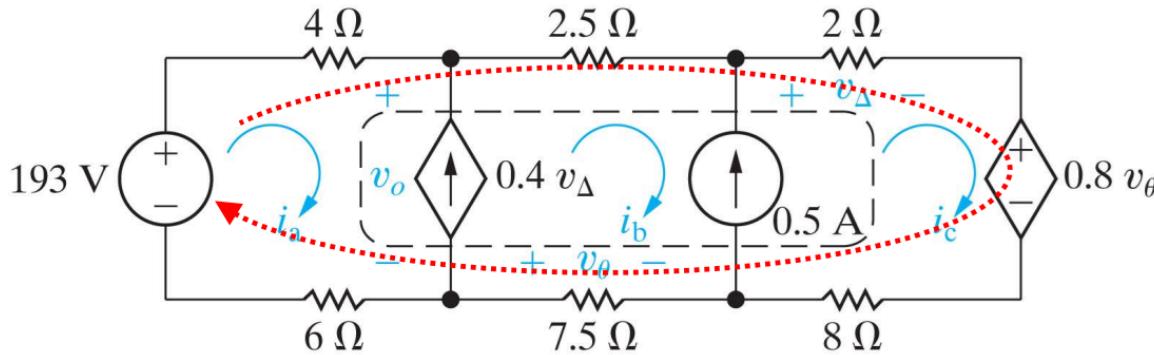

- You get the 2 equations from the constraints of the current sources of the supermesh, i.e. KCL...

$$0.5 + i_b = i_c$$

$$\text{And } i_b = i_a + 0.4v_\Delta = i_a + 0.4(2i_c) \rightarrow i_b = i_a + 0.8i_c$$

Now you are ready to go and solve the system of 3 equations.

Summary

- Methods for circuit analysis
 - Visual Inspection
 - Nodal analysis (based on KCL with nodal voltages as unknowns)
 - Mesh analysis (based on KVL with mesh currents as unknowns)
- Suitability of each method -> it comes with practical experience, **so practice, practice, practice!!!**



Next steps

- **SGH** (Self-Graded Homework assignments): posted today; submission due on Wednesday.
- **Seminar**: in groups on Tuesday & altogether on Friday.
- **Next week**:
 - Linearity
 - Superposition
 - Norton and Thévenin theorems & equivalent networks
 - Maximum power transfer
- **1hour DRY-RUN EXAM** on Tue September 23rd 16-17 (do take advantage of this!)

Thank you!