

EE1D1: Digital Systems A

BSc. EE, year 1, 2025-2026, lecture 2

Boolean Circuits


Computer Engineering Lab

Faculty of Electrical Engineering, Mathematics & Computer Science

Recap

- Introduction to Digital Systems
 - Hardware
 - Software
- Digital versus Analog
 - Digital needs more resources
 - Digital requires less accuracy
- Binary Systems and Boolean Algebra
 - Logic/Boolean operations
- Data Representation
 - Positive/negative numbers
 - Binary, decimal, hexadecimal
 - Fixed point numbers

Recap

 

Recap

Week	Lecture 1 (Mo)	Lecture 2 (Tue)	Assignments	Mock-Up/Exam
1.1	Intro	Boolean Circuits	GP-lec1, GP-lec2	
1.2	SystemVerilog	Logic minim.	GP-lec3, GP-lec4	
1.3	Combinational Modules		GP-lec5 Course Lab Part 1	
1.4			Course Lab Part 2	Mock Exam (Tuesday) Discuss Mock Exam (Friday)
1.5				Partial Exam 1 (Friday)

Week	Date	Lecture	Topics	Material
1.1	04/09	Lec 1	Introduction to Digital System	Sections 1 – 1.5.4
	05/09	Lec 2	Boolean Circuits	Sections 2.1, 2.3 (not yet 2.3.5) and 2.4
1.2	11/09	Lec 3	SystemVerilog	Sections 4.1, 4.2 (not 4.2.3, 4.2.6, 4.2.9), 4.3 and 4.9
	12/09	Lec 4	Logic Minimization	Sections 2.2, 2.3.5, 2.5, 2.7 and 2.9
1.3	18/09	Lec 5	Combinational Modules, Implementation Technology and Floating Point Numbers	Sections 1.6, 1.7.4-1.7.7, 2.6.2, 2.8, 5.3.1, and 5.3.2 (no rounding and addition)

System Descriptions

- Switches, truth table, gates, timing diagram, ...

System Types

- Combinatorial systems and Sequential systems

Boolean Algebra

- Laws and theorems
- Simplification, mapping to a circuit

Summary

Learning Objectives


As student you should be able to:

- describe digital systems using different formats (e.g. truth table, switches, etc.) and convert them from one format to the other
- explain how combinational and sequential circuits work at a high abstraction level
- recognize the symbols of the Boolean gates and draw Boolean circuits from expressions
- manipulate Boolean expressions using Boolean theorems and DeMorgan's law
- convert Boolean circuits to NAND, NOR, NOT equivalents

EE1D1: Digital Systems A

System Descriptions

System Descriptions

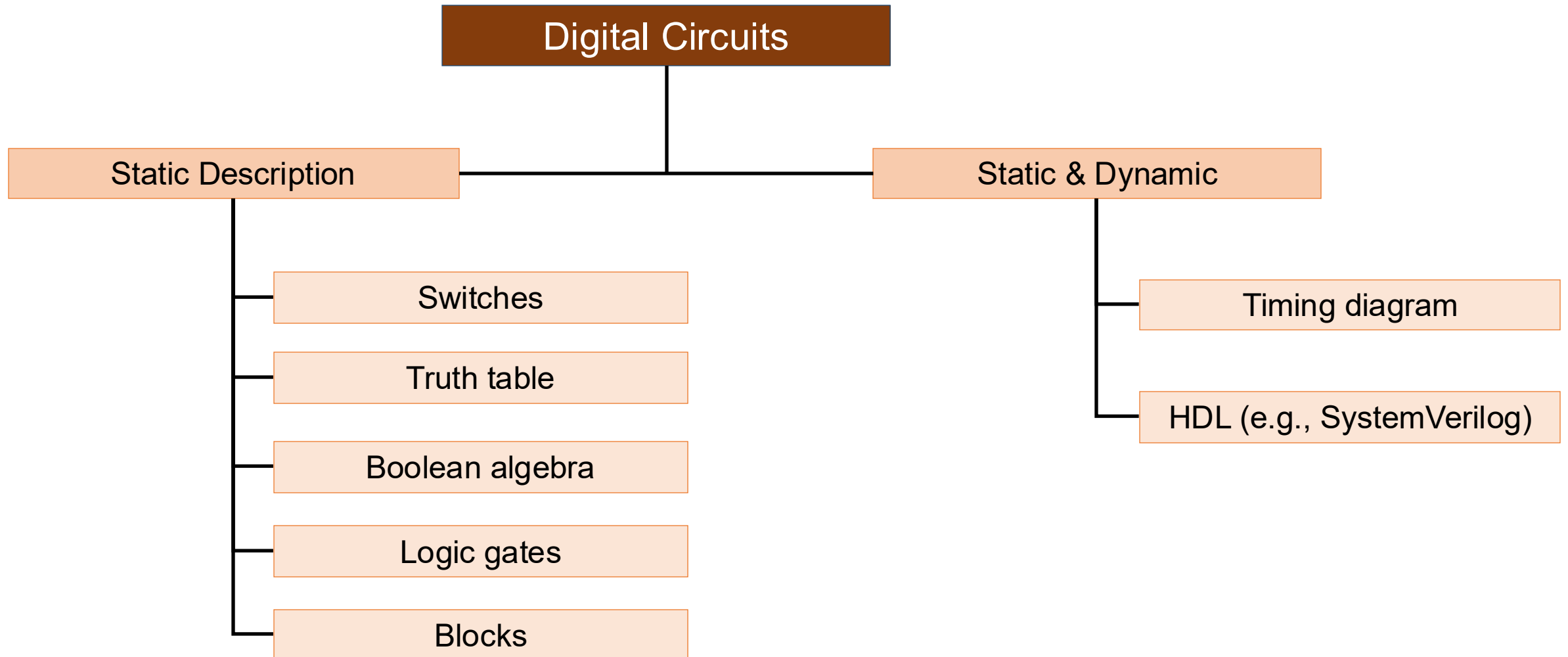


System Description — Static






- Switches

Types:

Normally Open:

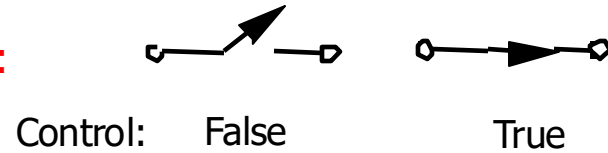


Normally Closed:

    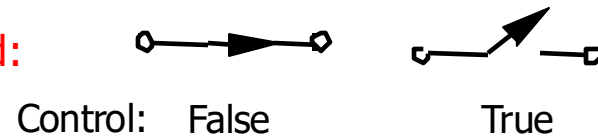


Implementation NOT, AND, OR:


NOT:

 

AND:

 

OR:

 

System Description — Static

- Truth Tables

- List the output values for all possible input value combinations
- Example:* Half Adder (add 2 binary values A and B)

$$\begin{array}{r} A \quad 0 \quad 0 \quad 1 \quad 1 \\ B \quad 0 \quad 1 \quad 0 \quad 1 \\ \hline 0 \quad 1 \quad 1 \quad 10 \end{array}$$

Carry

Sum

compare
to decimal
values:

$$\begin{array}{r} 6 \\ 7 \\ \hline 13 \end{array}$$

Carry

Sum

Truth table Half Adder:

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

System Description — Static

- Boolean algebra:

- *Values:* 0 (false), 1 (true)
- *Operations:* NOT, AND, OR, ...

$$\text{NOT } X \equiv X' \quad X \text{ AND } Y \equiv X \bullet Y \equiv XY \quad X \text{ OR } Y \equiv X + Y$$

- Derivation of Boolean description for Half Adder:

Note:

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\text{Sum} = A' B + A B'$$


$$\text{Carry} = A B$$

A	B	$A \bullet B$	$A' B$	$A' \bullet B$
0	0	0	1 0	0
0	1	0	1 1	1
1	0	0	0 0	0
1	1	1	0 1	0


System Description — Static

- Logic gates:
 - building blocks for which an electronic implementation exists

Basic logic gates:

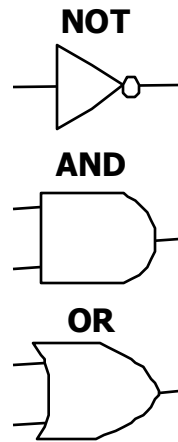

Circuit for a Half Adder:

 


$$\text{Sum} = A' B + A B'$$

$$\text{Carry} = A B$$

System Description — Static


- Blocks
 - emphasis on *structure* of the system instead of *behaviour*
 - possibility for hierarchical design

Full Adder made of
2 Half Adder blocks:

 


B.T.W. a Full Adder adds 3
bits: A, B en Cin

Block representation
for the Full Adder

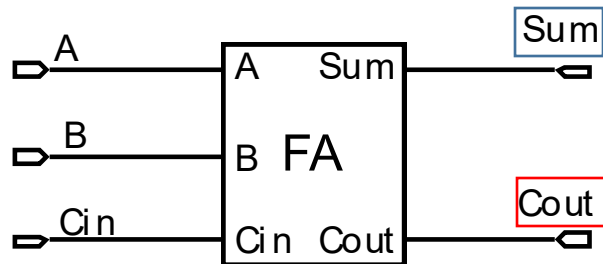

A	0	1	1	1
B	0	0	1	1
Cin	0+	0+	0+	1+
	<u>00</u>	<u>01</u>	<u>10</u>	<u>11</u>

 3-bit Full Adder
Computes $s = a + b$, where
 $a = a_2a_1a_0$, $b = b_2b_1b_0$





0110	(C)
011	(A)
011	(B) +
<u>110</u>	(S)

System Description – Dynamic

- Using Timing Diagrams

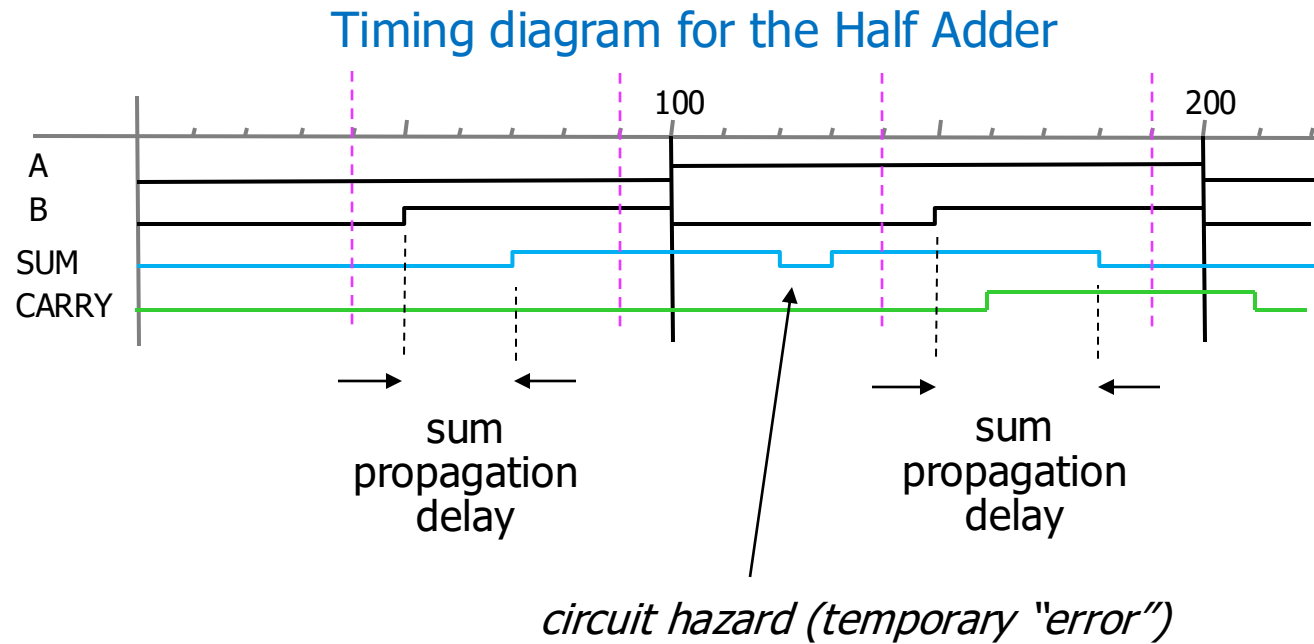 - Contains structural information and dynamic behaviour (delay/time!)



System Description - Overview

- Different Half Adder Descriptions

- Static:

Truth Table


A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Boolean Algebra

$$\text{Sum} = A' B + A B'$$


$$\text{Carry} = A B$$

Logic Gates

 


- Static + Dynamic:

Timing Diagram

 

SystemVerilog

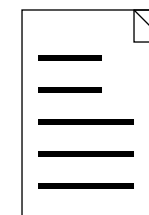

EE1D1: Digital Systems A


System Types

System Types - Combinatorial Systems

- Constructed from logic gates
- No feedback from outputs to inputs
- Outputs are only directly dependent on current input values
- No memory (no internal state)

Example: Full Adder


A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

A	0	1	1	1
B	0	0	1	1
Cin	0+	0+	0+	1+
	<u>00</u>	<u>01</u>	<u>10</u>	<u>11</u>

System Types – Sequential Systems

 - System has internal state space (set of possible states)
- Feedback van from outputs to inputs
- Outputs dependent on inputs and past (memory)



Synchronous systems

- State transitions triggered by special signal: clock
- E.g.: $i = \text{clock}$, counter goes to next state when i goes from 0 to 1

- Asynchronous systems

- State transitions at arbitrary moments
- E.g.: counter starts when $i = 1$

EE1D1: Digital Systems A

Boolean Algebra

Boolean Algebra

- Boolean algebra is used for specification desired behaviour
- Theorems/properties are used to rewrite Boolean expression:
 - *minimization* of the number of operations (*simplification*)
 - rewriting in terms of *available* operations
- In the coming lectures you will learn:
 - a *systematic procedure* to simplify Boolean expressions.
 - how to use SystemVerilog, and its synthesis tools, for this.

Boolean Algebra

- Boolean algebra consists of:

- set of numbers $B = \{0, 1\}$ ($\{\text{false}, \text{true}\}$)
- set of operations
 - unary operation $', \neg$ (NOT)
 - binary operations $\bullet, +$ (AND, OR)

Axioms:

$$0' = 1$$

$$1' = 0$$

$$0 \bullet 0 = 0$$

$$0 \bullet 1 = 0$$

$$1 \bullet 0 = 0$$

$$1 \bullet 1 = 1$$

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

Boolean Algebra

- Important Theorems

1. Involution property:

$$(i) \quad (a')' = a$$

2. Idempotent property:

$$(i) \quad a + a = a \qquad (ii) \quad a \cdot a = a$$

3. Identity property:

$$(i) \quad a + 0 = a \qquad (ii) \quad a \cdot 1 = a$$

4. Null element property

$$(i) \quad a + 1 = 1 \qquad (ii) \quad a \cdot 0 = 0$$

5. Complement property:

$$(i) \quad a + a' = 1 \qquad (ii) \quad a \cdot a' = 0$$

6. Commutative property:

$$(i) \quad a + b = b + a \quad (ii) \quad a \cdot b = b \cdot a$$

7. Associative property:

$$(i) \quad (a + b) + c = a + (b + c) = a + b + c$$

$$(ii) \quad (a \cdot b) \cdot c = a \cdot (b \cdot c) = a \cdot b \cdot c$$

8. Distributive property:

$$(i) \quad a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$(ii) \quad a \cdot (b + c) = a \cdot b + a \cdot c$$

All simply derived from:

$$0' = 1 \quad 0 \cdot 0 = 0 \quad 0 + 0 = 0$$

$$1' = 0 \quad 0 \cdot 1 = 0 \quad 0 + 1 = 1$$

$$1 \cdot 0 = 0 \quad 1 + 0 = 1$$

$$1 \cdot 1 = 1 \quad 1 + 1 = 1$$

Boolean Algebra

- Theorems (continued)

Also we often use the following properties:

De Morgan's laws:

$$(i) \quad (a + b)' = a' \cdot b'$$

$$(ii) \quad (a \cdot b)' = a' + b'$$

Absorption properties:

$$(i) \quad a \cdot b + a \cdot b' = a$$

$$(ii) \quad (a + b) \cdot (a + b') = a$$

$$(iii) \quad a + a \cdot b = a$$

$$(iv) \quad a \cdot (a + b) = a$$

$$(v) \quad a + a' \cdot b = a + b$$

$$(vi) \quad a \cdot (a' + b) = a \cdot b$$

Boolean Algebra – Some Proofs

Absorption property (i): $X \bullet Y + X \bullet Y' = X$

$$\text{distributive property (8)} \quad X \bullet Y + X \bullet Y' = X \bullet (Y + Y')$$

$$\text{complement p. (5)} \quad X \bullet (Y + Y') = X \bullet 1$$

$$\text{identity p. (3)} \quad X \bullet 1 = X$$

Absorption property (iii): $X + X \bullet Y = X$

$$\text{identity p. (3)} \quad X + X \bullet Y = X \bullet 1 + X \bullet Y$$

$$\text{distributive p. (8)} \quad X \bullet 1 + X \bullet Y = X \bullet (1 + Y)$$

$$\text{null element p. (4)} \quad X \bullet (1 + Y) = X \bullet 1$$

$$\text{identity p. (3)} \quad X \bullet 1 = X$$

Absorption property (v): $X + X' \bullet Y = X + Y$

$$\text{null element p. (4)} \quad X + X' \bullet Y = X \bullet (1 + Y) + X' \bullet Y$$

$$\text{distributive p. (8)} \quad X \bullet (1 + Y) + X' \bullet Y = X + X \bullet Y + X' \bullet Y$$

$$\text{distributive p. (8)} \quad X + X \bullet Y + X' \bullet Y = X + (X + X') \bullet Y$$

$$\text{complement p. (5)} \quad X + (X + X') \bullet Y = X + Y$$

1. Involution property:	(i) $(a')' = a$
2. Idempotent property:	(i) $a + a = a$ (ii) $a \bullet a = a$
3. Identity property:	(i) $a + 0 = a$ (ii) $a \bullet 1 = a$
4. Null element property	(i) $a + 1 = 1$ (ii) $a \bullet 0 = 0$
5. Complement property:	(i) $a + a' = 1$ (ii) $a \bullet a' = 0$
6. Commutative property:	(i) $a + b = b + a$ (ii) $a \bullet b = b \bullet a$
7. Associative property:	(i) $(a + b) + c = a + (b + c) = a + b + c$ (ii) $(a \bullet b) \bullet c = a \bullet (b \bullet c) = a \bullet b \bullet c$
8. Distributive property:	(i) $a + (b \bullet c) = (a + b) \bullet (a + c)$ (ii) $a \bullet (b + c) = a \bullet b + a \bullet c$

Boolean Algebra – Example: Cout of Full Adder

$$\begin{aligned}
 \text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} + A B \text{Cin} \\
 &= A' B \text{Cin} + A B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= (A' + A) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= (1) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} + A B \text{Cin} \\
 &= B \text{Cin} + A (B' + B) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= B \text{Cin} + A (1) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= B \text{Cin} + A \text{Cin} + A B (\text{Cin}' + \text{Cin}) \\
 &= B \text{Cin} + A \text{Cin} + A B (1) \\
 &= B \text{Cin} + A \text{Cin} + A B
 \end{aligned}$$

idempotent
distributive
complement
identity

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Boolean Algebra – Question 1

What is a simplification of $F = A B C + A B C' + A' B C'$?

a. $F = A' B + A C'$

b. $F = A B + A C'$

c. $F = A' B + B C'$

d. $F = A B + B C'$

$$\begin{aligned} F &= A B C + A B C' + A' B C' \\ &= A B (C + C') + A' B C' \\ &= A B + A' B C' \\ &= B (A + A' C') \\ &= B (A + C') \\ &= A B + B C' \end{aligned}$$

Hence answer d

$$\begin{aligned} F &= A B C + A B C' + A' B C' \\ &= A B C + \mathbf{A B C'} + A' B C' + \mathbf{A B C'} \\ &= A B (C + C') + B C' (A' + A) \\ &= A B + B C' \end{aligned}$$

Hence answer d

Boolean Algebra – De Morgan's law

$$(X + Y)' = X' \cdot Y'$$

X	Y	$\bar{X}$	$\bar{Y}$	$\overline{X+Y}$	$\bar{X} \cdot \bar{Y}$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$

$$(X \cdot Y)' = X' + Y'$$

X	Y	$\bar{X}$	$\bar{Y}$	$\overline{X \cdot Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

$$\overline{X \cdot Y} = \bar{X} + \bar{Y}$$

Also valid for more terms, e.g. $(X + Y + Z)' = X' \cdot Y' \cdot Z'$ as $(X + Y + Z)' = X' \cdot (Y+Z)' = X' \cdot Y' \cdot Z'$

Example application: find the complement of an AND/OR expression

$$Z = A' B' C + A' B C + A B' C + A B C'$$

$$Z' = (A' B' C + A' B C + A B' C + A B C')'$$

$$Z' = (A' B' C)' \cdot (A' B C)' \cdot (A B' C)' \cdot (A B C')'$$

$$Z' = (A + B + C') \cdot (A + B' + C') \cdot (A' + B + C') \cdot (A' + B' + C)$$

inverting both sides
using De Morgan

using De Morgan

$$\bar{Z} = \overline{A' B' C + A' B C + A B' C + A B C'}$$


$$\bar{Z} = \overline{A' B' C} \cdot \overline{A' B C} \cdot \overline{A B' C} \cdot \overline{A B C'}$$

$$\bar{Z} = (A+B+\bar{C}) \cdot (A+\bar{B}+\bar{C}) \cdot (\bar{A}+B+\bar{C}) \cdot (\bar{A}+\bar{B}+C)$$


Boolean Algebra

- Application: from expression to circuit

Example:

 

Alternative interpretation:

 

Rewriting an expression implies another circuit implementation

Boolean Algebra – Application

- A circuit for a practical problem using Boolean algebra

Example:

“When will I go carpooling ?” (Y):


- if Alex is going (A) and Ben is not going (B)
- for sure if Casper is going (C)”

Create a binary systems that decides when I will go

Y = ?

Corresponding Boolean expression:

$$Y = A B' + C$$

 


A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

When only inverters (NOT) and OR gates are available:

$$A B' = ((A B')')' = (A' + (B')')' = (A' + B)'$$

$$\text{Hence } Y = A B' + C = (A' + B)' + C$$

2 inverters (') and 2 OR gates (+)

 

Boolean Algebra – Application

- Simplification of expressions

Carpool example: Suppose we start with the truth table.

Simplify this to a Boolean expression:

$$Y = A' B' C + A' B C + A B' C' + A B' C + A B C$$

Minimization using Boolean properties:


$$\begin{aligned} Y &= BC(A' + A) + B'C(A' + A) + AB'C' \\ &= BC + B'C + AB'C' \\ &= C(B + B') + AB'C' \\ &= C + AB'C' \\ &= C + AB' \quad (\text{because } C + C'X = C + X, \text{ with } X = AB') \end{aligned}$$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$$\begin{aligned} Y &= A' B' C + A' B C + A B' C' + A B' C + A B' C + A B C \\ &= BC(A' + A) + B'C(A' + A) + AB'(C + C') \\ &= BC + B'C + AB' \\ &= C(B + B') + AB' \\ &= C + AB' \end{aligned}$$

Boolean Algebra – Compound operations


NAND

 

$$A \text{ NAND } B = \text{NOT } (A \text{ AND } B) = (A \cdot B)'$$

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 

$$A \text{ NOR } B = \text{NOT } (A \text{ OR } B) = (A + B)'$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

- As we will show later: in current technologies, NAND, NOR gates have better properties than AND, OR gates

- Every Boolean expression can be expressed in NAND, NOR, NOT using De Morgan:

$$A + B = ((A + B)')' = (A' \cdot B)'$$

OR is equivalent to NAND

with *inverted* inputs

$$A \cdot B = ((A \cdot B)')' = (A' + B')'$$

AND is equivalent to NOR


with *inverted* inputs

- BTW: NOT = NAND or NOR with both inputs connected to each other (proof this using Boolean algebra!)

Boolean Algebra – Compound operations

XOR (eXclusive OR): $X \text{ XOR } Y = (\text{NOT } X) Y \text{ OR } X (\text{NOT } Y)$

$$X \oplus Y = X' Y + X Y'$$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

XNOR:

$$(X \oplus Y)' = (X' Y + X Y')' = \dots = X' Y' + X Y$$




X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

Boolean Algebra

Example: alternative circuit realisations

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 (proof the equivalence
of the three realisation!)



2-level realisation
(inverters don't count)

multi-level realisation
(using simple gates)


compound gates
(min. # gates)

Boolean Algebra – Simplification of Expressions

- Aim: reduce complexity of resulting circuit
 - number operations/variables = number gates and number gate inputs
 - number bracket levels = number gate levels
- Background:
 - less gate inputs → faster gates
 - number of gate inputs in any case limited
 - less gates → lower costs / less power usage
 - less gate *levels* → less delay times

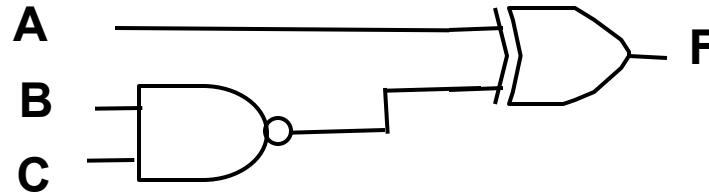Question 2

What is a logic expression for the circuit below:



- a. $F = A' B C + A B' + A C'$
- b. $F = A B C + A' B' + A' C'$
- c. $F = A B' C' + A B' + A' C$
- d. None of the above answers.

Let the output of the NAND be $X = (B C)'$. Then

$$\begin{aligned} F &= A X' + A' X \\ &= A ((B C)')' + A' (B C)' \\ &= A B C + A' (B' + C') \\ &= A B C + A' B' + A' C' \end{aligned}$$

Hence answer b

Summary

- System Descriptions
 - Switches, truth table, Boolean algebra, logic gates, timing diagram, HDL
- System Types
 - Combinational circuits
 - Sequential circuits
- Boolean algebra
 - Logic/Boolean operations
 - Boolean simplification/minimization
 - Prove system equivalence

To do list

- Reading Material book “Digital Design”:
 - Sections 2.1 and 2.3 (not yet 2.3.5) and 2.4
- Assignments for this lecture:
 - Gated Practise Lecture 2
- Reading material for next lecture: Logic Minimization
 - Sections 2.2, 2.3.5, 2.5, 2.7 and 2.9



Thank you