

EE1D1: Digital Systems A

BSc. EE, year 1, 2025-2026, lecture 7

Sequential Logic

Computer Engineering Lab

Faculty of Electrical Engineering, Mathematics & Computer Science

- **FSM Examples**


- Traffic light controller
- Candy dispenser
- Moore vs Mealy: snail crawler

- **FSM Assignment Courselab**

- State Table + Karnaugh Maps
- NAND Gate Implementation
- NOR Gate Implementation
- AOI and OAI Gate Implementation
- Circuit Diagram
- Simulation



FSM Example: Traffic Light Controller

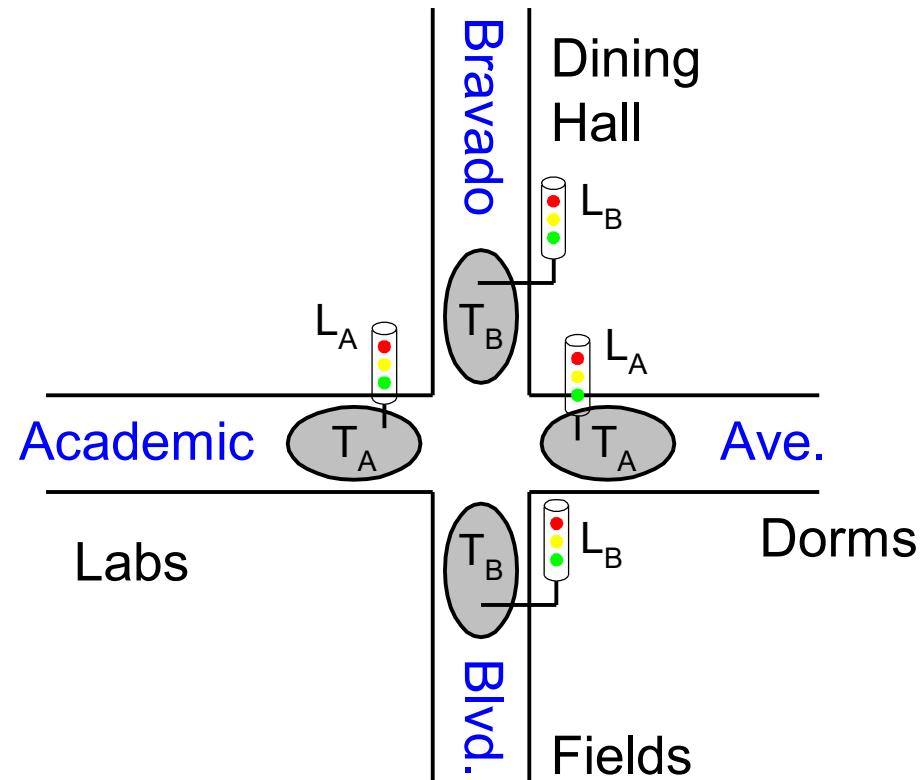- Traffic light controller at a busy intersection on campus
 - Traffic sensors: T_A , T_B (TRUE when there's traffic)
 - Traffic Lights: L_A , L_B (Three possible colors Green, Yellow and Red)



FSM Black Box and Finite-State Diagram

  
- Inputs: CLK , $Reset$, T_A , T_B
- Outputs: L_A , L_B
- CLK period is 5 seconds



FSM State Transition Table

Current State S	Inputs		Next State S'
	T_A	T_B	
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

S : Current State
 S' : Next State

 

FSM Encoded State Transition Table

State	Encoding
S0	00
S1	01
S2	10
S3	11

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0


$$S'_1 = \overline{S_1}S_0 + S_1\overline{S_0}\overline{T_B} + S_1\overline{S_0}T_B = \overline{S_1}S_0 + S_1\overline{S_0} = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1}\overline{S_0}T_A + S_1\overline{S_0}\overline{T_B}$$

FSM Output Table


Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1
 
$$\begin{aligned} L_{A1} &= S_1 \\ L_{A0} &= \overline{S_1} S_0 \\ L_{B1} &= \overline{S_1} \\ L_{B0} &= S_1 S_0 \end{aligned}$$



Output	Encoding
green	00
yellow	01
red	10

FSM Schematic

 

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} T_A + S_1 \overline{S_0} T_B$$



$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} S_0$$

$$L_{B1} = \overline{S_1}$$

$$L_{B0} = S_1 S_0$$

FSM Timing Diagram

  


FSM – Example: Candy Dispenser

Problem definition:

return gum after at least 15 cents has been inserted, using dimes (10 cent) and nickels (5 cent). No change is returned.

Step 1: Block scheme:

 


Coin sensor: N=1 or D=1 during 1 clock period after coin insertion

Step 2: State diagram:

States: 0, N, NN, NNN, D, DN, ND, ...


Inputs: N(ickel), D(ime), Reset

Output: open

 


Optimize: Re-use states when possible (S2 = S3, S4 = S5 = ... = S8)

Step 3: Simplification:

 

FSM – Example: Candy Dispenser

Step 3: Simplification:

 




Step 4: State encoding:

Current State	Q ₁	Q ₀	Inputs		Next State	D ₁	D ₀	Output Open
0¢	0	0	0	0	0¢	0	0	0
			0	1	5¢	0	1	0
			1	0	10¢	1	0	0
			1	1	X	X	X	X
5¢	0	1	0	0	5¢	0	1	0
			0	1	10¢	1	0	0
			1	0	15¢	1	1	0
			1	1	X	X	X	X
10¢	1	0	0	0	10¢	1	0	0
			0	1	15¢	1	1	0
			1	0	15¢	1	1	0
			1	1	X	X	X	X
15¢	1	1	0	0	15¢	1	1	1
			0	1	15¢	1	1	1
			1	0	15¢	1	1	1
			1	1	X	X	X	X

Step 5: State table:

FSM – Example: Candy dispenser


Step 6: Implementation:

   

$$D_1 = Q_1 + D + Q_0 N$$

$$D_0 = N Q_0' + Q_0 N' + Q_1 N + Q_1 D$$

$$\text{OPEN} = Q_1 Q_0$$

 


FSM – Question

Given the adjacent state diagram for an FSM with 1 input and 1 output.

Which input sequence (input value per clock period, last input value on the right) will give a 1 at the end?


- a. 0011
- b. 0111
- c. 1100
- d. 1110

 

From B to D when input is 1
From D to A when input is 1
From A to C when input is 1
From C to D when input is 0
=> answer d


Moore vs. Mealy FSM

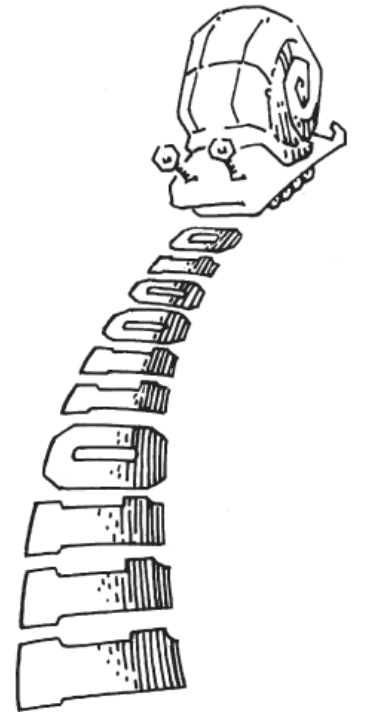Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are **01**. Design **Moore** and **Mealy** FSMs of the snail's brain.




State Transition Diagrams

Moore FSM

 


Mealy FSM

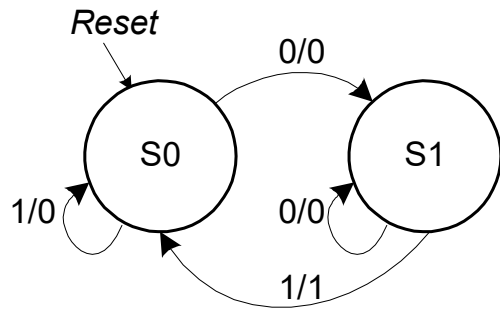

Moore FSM State Transition Table

Moore FSM

 

Current State		Inputs	Next State	
S_1	S_0		S'_1	S'_0
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0

State	Encoding
S0	00
S1	01
S2	10


$$S'_1 = S_0A$$

$$S'_0 = \overline{A}$$

Using don't care conditions
Not shown in the table

Moore FSM Output Table

Moore FSM

 

Current State		Output
S_1	S_0	Y
0	0	0
0	1	0
1	0	1

$$Y = S_1$$

State	Encoding
S0	00
S1	01
S2	10


Mealy State Transition & Output Table

Current State	Input	Next State	Output
S_0	A	S'_0	Y
0	0	1	0
0	1	0	0
1	0	1	0
1	1	0	1

State	Encoding
S0	0
S1	1

$$S'_0 = \overline{A}$$

$$Y = S_0 A$$

 

Moore FSM Schematic


Next State Equations

$$S_1' = S_0 A$$

$$S_0' = \overline{A}$$

Output Equation

$$Y = S_1$$

 


Mealy FSM Schematic

Next State Equation


$$S_0' = \overline{A}$$

Output Equation


$$Y = S_0 A$$

 


Moore and Mealy Timing Diagram

 

Moore FSM

 

Mealy FSM

 


Mealy FSM: asserts Y **immediately** when input pattern 01 is detected

Moore FSM: asserts Y one cycle **after** input pattern 01 is detected

FSM Assignment similar to Courselab Assignment 3B

 Given the following state diagram of a Moore machine called "system":



Herein, the five states are coded as follows:

State Encoding				output
	y2	y1	y0	z
A	0	0	0	1
B	1	1	1	0
C	0	1	0	1
D	1	0	1	1
E	1	0	0	0

with state A as the initial state.

The **inputs** of the systems are $x \in \{0,1\}$, $\text{reset} \in \{0,1\}$ and $\text{clk} \in \{0,1\}$.

The **current** state of the system is described by $Y = (y2, y1, y0)$ with $y_i \in \{0,1\}$


The **output** of the system is described by $z \in \{0,1\}$.

The functionality of the system is as follows. If $\text{reset} = 1$, the system returns to the initial state "A". If $\text{reset} = 0$, the system operates according to input x and synchronously on the rising clock edge.

Assignment:

1. Write SystemVerilog description that models the system described above, using only D-flipflops and the gates mentioned at point 2.
2. Implement z using only NOR-gates, $y2$ using NAND gates, $y1$ using an AOI gate, and $y0$ using an OAI gate. All NAND and NOR gates must have 2 or 4 inputs.
3. Write a test bench that verifies your own SystemVerilog model by starting with a reset and then going through all state transitions at least once. (Don't forget the clock signal clk).

State Table + Kargaug Maps

 

Karnaugh Maps

y2+

[1]

y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				

y1+

[2]

y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				

y0+

[3]

y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				

z

[4]

y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				

Inverted Karnaugh Maps

y2+'

[5]

y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				

y1+'

[6]

y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				

y0+'

[7]

y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				


z'

[8]


y2y1	00	01	11	10
y0x	00			
00				
01				
11				
10				

NAND Gate Implementation

 - Derive sum-of-products to find NAND implementation




$AB + CD$

 


$(AB + CD)''$
 $((AB)' \cdot (CD)')'$

NOR Gate Implementation

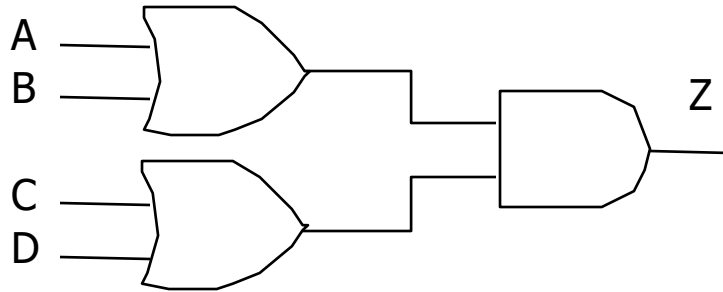- Derive product-of-sums to find NOR implementation




$$(A+B)(C+D)$$

 

$$((A+B)(C+D))' = ((A+B)' + (C+D)')'$$

AOI Gate Implementation

 
- Derive sum-of-products for inverted output to find AOI implementation




OAI Gate Implementation

- Derive product-of-sums for inverted output to find OAI implementation

OAI

 

2x2 OAI Schematic Symbol

 


$$F = \prod M(0,1,3,5)$$

$$\Rightarrow F' = \prod M(2,4,6,7)$$


C \ AB	A			
	00	01	11	10
0	1	0	0	0
1	1	1	0	1

Diagram showing a Karnaugh map for F' with groupings for A, B, and C.

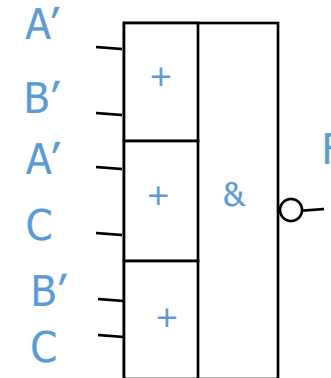

$$F' = (A' + B') (A' + C) (B' + C)$$


Circuit Diagram

 


SystemVerilog Implementation

- Library with components containing AOI gates etc.
- Need to create port maps to implement the circuit
- You start with a file where you only have to add the port maps and signal declarations


Circuit Diagram (with Signal names)

 

Test Bench Results

 

State Encoding				output
	y2	y1	y0	z
A	0	0	0	1
B	1	1	1	0
C	0	1	0	1
D	1	0	1	1
E	1	0	0	0

 

Summary

- Design Finite State Machines for traffic light and candy dispenser.
- Moore vs. Mealy machine
- FSM Assignment Courselab

To Do List

- Reading Material book “Digital Design”:
 - Section 3.4
- Assignments for this lecture:
 - Gated Practice Assignment Lecture 7

Thank you