

EE1D1: Digital Systems A


BSc. EE, year 1, 2025-2026, lecture 8

SystemVerilog Sequential Circuits

Computer Engineering Lab

Faculty of Electrical Engineering, Mathematics & Computer Science

Recap

 

Learning Objectives

As student you should be able to:

- Describe latches and flip-flops in SystemVerilog.
- Use the always statement in SystemVerilog to describe sequential circuits and combinational circuits.
- Describe Finite-State Machines in SystemVerilog.
- Describe counters in SystemVerilog.
- Simulate a sequential circuit in SystemVerilog.

Overview

- Recap
- D Flip-flop and Latch
- The Always Statement
- Finite State Machines
- Counters

Sections in book DDCA: 4.4 – 4.6



Learned earlier

```
module func1(input logic a, b, c,  
            output logic y);  
  
    logic n;  
  
    assign #1 y = n | c;    Order is not  
    assign #1 n = a & b;    important  
endmodule
```

```
module testfunc1();  
    logic a, b, c, y;  
  
    func1 dut(a, b, c, y);  
  
    initial begin  
        a = 0; b = 1; c = 0;  
        #10; a = 1;  
    end  
endmodule
```

Within this initial block, order is important.
Starting from begin, statements are executed
one after another (with specified delays)

Simulation with testbench

  

Sequential Logic


- SystemVerilog uses **idioms** to describe latches, flip-flops and FSMs
- Other coding styles may simulate correctly but produce incorrect hardware after synthesis
- So, you should **follow the recommended methods** to obtain reliable simulation results as well as good synthesis results.
- Always keep in mind that – although you may be using a high-level description - you are describing hardware: registers (flip-flops) and combinational logic, orchestrated by the clock.

EE1D1: Digital Systems A

**D flip-flop and
latch**

Describing a D flip-flop
 
```
module dff(input logic clk,  
           input logic d,  
           output logic q);  
  
    always_ff @ (posedge clk) // on a rising clock edge  
        q <= d; // q gets the value of d  
  
endmodule
```



`@(....)` is the sensitivity list.
It describes what triggers the
execution of the `always`
statement.

Describing a D flip-flop with reset

It is good practice to use resettable registers so that on **powerup** you can put your system in a known state.

synchronous reset => reset on
rising clock edge

asynchronous reset => reset at any
moment reset becomes 1

```
always_ff @ (posedge clk)
  if (reset) q <= 0;
  else q <= d;
```

```
always_ff @ (posedge clk, posedge reset)
  if (reset) q <= 0;
  else q <= d;
```


Registers

The following example shows a 4-bit register with **asynchronous reset** and **enable**. It retains its old value if both **reset** and **en** are FALSE.

```
module register4bit(input  logic      clk,
                     input  logic      reset,
                     input  logic      en,
                     input  logic [3:0] d,
                     output logic [3:0] q);


// asynchronous reset
always_ff @ (posedge clk, posedge reset)
  if      (reset) q <= 4'b0;
  else if (en)    q <= d;

endmodule
```

 

Describing a latch

 The **always_latch** statement is used to describe a latch



```
always_latch
    if (clk) q <= d;    // when clk = 1, q gets value of d
                          // when clk = 0, q remembers its value
```

A sensitivity list is not allowed; the **always_latch** statement is evaluated whenever one of the inputs (**clk** or **d**) changes value.


Normally, it is **not a good idea to use latches** in your circuit. They are transparent as long as $clk = 1$, so problematic combinational feedback loops may occur. Also, timing of input signals is more difficult to control.

The Always Statement

Using always statement to describe a combinational circuit

An **always_comb** statement can be used to describe a combinational circuit.

```
always_comb
begin
    p = a ^ b;
    q = a & b;
    s = p ^ cin;
    cout = q | (p & cin);
end
```

 

A sensitivity list is not allowed with **always_comb**; the block will be evaluated whenever one of the inputs (**a**, **b** and **cin**) change.

It is important that you specify *the value of all outputs in all cases*. Otherwise, unwanted latches may be created during synthesis.

```
always_comb
    if (s) y = x1;
    else y = x0;      ok
```

```
always_comb
    if (s) y = x1;
                           not ok
```

Using the **always** statement

A general **always** statement can also be used.

When it has no sensitivity list, the statement is evaluated whenever one of the inputs change:

```
always
```

When it has a sensitivity list, the statement is evaluated whenever one of the signals in the sensitivity list changes value:

```
always @ (a, b, cin)
```

where signal names in the sensitivity list may be preceded by **posedge** or **negedge** to indicate that evaluation is triggered by only a rising edge or falling edge event .

For flip-flops (registers), latches and combinational circuits, the usage of respectively **always_ff**, **always_latch** and **always_comb** is preferred.

The use of **always** should be restricted to testbenches.


Case Statement

A combinational circuit for a seven-segment display decoder that uses a case statement

```
module sevenseg(input logic [3:0] data,
                  output logic [6:0] segments);

  always_comb
    case(data)
      // abc_defg
      0: segments = 7'b111_1110;
      1: segments = 7'b011_0000;
      2: segments = 7'b110_1101;
      3: segments = 7'b111_1001;
      4: segments = 7'b011_0011;
      5: segments = 7'b101_1011;
      6: segments = 7'b101_1111;
      7: segments = 7'b111_0000;
      8: segments = 7'b111_1111;
      9: segments = 7'b111_0011;
      default: segments = 7'b000_0000;
    endcase
  endmodule
```

Synthesis:

 


Without default, outputs are not specified for all cases and latches will be inferred during synthesis!

If Statement

A priority circuit that uses a nested if-else statement

```
module priorityckt(input logic [3:0] a,  
                    output logic [3:0] y);  
  
    always_comb  
        if (a[3]) y = 4'b1000;  
        else if (a[2]) y = 4'b0100;  
        else if (a[1]) y = 4'b0010;  
        else if (a[0]) y = 4'b0001;  
        else y = 4'b0000;  
  
    endmodule
```

Synthesis:

 


Truth Tables with Don't Cares

- Truth tables may include don't cares to allow more logic simplification.
- The following shows how to describe the previous priority circuit with the inside keyword, which allows don't cares to be used.

```
module priority_case_dc(input logic [3:0] a,
                         output logic [3:0] y);
  always_comb
    case(a) inside
      4'b1??? : y = 4'b1000; // casez(a), as used in book,
      4'b01??? : y = 4'b0100; // is obsolete
      4'b001? : y = 4'b0010;
      4'b0001 : y = 4'b0001;
      default: y = 4'b0000;
    endcase
endmodule
```

Synthesis:

 

Blocking vs. Nonblocking Assignment

In an always statement, there is an important difference between using `<=` or `=` in an assignment.

- `<=` is a **nonblocking** assignment: The signal on the left receives the value **only after** the block has been evaluated. So, the assignments **are deferred**.
- `=` is a **blocking** assignment. The signal on the left receives the value **immediately** after the assignment. The execution of a subsequent statement is “blocked” until this has been done. So, the assignments are **immediate**, and the order **is important**.

```
always_ff @ (posedge clk)
begin
    n1 <= d; // nonblocking (deferred)
    q  <= n1; // nonblocking (deferred)
end
```

Suppose that initially $d = 1$, $n1 = 0$ and $q = 0$

Then, after 1 rising clock edge:

$n1 = 1$ and $q = 0$

And after a second rising clock edge:

$n1 = 1$ and $q = 1$

```
always_ff @ (posedge clk)
begin
    n1 = d; // blocking (immediate)
    q  = n1; // blocking (immediate)
end
```

$n1 = 1$ and $q = 1$

not different
from using $q = d$


$n1 = 1$ and $q = 1$

Blocking vs. Nonblocking Assignment


The different behavior also results in a different synthesis results.

(BTW: A synchronizer uses 2 D flip-flops in series to synchronize external inputs with clock.)
 
```
// Good synchronizer using
// nonblocking assignments
module syncgood(input logic clk,
                  input logic d,
                  output logic q);
    logic n1;
    always_ff @ (posedge clk)
    begin
        n1 <= d; // nonblocking
        q <= n1; // nonblocking
    end
endmodule
```



 
```
// Bad synchronizer using
// blocking assignments
module syncbad(input logic clk,
                  input logic d,
                  output logic q);
    logic n1;
    always_ff @ (posedge clk)
    begin
        n1 = d; // blocking
        q = n1; // blocking
    end
endmodule
```



Blocking vs. Nonblocking Assignment

For `always_comb` blocks it is ok to use blocking assignments:

```
always_comb
begin
    p = a ^ b;
    q = a & b;
    s = p ^ cin;
    cout = q | (p & cin);
end
```

 

Summary of rules for Signal Assignment

- **Synchronous sequential logic:** use `always_ff @ (posedge clk)` and nonblocking assignments (`<=`)

```
always_ff @ (posedge clk)  
q <= d; // nonblocking
```

- **Simple combinational logic:** use continuous assignments (`assign...`)

```
assign y = a & b;
```

- **More complex combinational logic:** use `always_comb` and blocking assignments (`=`)
- In an `always_comb` block, assign a value to *each* output for *all* input combinations.
- Assign a signal in *only one* `always` statement or continuous assignment statement.





Finite State Machines


Finite State Machines

- **Three blocks:**

  
- next state logic
- state register
- output logic



FSM Example 1: Divide by 3

 

 The arrow indicates the reset state
Sometimes also a double circle is used:



FSM Example 1: Divide by 3


```
module divideby3FSM(input logic clk,
                     input logic reset,
                     output logic y);

typedef enum logic [1:0] {S0, S1, S2} statetype;
statetype state, nextstate;

// state register
always_ff @(posedge clk, posedge reset)
  if (reset) state <= S0;
  else       state <= nextstate;

// next state logic
always_comb
  case (state)
    S0:      nextstate = S1;
    S1:      nextstate = S2;
    S2:      nextstate = S0;
    default: nextstate = S0;
  endcase

 // output logic
assign y = (state == S0);
endmodule
```




Note that a default case is used in the combinational block, to be sure that output **nextstate** receives a value in all cases.

When synthesized, this code will create a circuit with a register that has 2 flip-flops and an asynchronous reset.

FSM Example 2: Sequence Detector

Moore FSM

 

Which sequence will be detected?

Sequence Detector FSM: Moore

```
module patternMoore(input logic clk, reset, a,
                      output logic y);



typedef enum logic [1:0] {S0, S1, S2} statetype;
statetype state, nextstate;

// state register
always_ff @(posedge clk, posedge reset)
  if (reset) state <= S0;
  else        state <= nextstate;

// next state logic
always_comb
  case (state)
    S0:      if (a) nextstate = S0;
              else    nextstate = S1;
    S1:      if (a) nextstate = S2;
              else    nextstate = S1;
    S2:      if (a) nextstate = S0;
              else    nextstate = S1;
    default: nextstate = S0;
  endcase


// output logic
  assign y = (state == S2);
endmodule
```

Moore FSM

  

FSM Example 3: Sequence Detector

Mealy FSM

 

Sequence Detector FSM: Mealy


```
module patternMealy(input logic clk, reset, a,
                     output logic y);

  typedef enum logic {S0, S1} statetype;
  statetype state, nextstate;


  // state register
  always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else       state <= nextstate;

  // next state and output logic combined
  always_comb begin
    // make sure y receives value in all cases.
    y = 0;
    case (state)
      S0:   if (a) nextstate = S0;
             else   nextstate = S1;
      S1:   if (a) begin
              nextstate = S0;
              y = 1;
            end
             else   nextstate = S1;
      default: nextstate = S0;
    endcase
  end
endmodule
```


Mealy FSM

 

Mealy FSM

 

Synthesis:

 

FSM Testbench

```
`timescale 1ns/1ps

module patternMoore_tb();

logic clk;
logic reset;
logic a, y;



patternMoore dut (clk, reset, a, y);

initial
  clk = 0;
always
  #10 clk = ~clk;

initial begin
  reset = 1; a = 0;
  #20; reset = 0;
  #20;           a = 1;
end

endmodule
```

Moore FSM

  

Important: to avoid setup/hold time violations (next lecture), do not change input signals on the rising clock edge. Instead, do it on the negative clock edge.

EE1D1: Digital Systems A

Counters

Counter

A counter is an FSM that adds 1 to its state in its next state logic.


Usually there is no output logic.

```
module counter(input logic clk, reset, enable,
                output logic [7:0] count);

    logic [7:0] next_count;


    // register
    always_ff @(posedge clk)
    begin
        if (reset) count <= 0;
        else count <= next_count;
    end

     // next state logic
    always_comb
    begin
        if (enable) next_count = count + 1;
        else next_count = count;
    end
endmodule
```



Counter simulation
 
```
module counter_tb();  
  
logic clk;  
logic reset;  
logic enable;  
logic [7:0] count;  
  
counter dut (clk, reset, enable, count);  
  
initial  
    clk = 0;  
always  
    #10 clk = ~clk;  
  
initial begin  
    reset = 1; enable = 0;  
    #20; reset = 0;  
    #40; enable = 1;  
end  
  
endmodule
```



Summary

We have shown how to describe in SystemVerilog:

- Latches and flip-flops.
- More complex combinational circuits like decoders and encoders.
- Finite-State Machines.
- Counters.
- Testbenches for these circuits.