

EE1C2 “Linear Circuits B”

Week 2.8

Francesco Fioranelli / Ioan E. Lager

Today

- Recapitulation of week 2.7
- New topics:
 - Circuit analysis via Laplace transform
 - equivalent circuits in the Laplace-domain (s -domain)
 - circuit analysis in the Laplace-domain
 - Transfer functions in the Laplace-domain
- Summary of the day
- Next time

Recap of week 2.7

- Direct Laplace transform & properties
- Inverse Laplace transform
- Algebraic (+ table lookup) inversion method $\Rightarrow$ requisite skills:
 - familiarity with the Laplace transform properties
 - familiarity with the table of Laplace transforms
 - basic algebra: breaking down fractions

Recap of week 2.7

$$V_{\text{in}}(t) = A \cos(\omega t + \phi)$$

$$\xrightarrow{\mathcal{L}[V_{\text{in}}(t)]}$$

$$V_{\text{in}} = A \exp(j\phi)$$

$$\frac{d^3 V}{dt^3} + a \frac{d^2 V}{dt^2} + b \frac{dV}{dt} + cV = f(t)$$

Trigonometry

$$(j\omega)^3 V + a(j\omega)^2 V + b(j\omega)V + cV = F$$

Complex algebra

$$V_{\text{out}}(t) = B \cos(\omega t + \theta)$$

$$\xleftarrow{\mathcal{L}^{-1}[V_{\text{out}}(s)]}$$

$$V_{\text{out}} = B \exp(j\theta)$$

Recap of week 2.7

Definition:

$$\mathcal{L}[f(t)] = F(s) = \int_{0^-}^{\infty} f(t)e^{-st} dt \quad \text{with } s = \sigma + j\omega$$

Properties of the Laplace transform.

Property	$f(t)$	$F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F_1(s) + a_2F_2(s)$
Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
Time shift	$f(t-a)u(t-a)$	$e^{-as}F(s)$
Frequency shift	$e^{-at}f(t)$	$F(s+a)$
Time differentiation	$\frac{df}{dt}$	$sF(s) - f(0^-)$
	$\frac{d^2f}{dt^2}$	$s^2F(s) - sf(0^-) - f'(0^-)$
	$\frac{d^3f}{dt^3}$	$s^3F(s) - s^2f(0^-) - sf'(0^-) - f''(0^-)$
	$\frac{d^nf}{dt^n}$	$s^nF(s) - s^{n-1}f(0^-) - s^{n-2}f'(0^-) - \dots - f^{(n-1)}(0^-)$
Time integration	$\int_0^t f(x)dx$	$\frac{1}{s}F(s)$
Frequency differentiation	$tf(t)$	$-\frac{d}{ds}F(s)$
Frequency integration	$\frac{f(t)}{t}$	$\int_s^{\infty} F(s)ds$


Recap of week 2.7

Quantity		Measure unit
Time-domain		
time	t	s
voltage	$v(t)$	V
current	$i(t)$	A
Laplace-domain	$\mathcal{L}[f(t)] = F(s) = \int_{0^-}^{\infty} f(t)e^{-st} dt$ with $s = \sigma + j\omega$	
Laplace variable	s	s^{-1}
voltage	$V(s)$	V·s
current	$I(s)$	A·s


Circuit analysis via Laplace transform

Laplace transform & circuit elements: the resistance

$$v(t) = Ri(t)$$

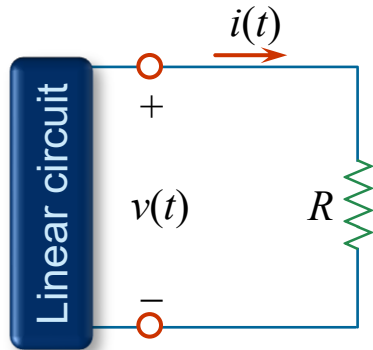

$$\mathbf{V}(s) = R\mathbf{I}(s)$$

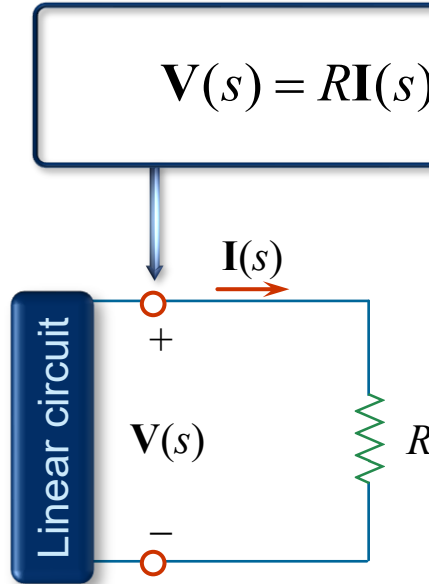


Properties of the Laplace transform.

Property	$f(t)$	$F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F_1(s) + a_2F_2(s)$
Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
Time shift	$f(t - a)u(t - a)$	$e^{-as}F(s)$

Laplace transform & circuit elements: the capacitance


$$i(t) = C \frac{dv(t)}{dt}$$
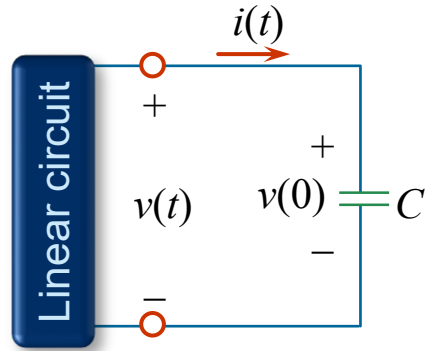
$$v(t) = \frac{1}{C} \int_0^t i(x) dx + v(0)$$



$$\int_0^t f(x) dx \Leftrightarrow \frac{1}{s} F(s) + u(t) \Leftrightarrow \frac{1}{s}$$

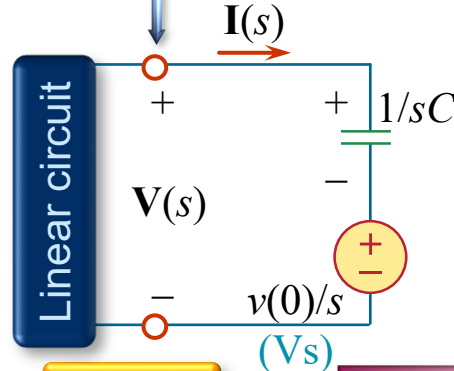
$$\mathbf{V}(s) = \frac{\mathbf{I}(s)}{sC} + \frac{v(0)}{s}$$



Main

$$\frac{df}{dt} \Leftrightarrow sF(s) - f(0^-)$$
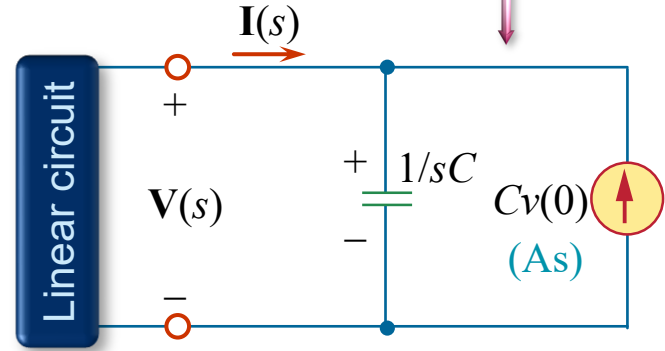
$$\mathbf{I}(s) = sC\mathbf{V}(s) - Cv(0)$$




Thévenin-Norton

Laplace transform & circuit elements: the inductance


$$v(t) = L \frac{di(t)}{dt}$$
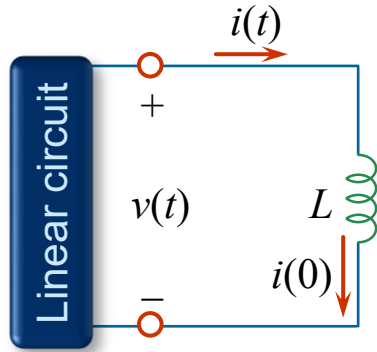
$$i(t) = \frac{1}{L} \int_0^t v(x) dx + i(0)$$




$$\frac{df}{dt} \Longleftrightarrow sF(s) - f(0^-)$$
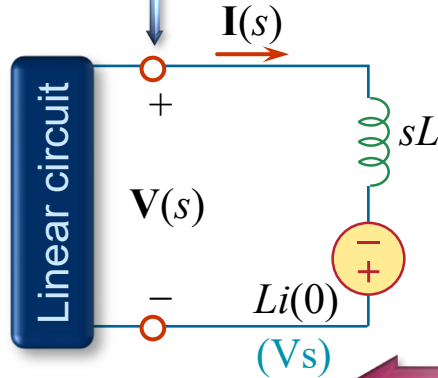
$$\mathbf{V}(s) = sL\mathbf{I}(s) - Li(0)$$



$$\int_0^t f(x) dx \Longleftrightarrow \frac{1}{s} F(s) + u(t) \Longleftrightarrow \frac{1}{s}$$
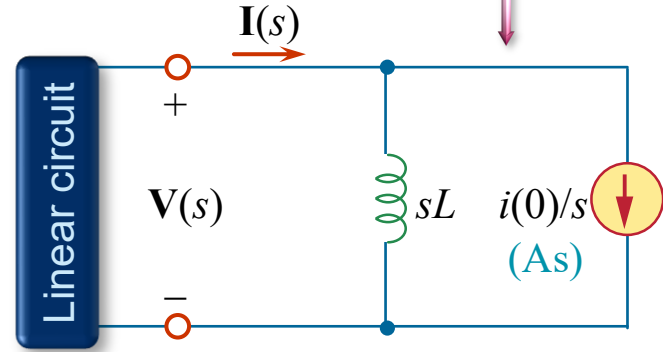
$$\mathbf{I}(s) = \frac{\mathbf{V}(s)}{sL} + \frac{i(0)}{s}$$




Norton-Thévenin

Main

Laplace transform & circuit elements: magnetically coupled inductances


$$v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt}$$
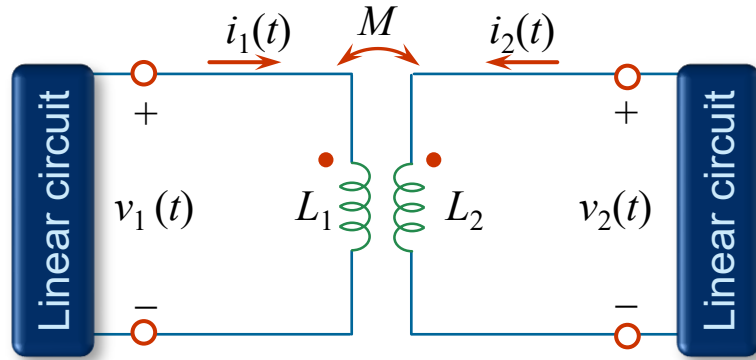
$$v_2(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$$



$$\mathbf{V}_1(s) = sL_1\mathbf{I}_1(s) - L_1i_1(0) + sM\mathbf{I}_2(s) - Mi_2(0)$$
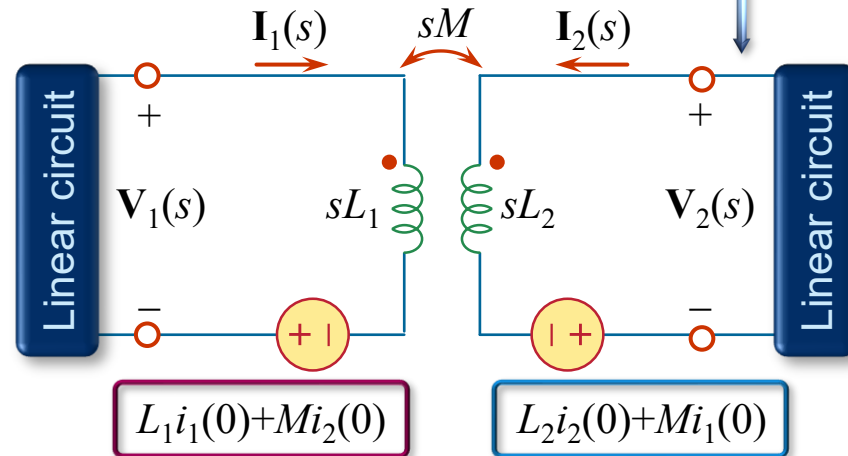
$$\mathbf{V}_2(s) = sL_2\mathbf{I}_2(s) - L_2i_2(0) + sM\mathbf{I}_1(s) - Mi_1(0)$$



Laplace transform & circuit elements: problem-solving strategy

- **Step 1:** Assume that the circuit has reached steady state before a switch is moved:
 - i. draw the circuit valid for $t = 0^-$ replacing capacitors with open circuits and inductors with short circuits;
 - ii. solve for the initial conditions: voltages across capacitor and currents flowing through inductor

Remember that $v_C(0^-) = v_C(0^+) = v_C(0)$ and $i_L(0^-) = i_L(0^+) = i_L(0)$

- **Step 2:** Draw the circuit for $t > 0 \Rightarrow$ use the equivalent circuits for circuit elements $\longleftrightarrow$ writing Laplace-domain transformed, integro-differential equations

Laplace transform & circuit elements: problem-solving strategy


- **Step 3:** Use circuit analysis techniques for analysing the resulting circuit $\Rightarrow$ Laplace-domain algebraic equations
- **Step 4:** Solve the algebraic equations for the variable of interest $\Rightarrow$ the result will be a ratio of polynomials in the complex variable s
- **Step 5:** Perform an inverse Laplace transform to solve for the circuit response in the time-domain $\Rightarrow$ **revisit the algebraic + table lookup inversion steps!!!**



La Persistance de la mémoire

Analysis: example



- Determine $v_o(t)$ in the circuit:

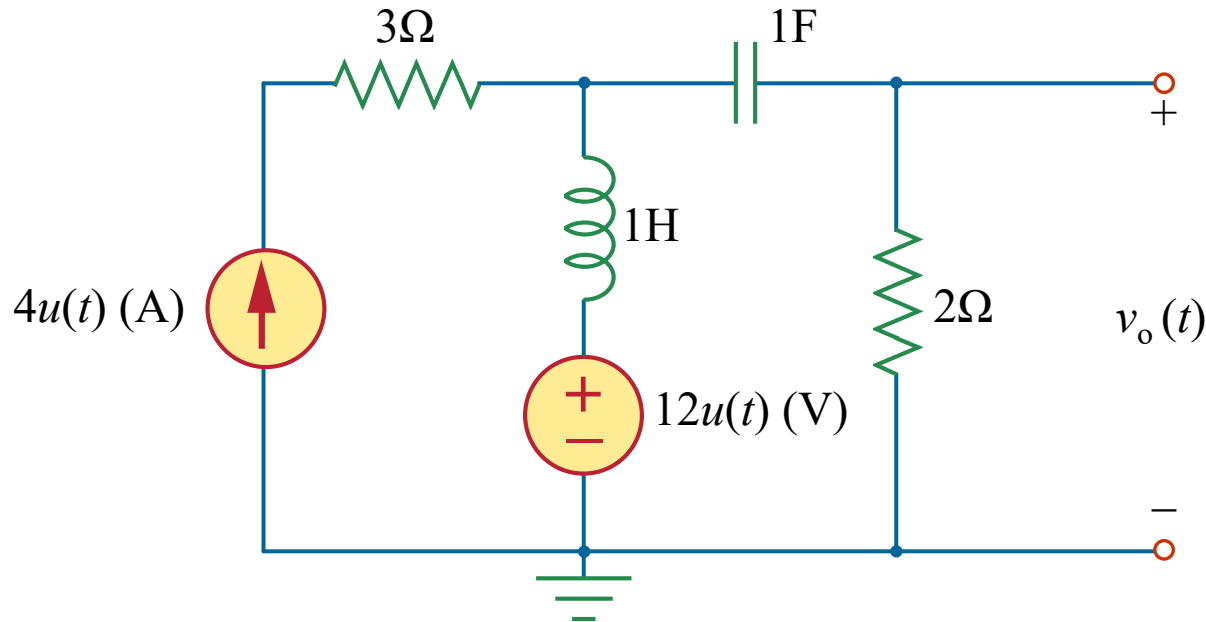

Analysis: example

Laplace-domain circuit

Resistances

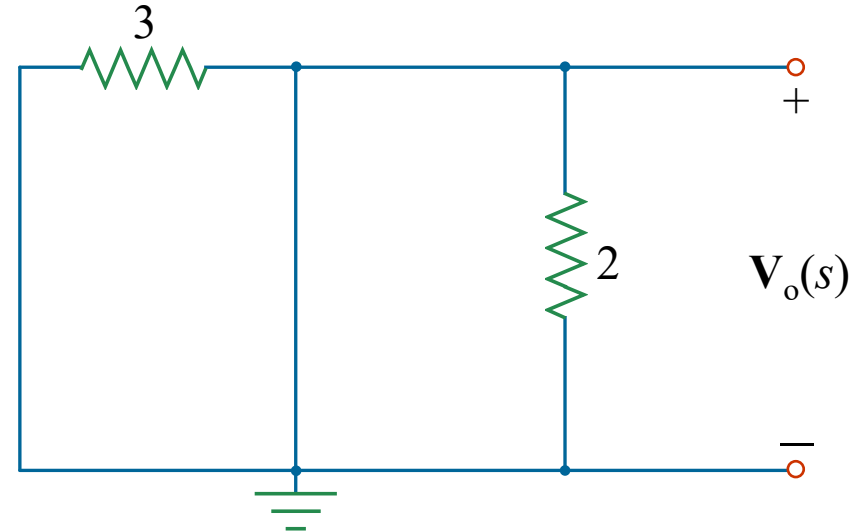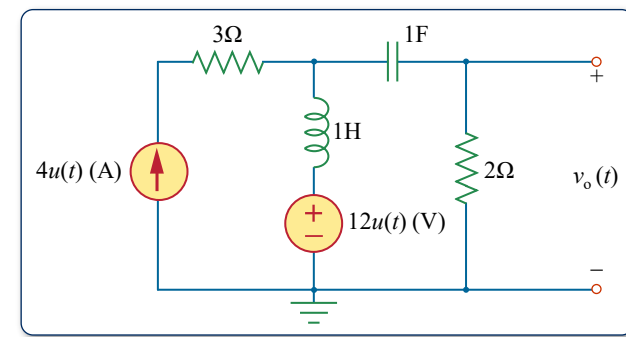



Analysis: example

Laplace-domain circuit

Sources

Laplace transform pairs.*





$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$

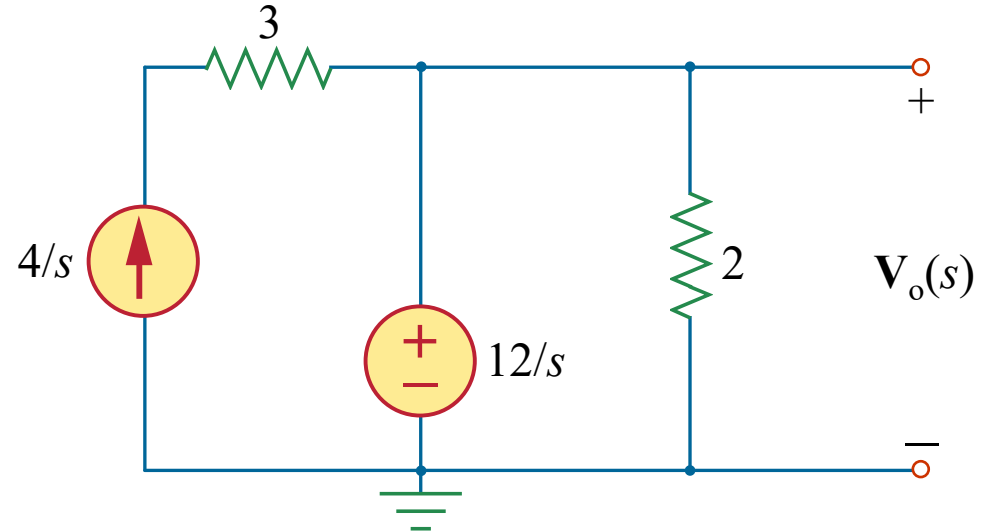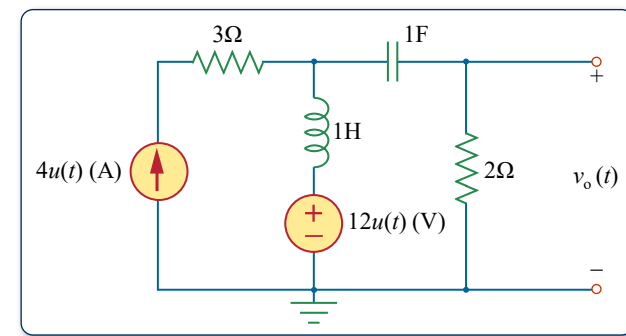

Analysis: example

Laplace-domain circuit




Inductances

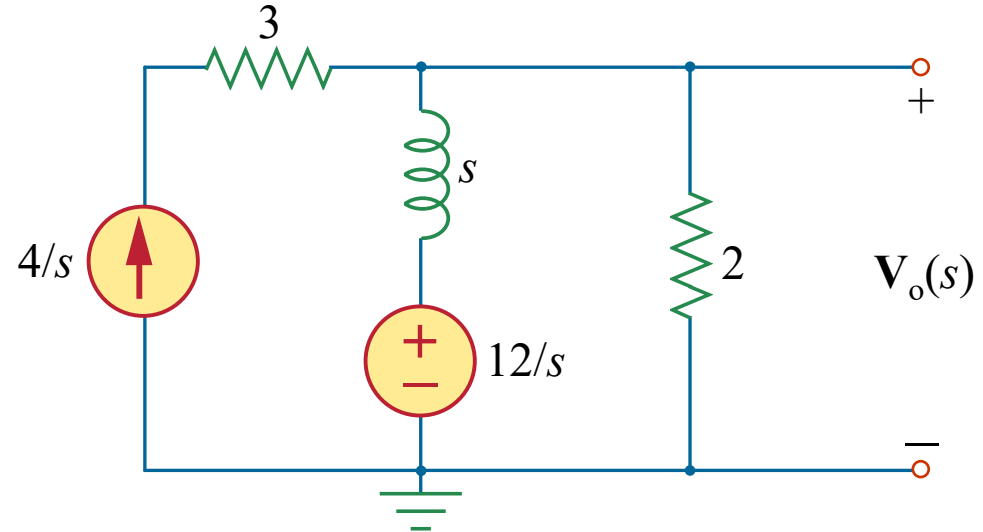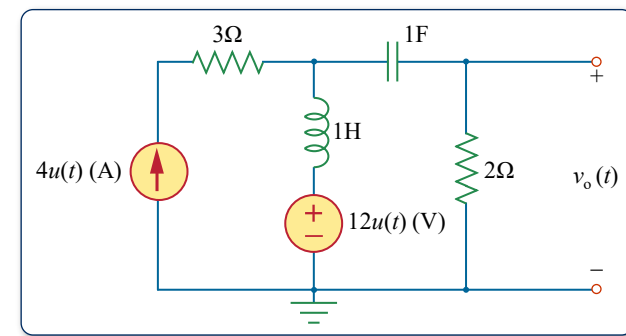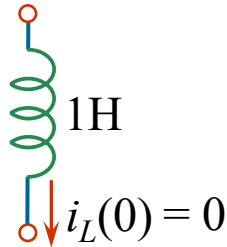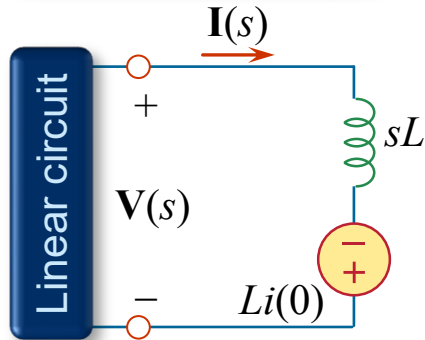



Analysis: example

Laplace-domain circuit

Capacitances

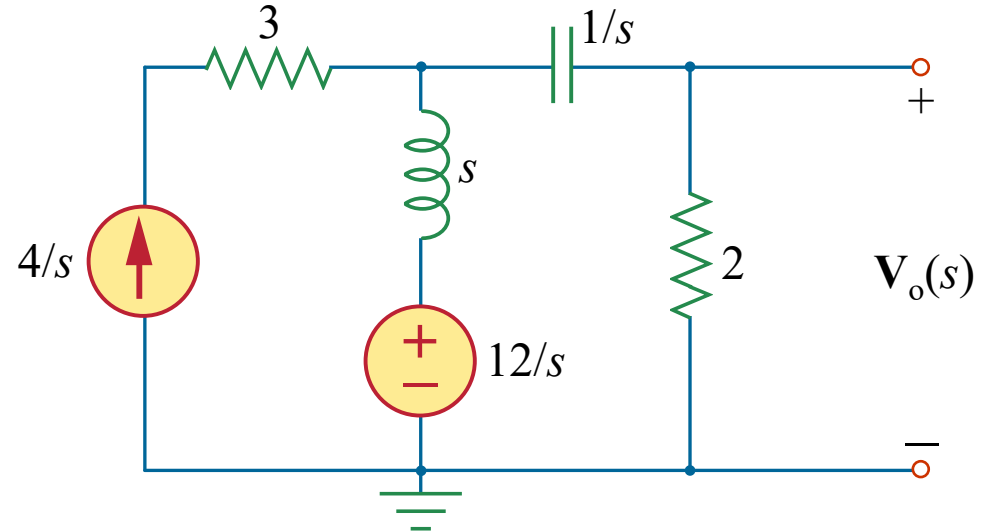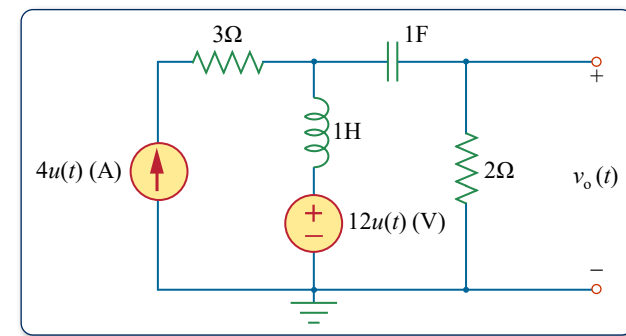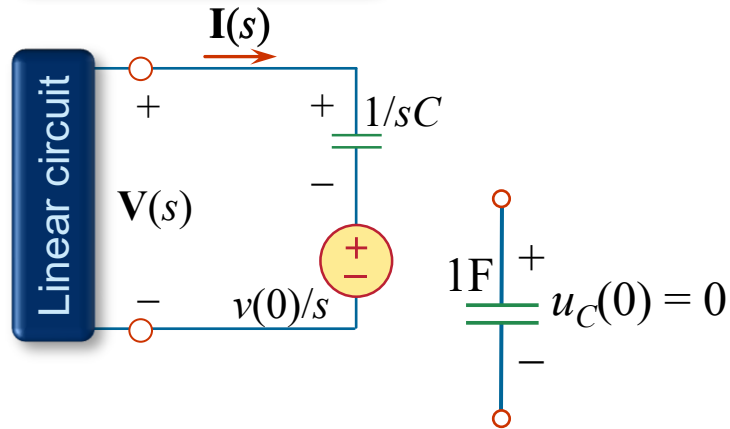


Analysis: example

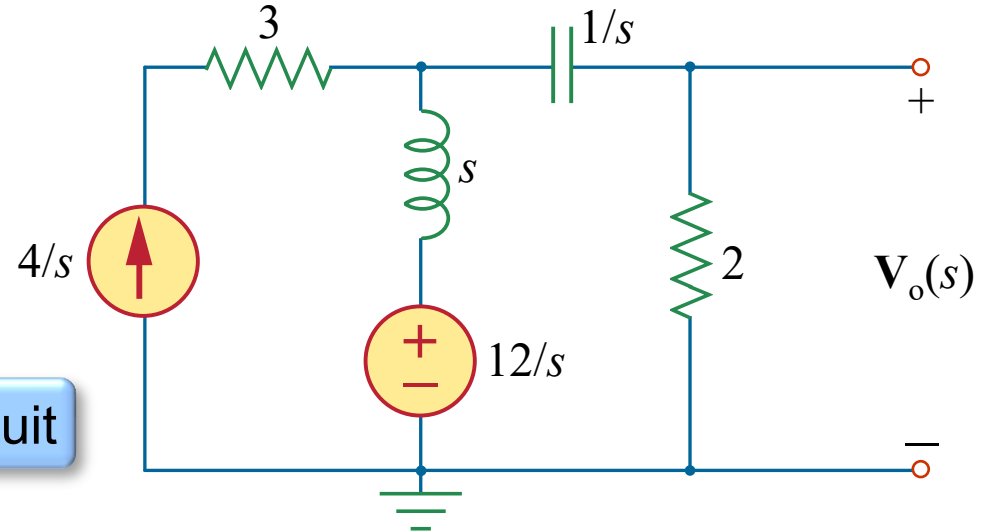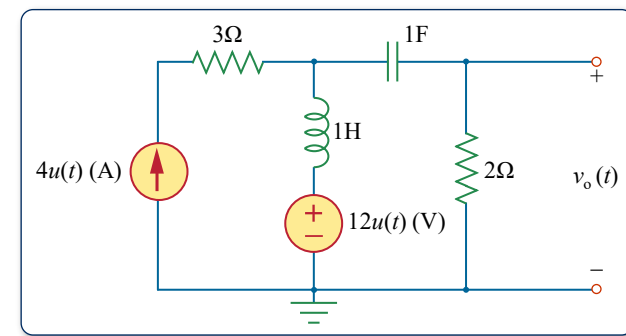

Assembled Laplace-domain circuit

Analysis: example

Nodal analysis

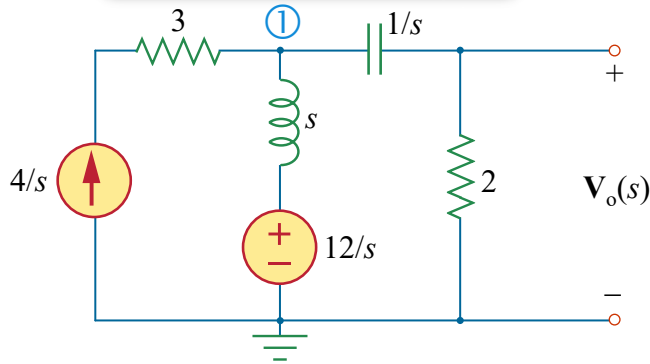


KCL at node ①

$$-\frac{4}{s} + \frac{V_1(s) - \frac{12}{s}}{s} + \frac{V_1(s)}{\frac{1}{s} + 2} = 0$$

Analysis: example

Nodal analysis

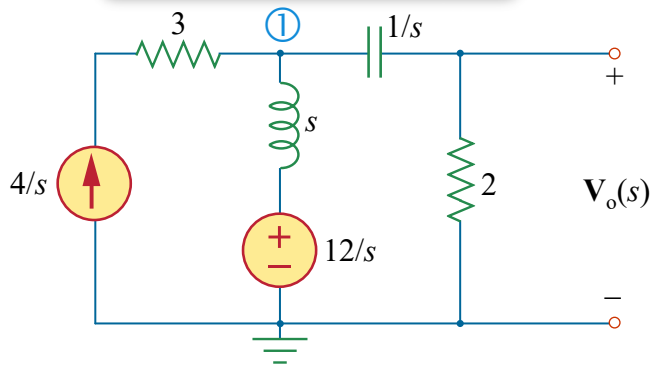

KCL at node ①

$$-\frac{4}{s} + \frac{V_1(s) - \frac{12}{s}}{s} + \frac{V_1(s)}{\frac{1}{s} + 2} = 0$$

$$V_1(s) = \frac{4(s+3)(2s+1)}{s(s^2 + 2s + 1)}$$


Apply voltage division

$$V_o(s) = V_1(s) \left(\frac{2}{\frac{1}{s} + 2} \right) = V_1(s) \left(\frac{2s}{2s+1} \right)$$

$$= \frac{8(s+3)}{(s+1)^2}$$

Analysis: example

Mesh analysis

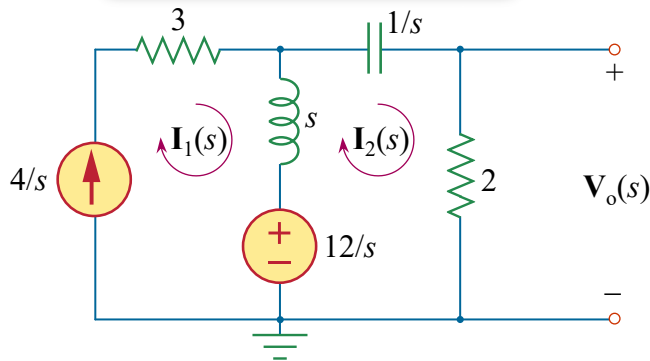

KVL on mesh $\mathbf{I_1(s)}$

$$\mathbf{I_1(s) = \frac{4}{s}}$$

KVL on mesh $\mathbf{I_2(s)}$

$$\frac{12}{s} - [\mathbf{I_2(s) - I_1(s)}]s - \frac{\mathbf{I_2(s)}}{s} - 2\mathbf{I_2(s)} = 0$$

substitute $\mathbf{I_1(s)}$




$$\mathbf{I_2(s) = \frac{4(s+3)}{(s+1)^2}}$$

account for the
 2Ω resistance

$$\mathbf{V_o(s) = \frac{8(s+3)}{(s+1)^2}}$$




Analysis: example

Superposition

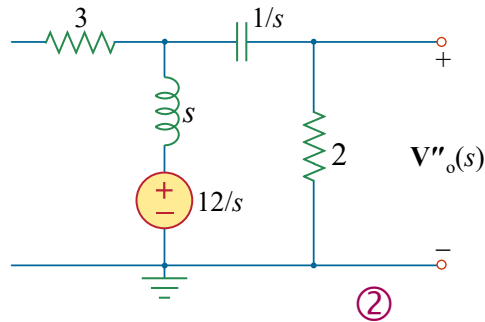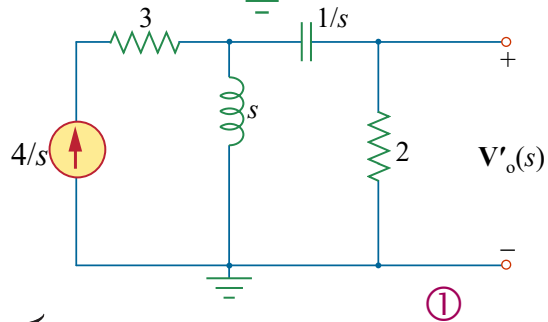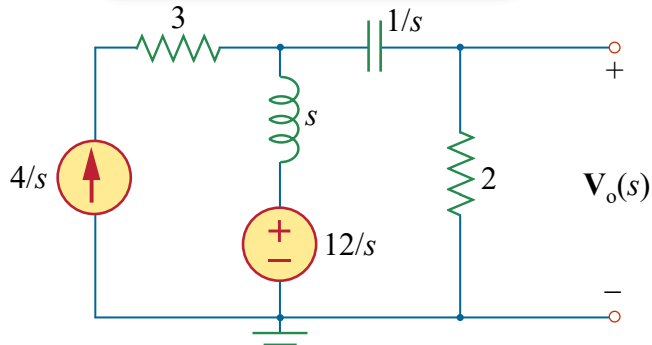

Analysis: example

Superposition

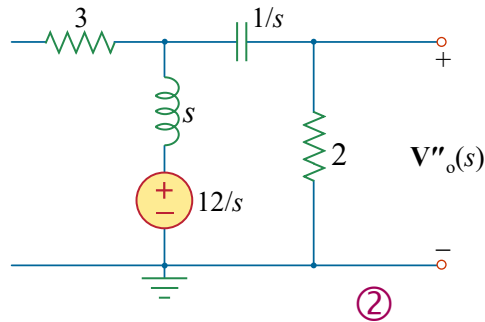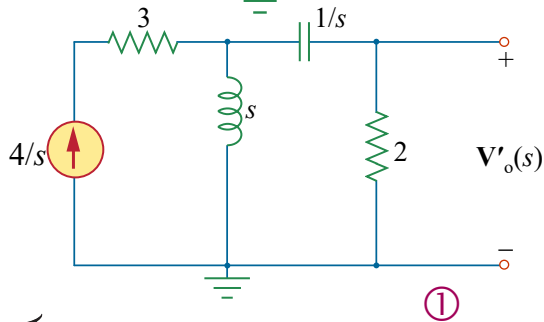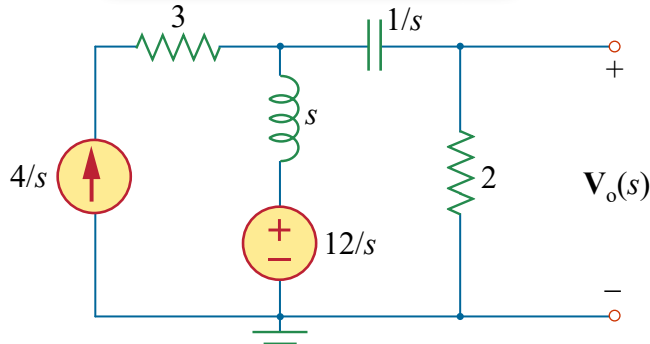



$$\textcircled{1}: V'_o(s) = \left[\frac{2 \frac{4}{s} s}{s + \frac{1}{s} + 2} \right] = \frac{8s}{s^2 + 2s + 1}$$

$$\textcircled{2}: V''_o(s) = \left[\frac{\frac{12}{s} 2}{s + \frac{1}{s} + 2} \right] = \frac{24}{s^2 + 2s + 1}$$

$$V_o(s) = V'_o(s) + V''_o(s) = \frac{8(s+3)}{(s+1)^2}$$

Analysis: example

Inversion to time-domain

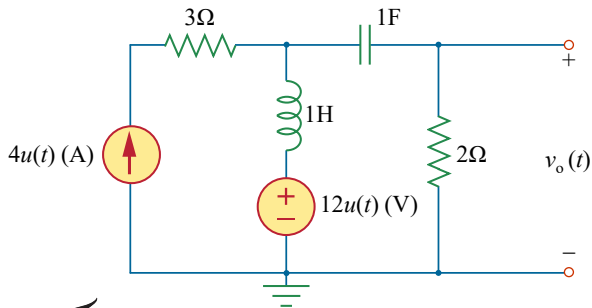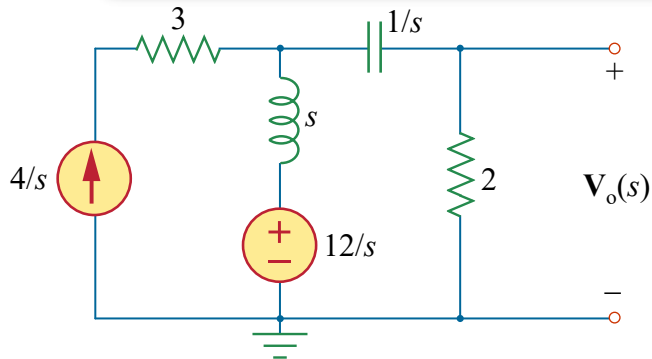

$$\begin{aligned} V_o(s) &= \frac{8(s+3)}{(s+1)^2} \\ &= \frac{K_{11}}{(s+1)^2} + \frac{K_{12}}{s+1} \\ &= \frac{16}{(s+1)^2} + \frac{8}{s+1} \end{aligned}$$

$$v_o(t) = (16te^{-t} + 8e^{-t})u(t) \text{ V}$$

Laplace transform pairs.*

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$
e^{-at}	$\frac{1}{s+a}$
t	$\frac{1}{s^2}$

Properties of the Laplace transform.

Property	$f(t)$	$F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F_1(s) + a_2F_2(s)$
Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
Time shift	$f(t-a)u(t-a)$	$e^{-as}F(s)$
Frequency shift	$e^{-at}f(t)$	$F(s+a)$

Transfer functions in the Laplace-domain

Transfer functions

- Laplace domain definition:

$$\mathbf{H}(s) = \frac{\mathbf{Y}_o(s)}{\mathbf{X}_i(s)}$$



$$\mathbf{Y}_o(s) = \mathbf{H}(s) \cdot \mathbf{X}_i(s)$$

- Particular cases:

- unit impulse response:

$$\mathbf{X}_i(s) = 1 \Rightarrow x_i(t) = \delta(t)$$

- time-domain response:

$$y_o(t) = h(t)$$

Laplace transform pairs.*

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$

Properties of the Laplace transform.

Property	$f(t)$	$F(s)$
Time integration	$\int_0^t f(x) dx$	$\frac{1}{s} F(s)$
Initial value	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
Convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$

Transfer functions

- Laplace domain definition:

$$\mathbf{H}(s) = \frac{\mathbf{Y}_o(s)}{\mathbf{X}_i(s)}$$



$$\mathbf{Y}_o(s) = \mathbf{H}(s) \cdot \mathbf{X}_i(s)$$

- Particular cases:

- step response:

$$\mathbf{X}_i(s) = 1/s \Rightarrow \mathbf{Y}_o(s) = \mathbf{H}(s)/s$$

- time-domain response:

$$y_o(t) = h(t) * u(t) = \int_0^t h(\tau) d\tau$$

Laplace transform pairs.*

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$

Properties of the Laplace transform.

Property	$f(t)$	$F(s)$
Time integration	$\int_0^t f(x) dx$	$\frac{1}{s} F(s)$
Initial value	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
Convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$

Transfer functions

- Laplace domain definition:

$$\mathbf{H}(s) = \frac{\mathbf{Y}_o(s)}{\mathbf{X}_i(s)}$$



$$\mathbf{Y}_o(s) = \mathbf{H}(s) \cdot \mathbf{X}_i(s)$$

- Particular cases:

- step response:

$$\mathbf{X}_i(s) = 1/s \Rightarrow \mathbf{Y}_o(s) = \mathbf{H}(s)/s$$

- time-domain response:

$$y_o(t) = h(t) * u(t) = \int_0^t h(\tau) d\tau$$

The transfer function provides critical information on the operation and the stability of a system

Stable systems:
All poles and zeros lie in the left half of the s -plane


Recap: characteristic equation

Case 1: overdamped circuit

- $s_1 \neq s_2$, **and** s_1 and s_2 are real $\longrightarrow F(s) = \frac{k_1}{s + \underbrace{s_1}_{\text{simple poles}}} + \frac{k_2}{s + \underbrace{s_2}_{\text{simple poles}}}$
- discriminant: $b^2 - 4c > 0$

$$s_{1,2} = -\frac{b}{2} \pm \frac{\sqrt{b^2 - 4c}}{2}$$
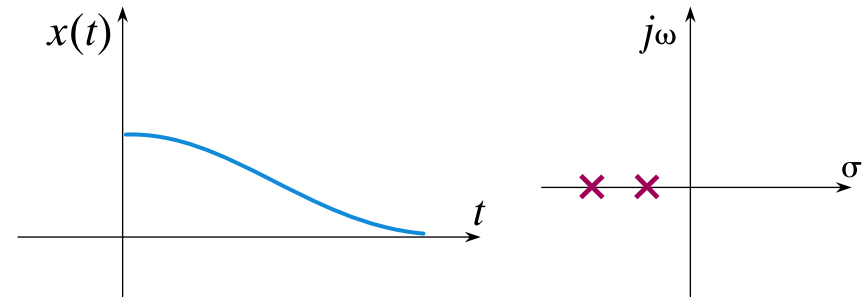
$$x(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} + K_3$$



Recap: characteristic equation

Case 2: underdamped circuit



- $s_1 \neq s_2$, **and** s_1 and s_2 are complex $\longrightarrow F(s) = \frac{k_1}{s + \underbrace{s_1}} + \frac{k_2}{s + \underbrace{s_2}}$
 - discriminant: $b^2 - 4c < 0$
- complex conjugate poles

$$s_{1,2} = -\frac{b}{2} \pm j \frac{\sqrt{4c - b^2}}{2} = -\sigma \pm j\omega_d$$

$$x(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} + K_3$$


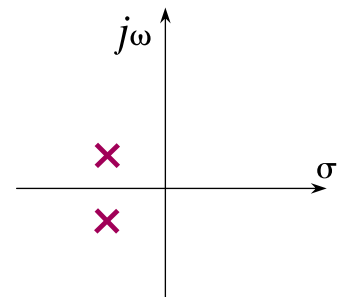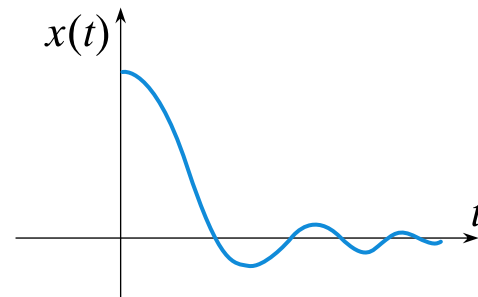
$$x(t) = e^{-\sigma t} [A \cos(\omega_d t) + B \sin(\omega_d t)] + k_3$$



Recap: characteristic equation



Case 3: critically damped circuit

- $s_1 = s_2$, **and** s_1 and s_2 are real $\longrightarrow F(s) = \frac{k_1}{s + \textcircled{s_1}} + \frac{k_2}{(s + \textcircled{s_1})^2}$
- discriminant: $b^2 - 4c = 0$

overlapped poles


$$s_1, s_2 = -\frac{b}{2}$$

$$x(t) = (K_1 + K_2 t) e^{s_1 t} + K_3$$

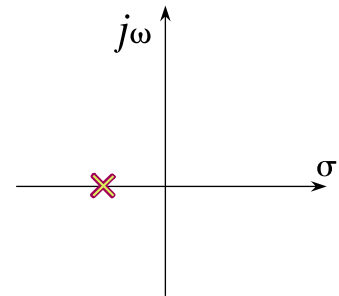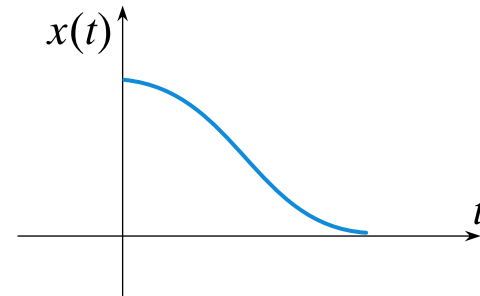

Transfer function: example

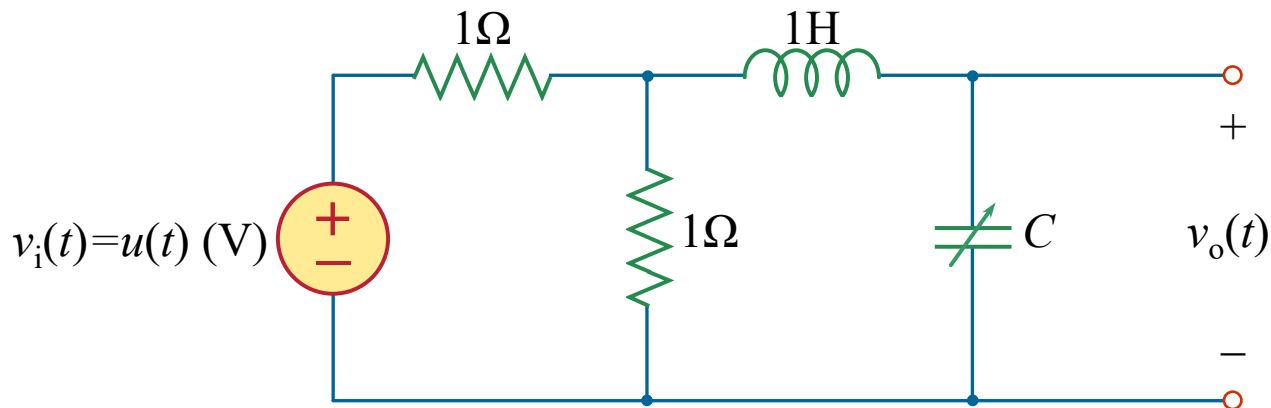
- Determine $V_o(s)/V_i(s)$ for the circuit in the figure below and the step response




3 cases:

1. $C = 8F$
2. $C = 16F$
3. $C = 32F$


Transfer function: example

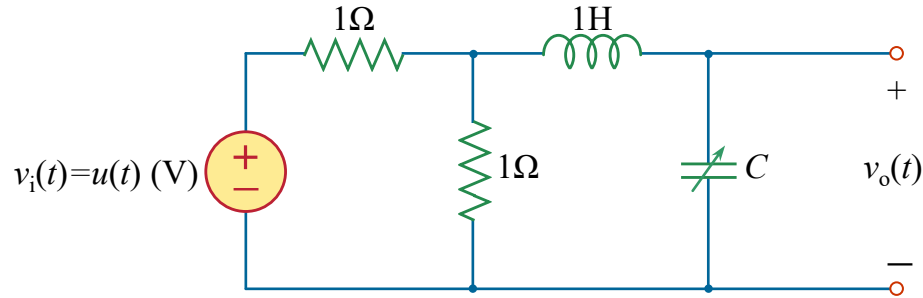

Laplace-domain circuit

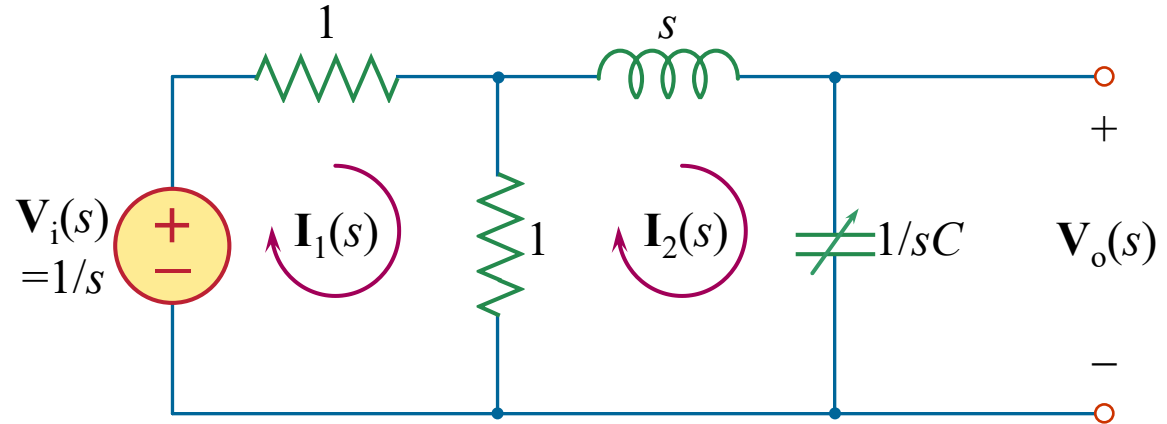

Transfer function: example

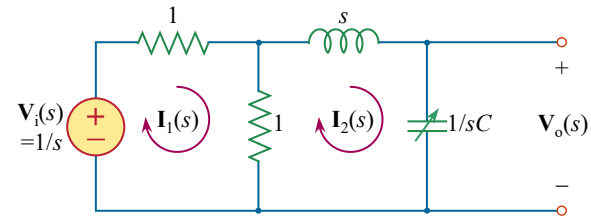

- Transfer function:

$$\mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_i(s)} = \frac{\frac{1}{2C}}{s^2 + \frac{1}{2}s + \frac{1}{C}}$$

- Step response:

$$\mathbf{V}_o(s) = \frac{\frac{1}{2C}}{s \left(s^2 + \frac{1}{2}s + \frac{1}{C} \right)}$$

KVL on mesh $\mathbf{I}_2(s)$

$$-\mathbf{I}_1(s) + \left(s + \frac{1}{sC} + 1 \right) \mathbf{I}_2(s) = 0$$

KVL on mesh $\mathbf{I}_1(s)$

$$2\mathbf{I}_1(s) - \mathbf{I}_2(s) = \mathbf{V}_i(s)$$

$$\mathbf{V}_o(s) = \frac{1}{sC} \mathbf{I}_2(s)$$


Transfer function: example

- Transfer function:


$$\mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_i(s)} = \frac{\frac{1}{2C}}{s^2 + \frac{1}{2}s + \frac{1}{C}} = \frac{\frac{1}{16}}{s^2 + \frac{1}{2}s + \frac{1}{8}} = \frac{\frac{1}{16}}{\left(s + \frac{1}{4} - \frac{j}{4}\right)\left(s + \frac{1}{4} + \frac{j}{4}\right)}$$

- Step response:

$$\mathbf{V}_o(s) = \frac{\frac{1}{16}}{s\left(s + \frac{1}{4} - \frac{j}{4}\right)\left(s + \frac{1}{4} + \frac{j}{4}\right)}$$

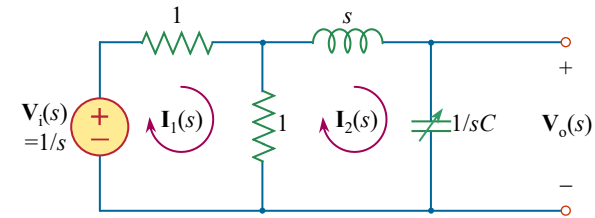


Case 1: $C = 8\text{F}$

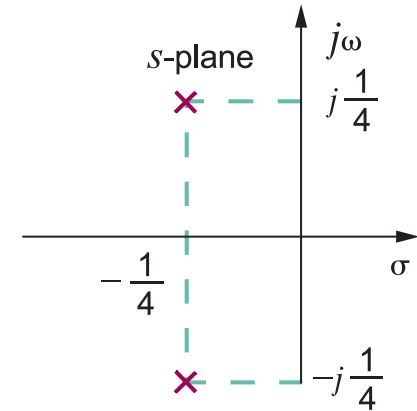

Transfer function: example

- Step response:

$s \rightarrow t$

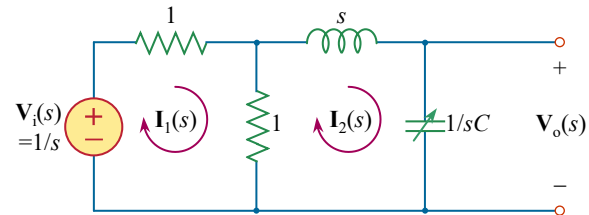

Case 1: $C = 8\text{F}$

$$V_o(s) = \frac{1}{16} \frac{1}{s \left(s + \frac{1}{4} - \frac{j}{4} \right) \left(s + \frac{1}{4} + \frac{j}{4} \right)}$$

$$= \frac{\frac{1}{2}}{s} + \frac{-\frac{1}{2}(s + \frac{1}{4})}{(s + \frac{1}{4})^2 + (\frac{1}{4})^2} + \frac{-\frac{1}{2}(\frac{1}{4})}{(s + \frac{1}{4})^2 + (\frac{1}{4})^2}$$

Also follows from the final value theorem

shift in s -domain $\rightarrow e^{-at}$

$$v_o(t) = \left[\frac{1}{2} - \frac{1}{2} e^{-t/4} \left(\cos \frac{t}{4} + \sin \frac{t}{4} \right) \right] u(t) \text{ V}$$


$$= \left[\frac{1}{2} + \frac{1}{\sqrt{2}} e^{-t/4} \cos \left(\frac{t}{4} + 135^\circ \right) \right] u(t) \text{ V}$$

$$e^{-at} \sin \omega t$$

$$\frac{\omega}{(s+a)^2 + \omega^2}$$

$$e^{-at} \cos \omega t$$

$$\frac{s+a}{(s+a)^2 + \omega^2}$$

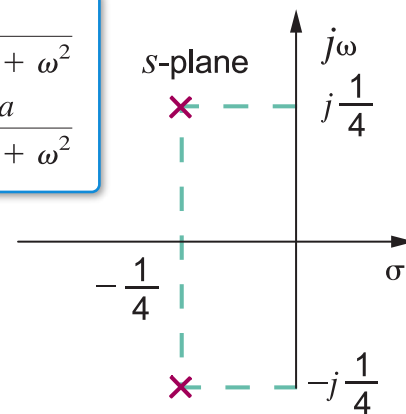


Transfer function: example

- Transfer function:


$$\mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_i(s)} = \frac{\frac{1}{2C}}{s^2 + \frac{1}{2}s + \frac{1}{C}} = \frac{\frac{1}{32}}{s^2 + \frac{1}{2}s + \frac{1}{16}} = \frac{\frac{1}{32}}{\left(s + \frac{1}{4}\right)^2}$$

- Step response:

$$\mathbf{V}_o(s) = \frac{\frac{1}{32}}{s \left(s + \frac{1}{4}\right)^2}$$

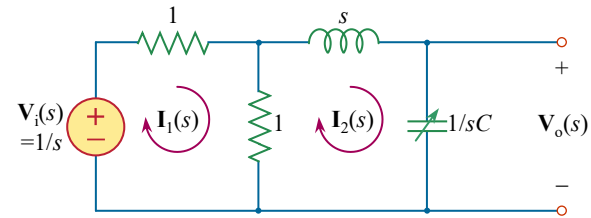


Case 2: $C = 16\text{F}$

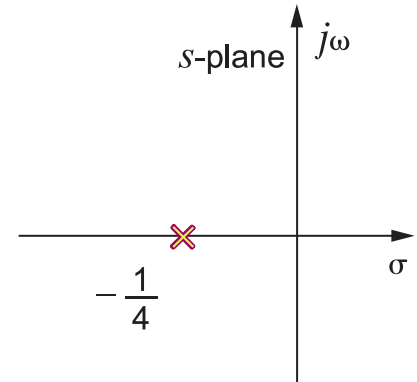

Transfer function: example

- Step response:

$$s \longrightarrow t$$

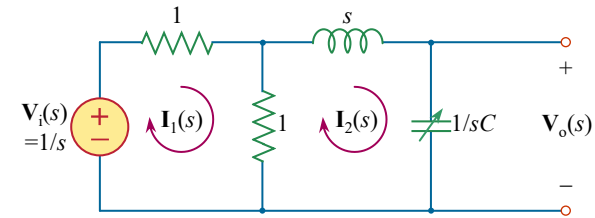

Case 2: $C = 16\text{F}$

$$V_o(s) = \frac{1}{32} \frac{1}{s \left(s + \frac{1}{4} \right)^2}$$


Also follows from the final value theorem

$$= \frac{\frac{1}{2}}{s} + \frac{-\frac{1}{2}}{s + \frac{1}{4}} + \frac{-\frac{1}{8}}{\left(s + \frac{1}{4} \right)^2}$$

shift in s -domain $\Rightarrow e^{-at}$

$$v_o(t) = \left[\frac{1}{2} - \left(\frac{t}{8} + \frac{1}{2} \right) e^{-t/4} \right] u(t) \text{ V}$$

e^{-at}	$\frac{1}{s + a}$
t	$\frac{1}{s^2}$

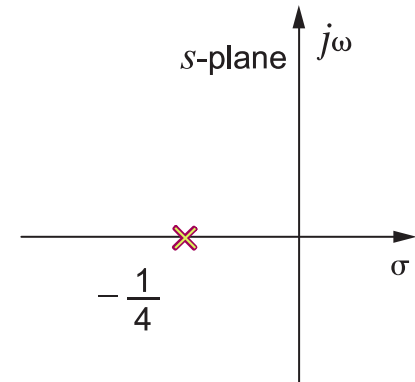


Transfer function: example

- Transfer function:


$$\mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_i(s)} = \frac{\frac{1}{2C}}{s^2 + \frac{1}{2}s + \frac{1}{C}} = \frac{\frac{1}{64}}{s^2 + \frac{1}{2}s + \frac{1}{32}} = \frac{\frac{1}{64}}{(s + 0,427)(s + 0,073)}$$

- Step response:

$$\mathbf{V}_o(s) = \frac{\frac{1}{64}}{s(s + 0,427)(s + 0,073)}$$

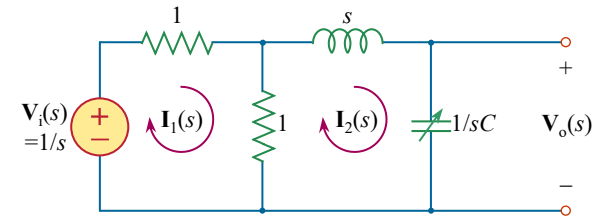

Case 3: $C = 32\text{F}$

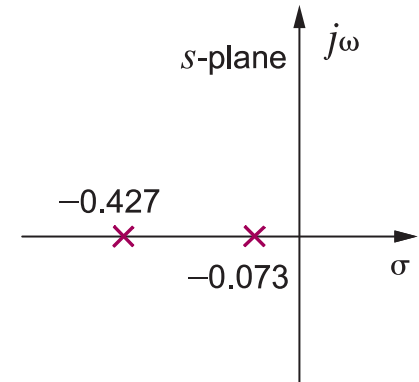

Transfer function: example

- Step response:


$$s \rightarrow t$$

$$V_o(s) = \frac{1}{64} \frac{1}{s(s + 0,427)(s + 0,073)}$$

$$= \boxed{\frac{1}{2}} \frac{1}{s} + \frac{0,103}{s + 0,427} + \frac{-0,603}{s + 0,073}$$

Also follows
from the final
value theorem


$$v_o(t) = \left[\boxed{\frac{1}{2}} + 0,103e^{-0,427t} - 0,603e^{-0,073t} \right] u(t) \text{ V}$$

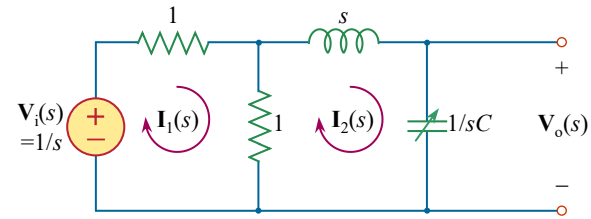

Case 3: $C = 32\text{F}$

$$e^{-at}$$


$$\frac{1}{s + a}$$

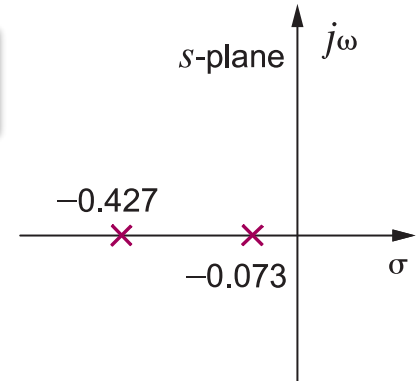

Exam exercise example

Exam(ple)

Consider the following circuit:

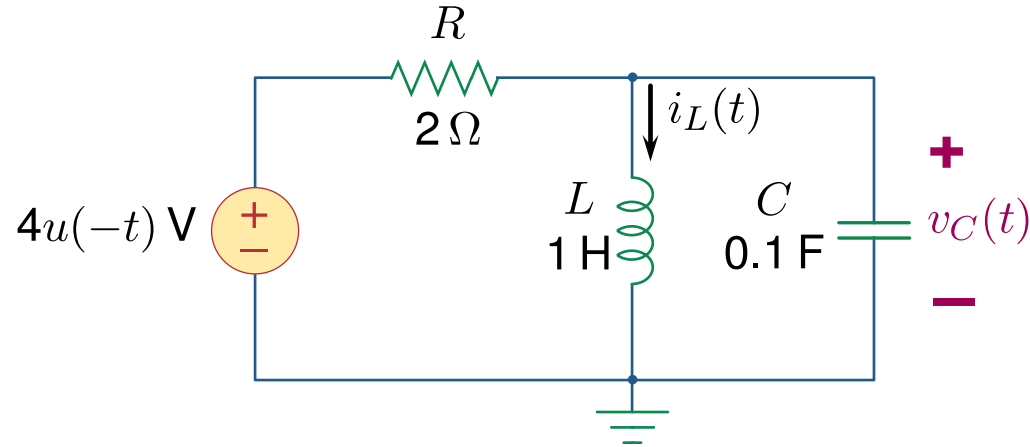

- Redraw the circuit in the s -domain.
- Determine $v_C(t)$ by means of the Laplace transform.



Exam(ple)

a) Redraw the circuit in the s -domain.

- Analyse the circuit at $t < 0$:

- $v_C(0^-) = 0 \text{ (V)}$
- $i_L(0^-) = \frac{4}{2} = 2 \text{ (A)}$

- Redraw the circuit in the s -domain.

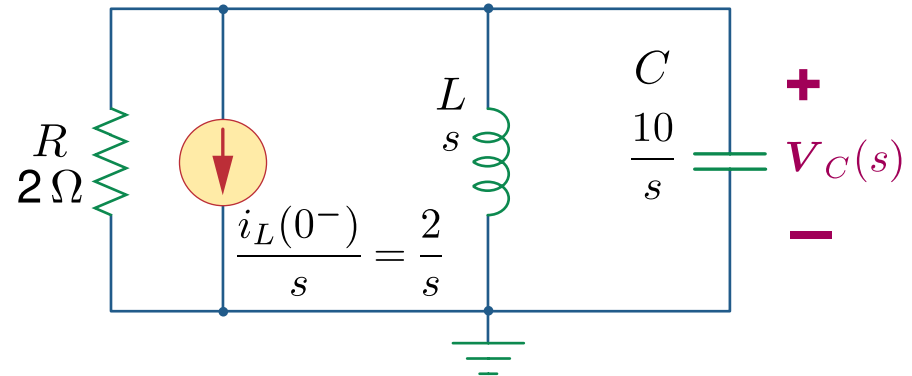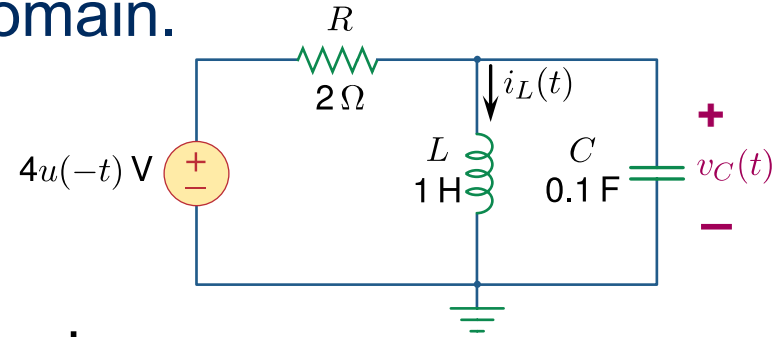

Exam(ple)


b) Determine $v_C(t)$ by means of the Laplace transform.

- Apply KCL @ A:

- $\frac{V_C}{2} + \frac{V_C}{s} + \frac{V_C}{10/s} + \frac{2}{s} = 0$

- $V_C \left(\frac{1}{2} + \frac{1}{s} + \frac{s}{10} \right) = -\frac{2}{s}$

- $V_C = -\frac{20}{s^2 + 5s + 10}$

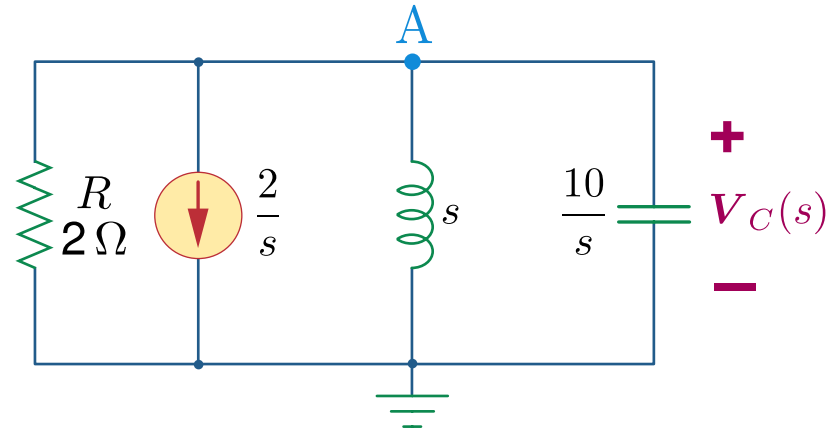

Exam(ple)

$$V_C = -\frac{20}{s^2 + 5s + 10}$$

b) Determine $v_C(t)$ by means of the Laplace transform.

- Inverse Laplace transform:

- denominator's discriminant: $\Delta = 25 - 40 < 0$

- completing the square in the denominator:

$$s^2 + 5s + 10 = (s + 2.5)^2 + 3.75 = (s + 2.5)^2 + \left(\frac{\sqrt{15}}{2}\right)^2$$

- $V_C = -\frac{20}{(s + \underbrace{2.5}_a)^2 + \left(\underbrace{\frac{\sqrt{15}}{2}}_\omega\right)^2} = -\frac{20}{\frac{\sqrt{15}}{2}} \frac{\frac{\sqrt{15}}{2}}{(s + 2.5)^2 + \left(\frac{\sqrt{15}}{2}\right)^2}$

$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	$\frac{s + a}{(s + a)^2 + \omega^2}$

Exam(ple)

$$V_C = -\frac{20}{s^2 + 5s + 10}$$

b) Determine $v_C(t)$ by means of the Laplace transform.

- Inverse Laplace transform:

- denominator's discriminant: $\Delta = 25 - 40 < 0$

- completing the square in the denominator:

$$s^2 + 5s + 10 = (s + 2.5)^2 + 3.75 = (s + 2.5)^2 + \left(\frac{\sqrt{15}}{2}\right)^2$$

$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	$\frac{s + a}{(s + a)^2 + \omega^2}$

- Inverse Laplace transform:

$$v_C(t) = -\frac{40}{\sqrt{15}} e^{-2.5t} \sin\left(\frac{\sqrt{15}}{2}t\right) u(t) \text{ (V)} = -10.33 e^{-2.5t} \sin(1.94t) u(t) \text{ (V)}$$

Summary of the day

- Equivalent circuits in the Laplace-domain
- Circuit analysis in the Laplace-domain
(actually, not new)
- Transfer functions in the Laplace-domain
(technically, not new, but new insights)

Next tasks

- Please do the SGH6
- Seminars on Tuesday and Friday
- Next week: Two-ports

Thank you!